

North South University

Department of Computer Science and Engineering


Quiz-4, Section – 5, Spring-2017

Course No: **CSE 231** Course Title: **Digital Logic Design**

Time: 20 min

Full Marks: 12

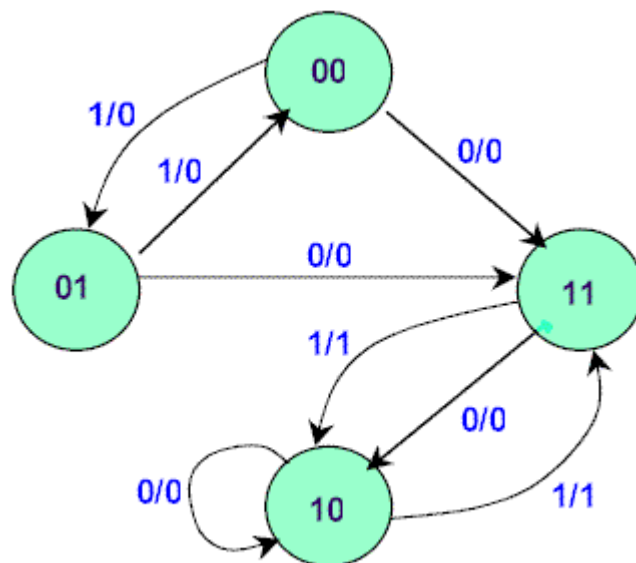- 1 a. Identify the number of states, inputs and outputs from the following state diagram 7
- b. Draw the state table based on the following state diagram
- c. How many flip flops required to implement the circuit based on this state diagram



- 2 Draw the output of the following J-K flip flop (rising edge type). You can assume the initial value of Q = 0 5

