



**North South University**  
Department of Electrical & Computer Engineering

**LAB REPORT**

Course Name: **CSE231L**

Experiment Number: 08

Experiment Name: **Synchronous Sequential Circuits**

Experiment Date: 03/01/2021

Report Submission Date: 09/01/2021

Section:

Student Name: Zahid Hasan

Score

Student ID: 1911509642

Remarks:

## **LAB-08: Synchronous Sequential Circuits**

### **Objectives:**

- Gain a practical understanding of State Diagrams and State Tables.
- Understand the concept of designing Sequential Circuits using Flip-Flops.
- Design and implement a Synchronous Sequential Circuit given a State Diagram.

### **Apparatus:**

- IC 7474 (Dual D Flip-Flops)
- IC 74107 (Dual JK Flip-Flops)
- IC 7408 2-input AND gates
- IC 7404 Hex inverters (NOT gates)
- IC 7432 2-input OR gates

### **Theory:**

#### **Synchronous Sequential Circuits:**

Sequential Circuit is made of combinational circuits and memory storage where circuits conduct the operation of present output based on present inputs and past outputs stored in memory storage. In a sequential circuit, the values of the outputs depend on the past behavior of the circuit, as well as the present values of its inputs. A sequential circuit has states, which in conjunction with the present values of inputs determine its behavior. Sequential circuits can be Synchronous where flip-flops are used to implement the states, and a clock signal is used to control the operation.

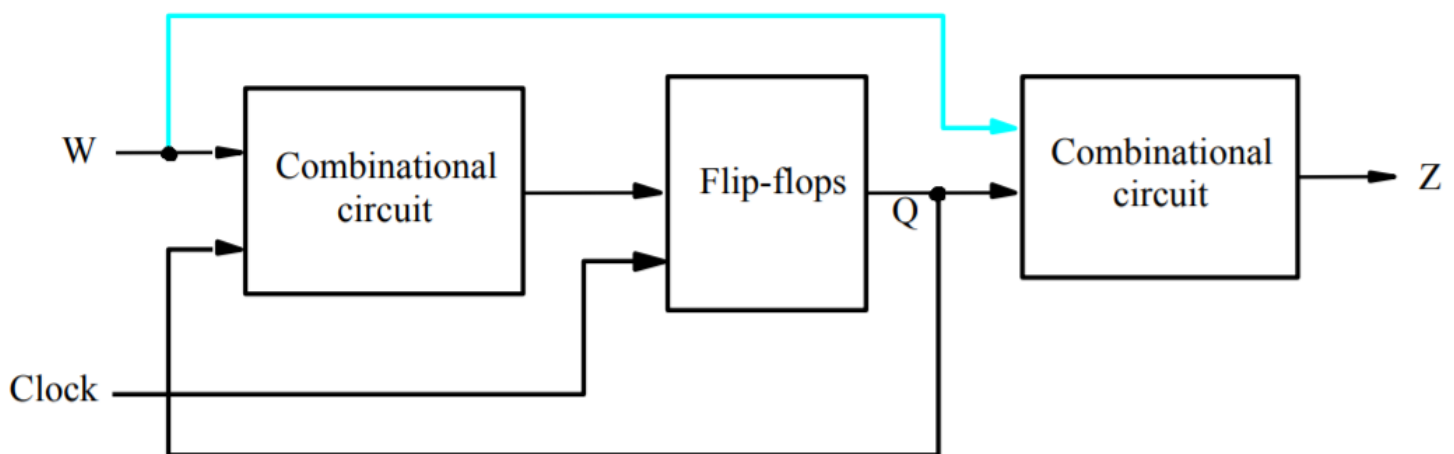


Figure: The general form of a synchronous sequential circuit.

### State Table:

The state table representation of a sequential circuit consists of three sections labeled present state, next state and output. The present state designates the state of flip-flops before the occurrence of a clock pulse. The next state shows the states of flip-flops after the clock pulse, and the output section lists the value of the output variables during the present state.

### State Diagram:

In addition to graphical symbols, tables or equations, flip-flops can also be represented graphically by a state diagram. In this diagram, a state is represented by a circle, and the transition between states is indicated by directed lines (or arcs) connecting the circles.

### Circuit Diagram:

#### Experiment-1:

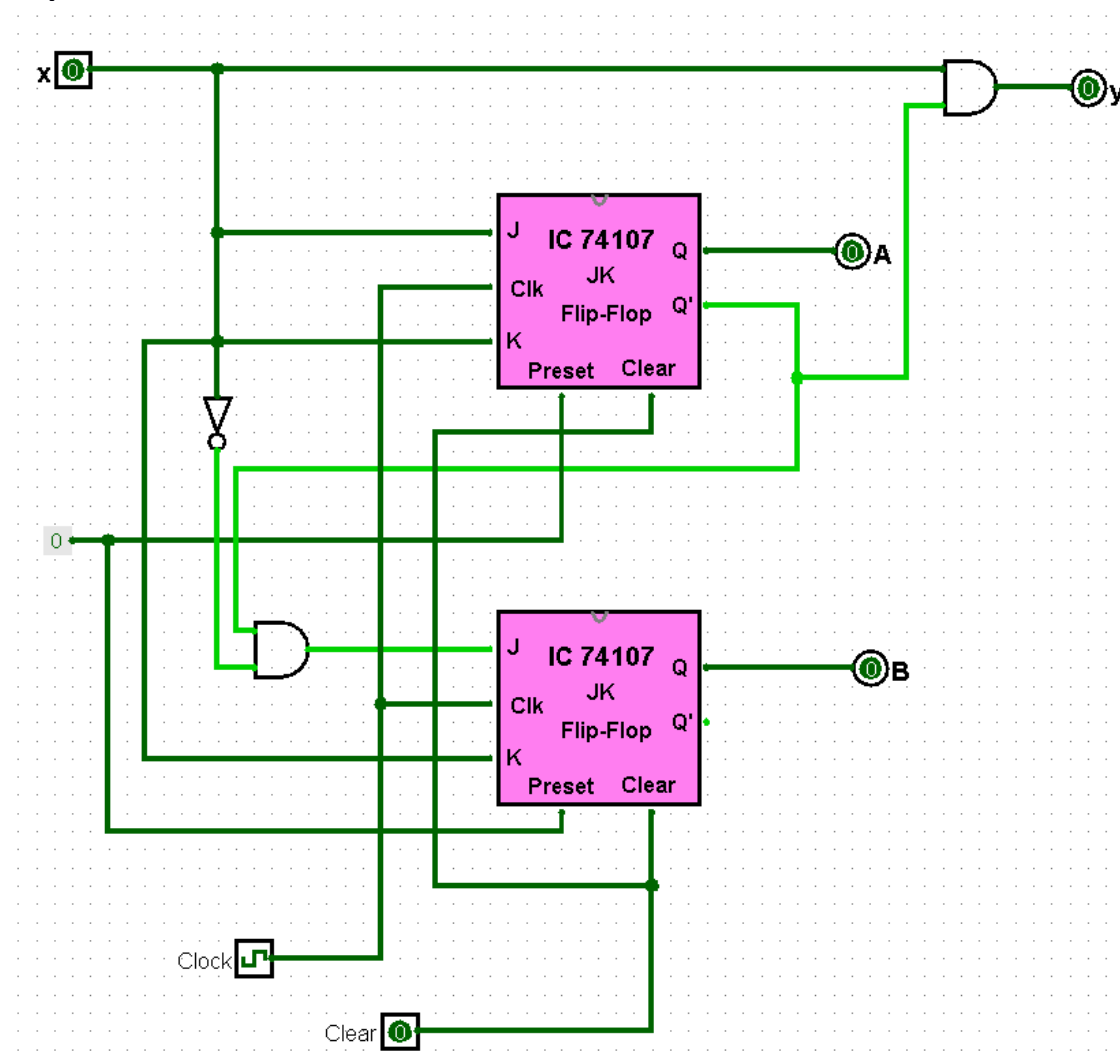


Figure F1: Constructing a Sequential Circuit using JK Flip-Flop.

## Experiment-2:

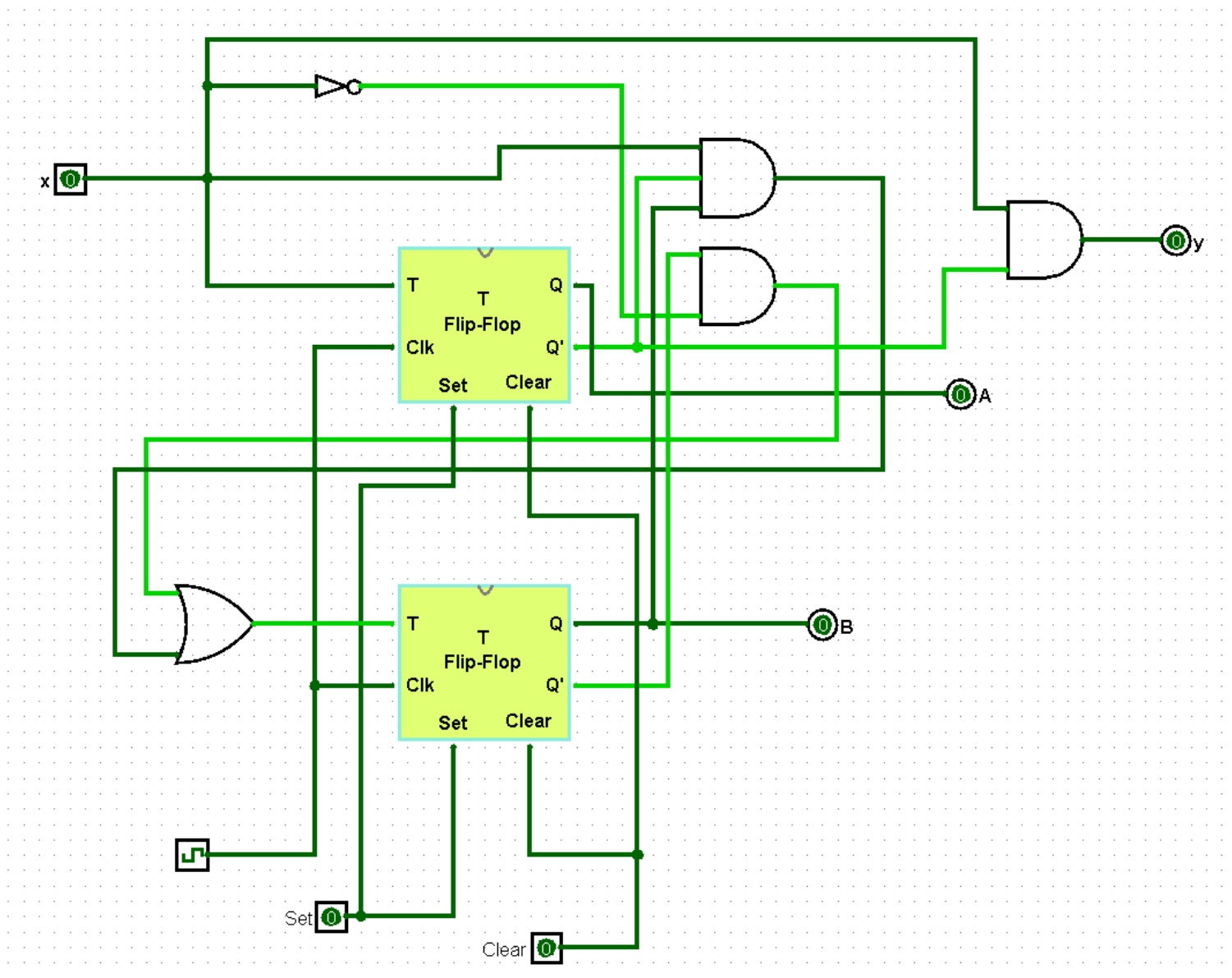


Figure F2: Constructing a Sequential Circuit using **T Flip-Flop**.

### Experiment-3:

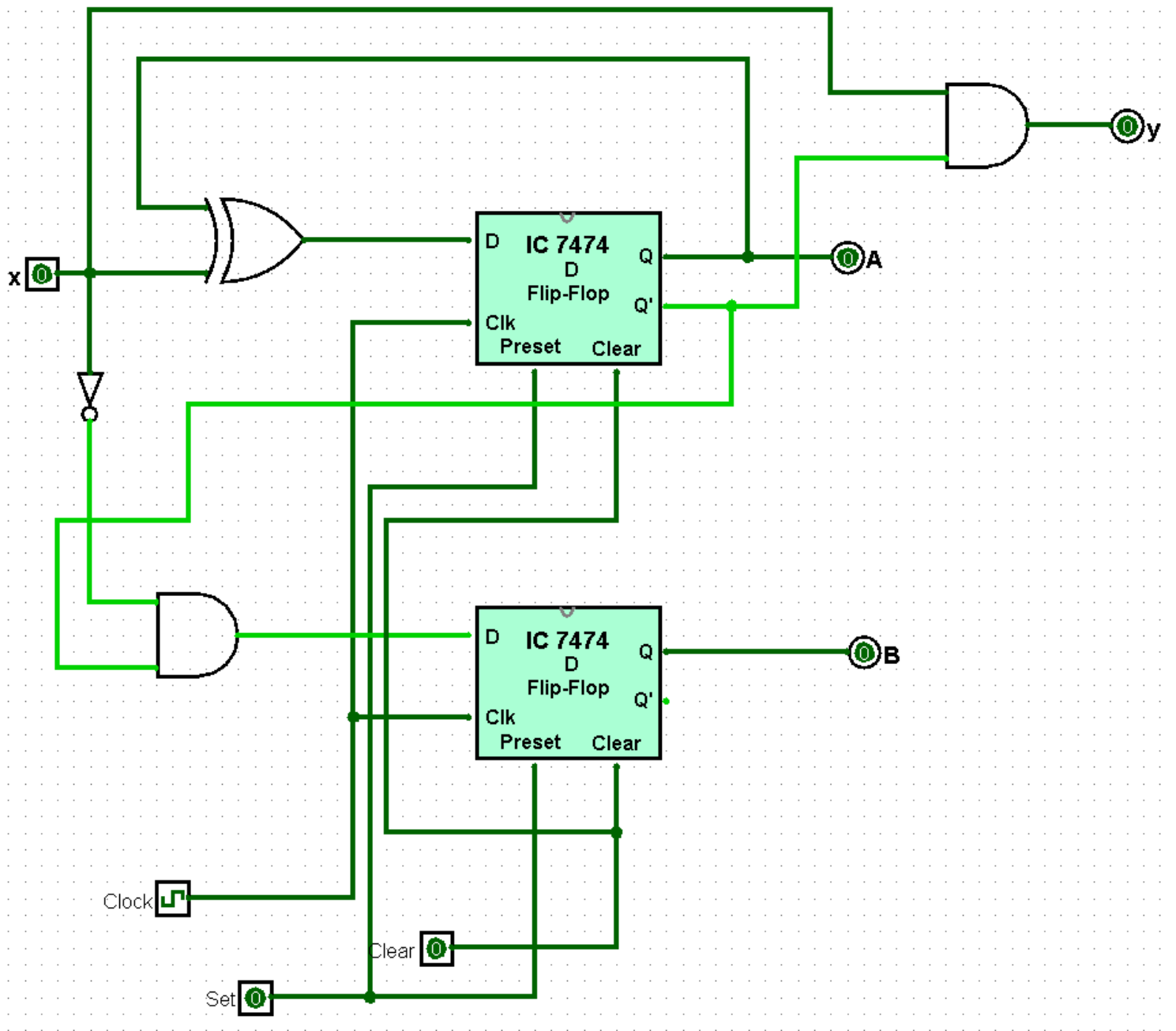


Figure F3: Constructing a Sequential Circuit using D Flip-Flop.

### Data Table:

Experiment-1: Table 01: State table for circuit using **JK Flip-Flop**.

Present state		Input	Next state		Output	Flip-flop input functions			
A	B	X	A	B	Y	J <sub>A</sub>	K <sub>A</sub>	J <sub>B</sub>	K <sub>B</sub>
0	0	0	0	1	0	0	X	1	X
0	0	1	1	0	1	1	X	0	X
0	1	0	0	1	0	0	X	X	0
0	1	1	1	0	1	1	X	X	1
1	0	0	1	0	0	X	0	0	X
1	0	1	0	0	0	X	1	0	X
1	1	0	X	X	X	X	X	X	X
1	1	1	X	X	X	X	X	X	X

0	0	X	X
1	1	X	X

$$J_A = X$$

X	X	0	X
X	X	1	X

$$K_A = X$$

1	X	0	X
0	X	0	X

$$J_B = X'A'$$

X	0	X	X
X	1	X	X

$$K_B = X$$

0	0	0	X
1	1	0	X

$$Y = XA'$$

Experiment-2: Table 02: State table for circuit using **T Flip-Flop**.

Present state		Input	Next state		Output	Flip-flop input functions	
A	B	X	A	B	Y	T <sub>A</sub>	T <sub>B</sub>
0	0	0	0	1	0	0	1
0	0	1	1	0	1	1	0
0	1	0	0	1	0	0	0
0	1	1	1	0	1	1	1
1	0	0	1	0	0	0	0
1	0	1	0	0	0	1	0
1	1	0	X	X	X	X	X
1	1	1	X	X	X	X	X

0	0	0	X
1	1	1	X

$$T_A = X$$

1	0	0	X
0	1	0	X

$$T_B = XA'B + X'B'$$

0	0	0	X
1	1	0	X

$$Y = XA'$$

Experiment-3: Table 03: State table for circuit using D Flip-Flop.

Present state		Input	Next state		Output	Flip-flop input functions	
A	B	X	A	B	Y	D <sub>A</sub>	D <sub>B</sub>
0	0	0	0	1	0	0	1
0	0	1	1	0	1	1	0
0	1	0	0	1	0	0	1
0	1	1	1	0	1	1	0
1	0	0	1	0	0	1	0
1	0	1	0	0	0	0	0
1	1	0	X	X	X	X	X
1	1	1	X	X	X	X	X

0	0	1	X
1	1	0	X

$$D_A = XA' + X'A$$

1	1	0	X
0	0	0	X

$$D_B = X'A'$$

0	0	0	X
1	1	0	X

$$Y = XA'$$


## Question and Answer:

### Experiment-2:

**Ques-01:** Reason behind the output  $y$  equation of JK and T be the same

**ANS:** from given state diagram, the obtained output values of  $y$  depend on the flip-flop output and external input for both JK flip-flop and T flip-flop. As the values of external output  $y$  is same for JK flip-flop and T flip-flop, the output equation obtained from k-map will also be same.
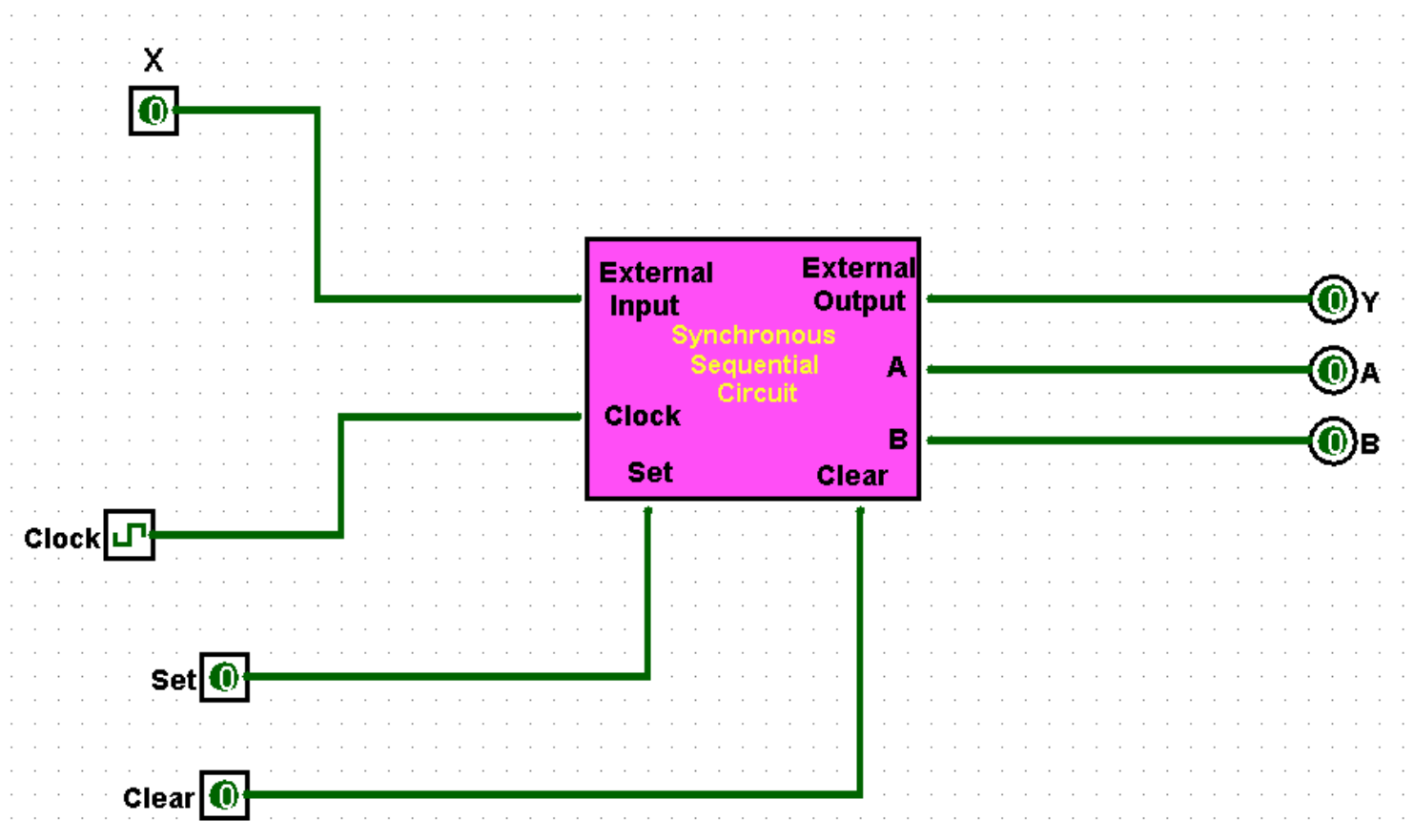
### Experiment-3: IC Diagram for the logic circuit in T Flip-Flop





**Discussion:**

The overall lab experiment was about the implementation of synchronous sequential circuit using different types of flip-flops.

At the beginning of the experiment, I implemented the synchronous sequential circuit using JK flip-flop. At first, from given state diagram, I had to complete the state table with next state values and external output values. Then using Karnaugh map built from state table, I got required state equations. Using these state equations, I constructed the sequential circuit.

Then I constructed synchronous sequential circuit using D flip-flop and T flip-flop as same as did for JK flip-flop.

Additionally, I did the implementation with basic logic gate ICs and T flip-flop.

During experiment, Logisim worked properly.

Above all, from the experiment, I learned how to implement the synchronous sequential circuit using JK, D, T flip-flops.