

# North South University

Department of Computer Science and Engineering

Quiz-4, Section – 4, Spring-2017

Course No: **CSE 231** Course Title: **Digital Logic Design**

Time:20 min

Full Marks:12

- 1 a. Draw the state diagram from the following state table 7
- b. How many different states are there into this state table?
- c. How many flip flops you need to implement the circuit based on this state table?

Present State		Input	Next State		Output
<b>A</b>	<b>B</b>	<b>x</b>	<b>A</b>	<b>B</b>	<b>y</b>
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

- 2 Draw the output of the following J-K flip flop (rising edge type). You can assume the initial value of Q =0 5

