 


Combinational Logic Design

**Dept. of Electrical Engineering and
Computer Science
North South University**

Combinational Logic

- Logic circuits for digital systems may be
combinational
sequential
- A combinational circuit consists of input variables, logic gates, and output variables.



Analysis procedure


- To obtain the output Boolean functions from a logic diagram, proceed as follows:
 1. Label all gate outputs that are a function of input variables with arbitrary symbols. Determine the Boolean functions for each gate output.
 2. Label the gates that are a function of input variables and previously labeled gates with other arbitrary symbols. Find the Boolean functions for these gates.
 3. Repeat the process outlined in step 2 until the outputs of the circuit are obtained.
 4. By repeated substitution of previously defined functions, obtain the output Boolean functions in terms of input variables.

Example

$$F_2 = AB + AC + BC; \quad T_1 = A + B + C; \quad T_2 = ABC; \quad T_3 = F_2' T_1;$$

$$F_1 = T_3 + T_2$$
 
$$F_1 = T_3 + T_2 = F_2' T_1 + ABC = A'BC' + A'B'C + AB'C' + ABC$$



Combinational Logic Design

- A process with 5 steps
 - Specification
 - Formulation
 - Optimization
 - Technology mapping
 - Verification
- 1st three steps and last best illustrated by example

Specifications

- Write a specification for the circuits
- Specification includes
 - What are the inputs: how many, how many bits in a given output, how are they grouped,, are they control, are they active high?
 - What are the outputs: how many and how many bits in a each, active high, active low, tristate output?
 - The functional operation that takes place in the chip, i.e., for given inputs what will appear on the outputs.

Formulation step

- Convert the specifications into a variety forms for optimal implementation.
 - Possible forms
 - Truth Tables
 - Expressions
 - K-maps
 - Binary Decision Diagrams
- IF THE SPECIFICATION IS ERRONOUS OR INCOMPLETE (open for various interpretation) then the circuit will perform as specified but will not perform as desired.

Last 3 steps

- Best illustrated by example
 - A BCD to Excess-3 code converter
 - BCD-to-7-segment decoder

BCD-to-Excess-3 Code converter

- BCD is a code for the decimal digits 0-9
- Excess-3 is also a code for the decimal digits

Decimal Digit	Input BCD	Output Excess-3
0	0 0 0 0	0 0 1 1
1	0 0 0 1	0 1 0 0
2	0 0 1 0	0 1 0 1
3	0 0 1 1	0 1 1 0
4	0 1 0 0	0 1 1 1
5	0 1 0 1	1 0 0 0
6	0 1 1 0	1 0 0 1
7	0 1 1 1	1 0 1 0
8	1 0 0 0	1 0 1 1
9	1 0 0 1	1 1 0 0

Design Procedure for BCD-to-Excess3

- **Specification:**

- Inputs: a BCD input, A,B,C,D with A as the most significant bit and D as the least significant bit.
- Outputs: an Excess-3 output W,X,Y,Z that corresponds to the BCD input.
- Internal operation – circuit to do the conversion in combinational logic.

- **Formulation**

- Excess-3 code is easily formed by adding a binary 3 to the binary or BCD for the digit.
- There are 16 possible inputs for both BCD and Excess-3.
- It can be assumed that only valid BCD inputs will appear so the six combinations not used can be treated as don't cares. 10

Optimization – BCD-to-Excess-3

Lay out K-maps for each output, W X Y Z

W

		C			
		D		C	
		00	01	11	10
A	B	00			
	01		1	1	1
	11	X	X	X	X
	10	1	1	X	X

Groupings:
 - A group of 4 (rows 11, 10)
 - B group of 4 (columns 01, 11, 10)
 - D group of 4 (columns 00, 01, 11, 10)

X

		C			
		D		C	
		00	01	11	10
A	B	00		1	1
	01	1			
	11	X	X	X	X
	10		1	X	X

Groupings:
 - A group of 4 (rows 11, 10)
 - B group of 4 (columns 01, 11, 10)
 - D group of 4 (columns 00, 01, 11, 10)

Y

		C			
		D		C	
		00	01	11	10
A	B	00	1		1
	01	1		1	
	11	X	X	X	X
	10	1		X	X

Groupings:
 - A group of 4 (rows 11, 10)
 - B group of 4 (columns 01, 11, 10)
 - D group of 4 (columns 00, 01, 11, 10)

Z

		C			
		D		C	
		00	01	11	10
A	B	00	1		1
	01	1			1
	11	X	X	X	X
	10	1		X	X


Groupings:
 - A group of 4 (rows 11, 10)
 - B group of 4 (columns 01, 11, 10)
 - D group of 4 (columns 00, 01, 11, 10)

Expressions for W X Y Z

- $W(A,B,C,D) = \sum m(5,6,7,8,9) + d(10,11,12,13,14,15)$
- $X(A,B,C,D) = \sum m(1,2,3,4,9) + d(10,11,12,13,14,15)$
- $Y(A,B,C,D) = \sum m(0,3,4,7,8) + d(10,11,12,13,14,15)$
- $Z(A,B,C,D) = \sum m(0,2,4,6,8) + d(10,11,12,13,14,15)$

Minimize K-Maps


K-map for Y

 

- Y minimization

$$Y = CD + C'D'$$

K-map for Z

 


- Z minimization

$$Z = D'$$

Minimize K-Maps


K-map for W

 

- W minimization

$$W = A + BC + BD$$

K-map for X

 

- X minimization

$$X = BC'D' + B'C + B'D$$

Two level circuit implementation

- Have equations

$$W = A + BC + BD = A + B(C+D)$$

$$X = B'C + B'D + BC'D' = B'(C+D) + BC'D'$$

$$Y = CD + C'D'$$

$$Z = D'$$

- Factoring out (C+D) and call it T
- Then $T' = (C+D)' = C'D'$


$$W = A + BT$$

$$X = B'T + BT'$$

$$Y = CD + T'$$

$$Z = D'$$

Create the digital circuit

 


- Implementing the second set of equations where $T=C+D$ results in a lower gate count.
- This gate has a fanout of 3

BCD-to-Seven-Segment Decoder

- **Specification**

 - Digital readouts on many digital products often use LED seven-segment displays.
- Each digit is created by lighting the appropriate segments. The segments are labeled a,b,c,d,e,f,g
- The decoder takes a BCD input and outputs the correct code for the seven-segment display.



- **Formulation**

- Input: A 4-bit binary value that is a BCD coded input.
- Outputs: 7 bits, a through g for each of the segments of the display.
- Operation: Decode the input to activate the correct segments.

Formulation

- Construct a truth table

Decimal Digit	Input BCD	Seven-Segment Decoder Outputs						
		a	b	c	d	e	f	g
0	0 0 0 0	1	1	1	1	1	1	0
1	0 0 0 1	0	1	1	0	0	0	0
2	0 0 1 0	1	1	0	1	1	0	1
3	0 0 1 1	1	1	1	1	0	0	1
4	0 1 0 0	1	0	1	1	0	1	1
5	0 1 0 1	1	0	1	1	0	1	1
6	0 1 1 0	1	0	1	1	1	1	1
7	0 1 1 1	1	1	1	0	0	0	0
8	1 0 0 0	1	1	1	1	1	1	1
9	1 0 0 1	1	1	1	1	0	1	1
All other inputs		0	0	0	0	0	0	0

Optimization

- Create a K-map for each output and get

$$a = A'C + A'BD + B'C'D' + AB'C'$$

$$b = A'B' + A'C'D' + A'CD + AB'C'$$

$$c = A'B + A'D + B'C'D' + AB'C'$$

$$d = A'CD' + A'B'C + B'C'D' + AB'C' + A'BC'D$$

$$e = A'CD' + B'C'D'$$

$$f = A'BC' + A'C'D' + A'BD' + AB'C'$$

$$g = A'CD' + A'B'C + A'BC' + AB'C'$$

Note on implementation



- Direct implementation would require 27 AND gates and 7 OR gates
- By sharing terms, can actualize and implementation with 14 less gates.
- Normally decoder in a device name indicates that the number of outputs is less than the number of inputs.

Binary Adder-Subtractor

- A combinational circuit that performs the addition of two bits is called a **half adder**.
- The truth table for the half adder is listed below:

Truth Table – Half Adder

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

  

Full-Adder

- Performs the addition of three bits (two significant bits and a previous carry)

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

S

	YZ	00	01	11	10
X	0		1		1
	1	1		1	


$$\begin{aligned}
 S &= X' Y' Z + X' Y Z' + X Y' Z' + X Y Z \\
 &= X \oplus Y \oplus Z \\
 &= (X \oplus Y) \oplus Z
 \end{aligned}$$

C


	YZ	00	01	11	10
X	0			1	
	1		1	1	1

$$\begin{aligned}
 C &= XY + XY' Z + X' YZ \\
 &= XY + Z (XY' + X' Y) \\
 &= XY + Z (X \oplus Y)
 \end{aligned}$$

Full adder Implementation

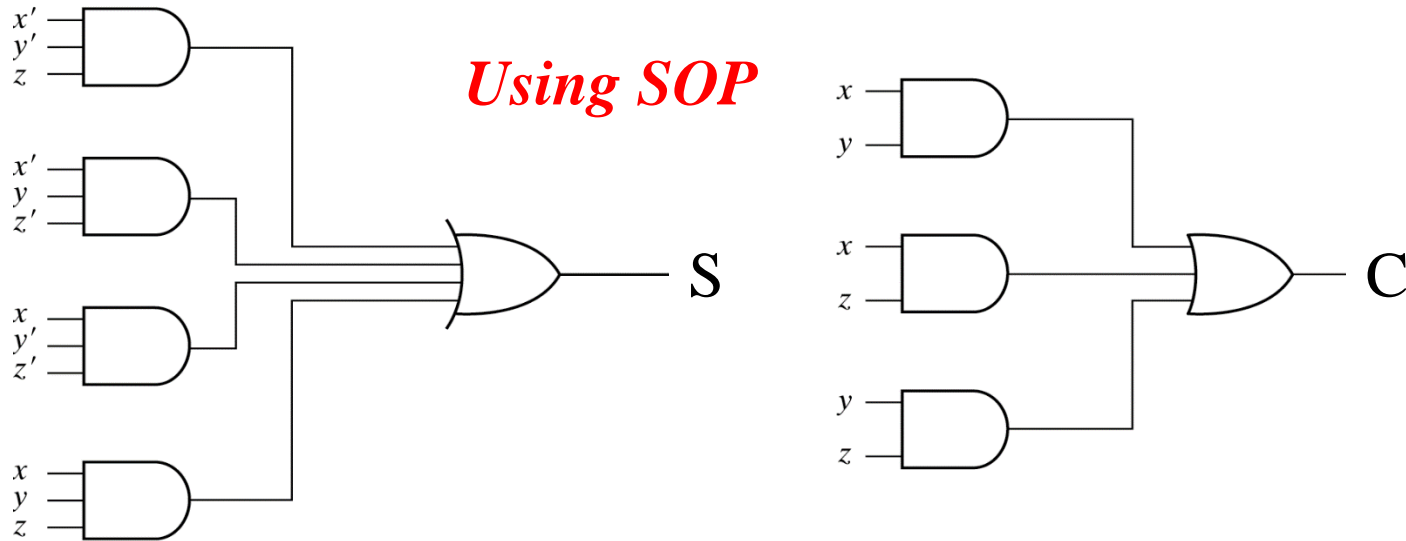


 Using two half adders and one OR gate (Carry Look-Ahead adder)



Full Adder Symbol

 - For a multibit implementation need a symbol for the unit. And then can use that symbol in multi-bit or hierarchical representations.




Binary adder

Ripple Carry Adder (RCA): full adders are connected in cascade.

All inputs, A_s , B_s , and C_0 arrive \rightarrow C_1 becomes valid \rightarrow C_2 becomes valid \rightarrow C_3 becomes valid \rightarrow C_4 becomes valid

Subscript i :	3	2	1	0	
Input carry	0	1	1	0	C_i
Augend	1	0	1	1	A_i
Addend	0	0	1	1	B_i
Sum	1	1	1	0	S_i
Output carry	0	0	1	1	C_{i+1}

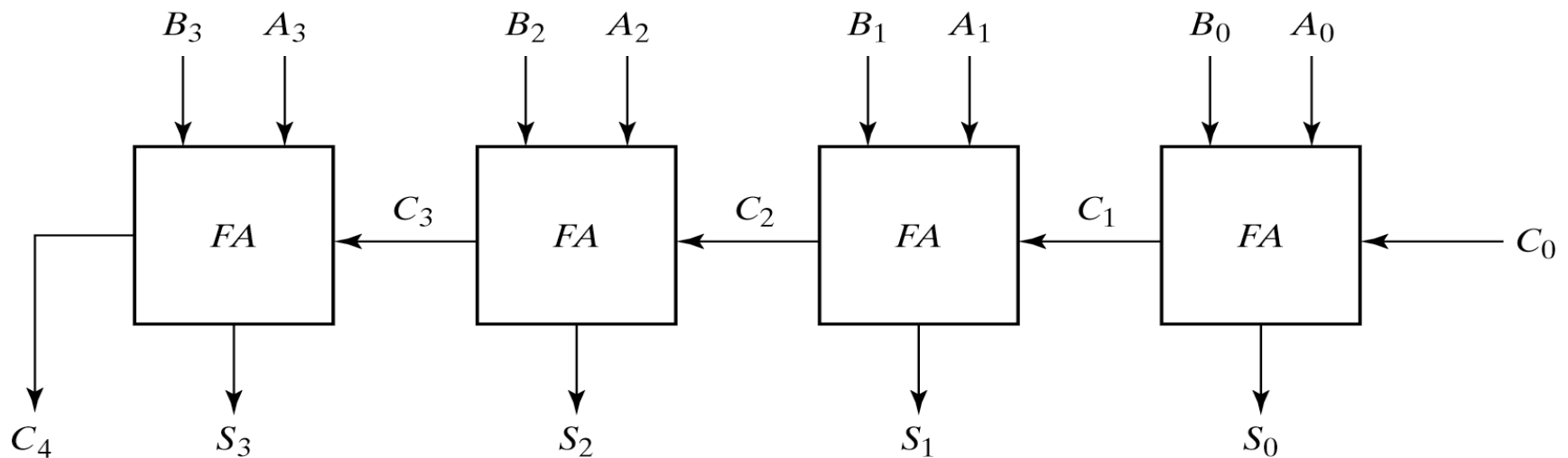


Carry Propagation

- Causes a **unstable** factor on **carry bit**, and produces a **longest propagation delay**.
- The signal from C_i to the output carry C_{i+1} , **propagates through an AND and OR gates**, so, for an n-bit RCA, there are **$2n$** gate levels for the carry to propagate from input to output.

Carry Propagation

 - Because the propagation delay will affect the output signals on different time, so the signals are given enough time to get the precise and stable outputs.
- The most widely used technique employs the principle of **carry look-ahead** to improve the speed of the algorithm.



Boolean functions of CLA-Adder

$$P_i = A_i \oplus B_i \quad \text{steady state value}$$

$$G_i = A_i B_i \quad \text{steady state value}$$

Output sum and carry

$$S_i = P_i \oplus C_i$$

$$C_{i+1} = G_i + P_i C_i$$

G_i : carry generate P_i : carry propagate

C_0 = input carry

$$C_1 = G_0 + P_0 C_0$$


$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$

- C_3 does not have to wait for C_2 and C_1 to propagate.


Logic Diagram of CLA Generator

 - C_3 is propagated at the same time as C_2 and C_1 .




4-bit CLA-Adder

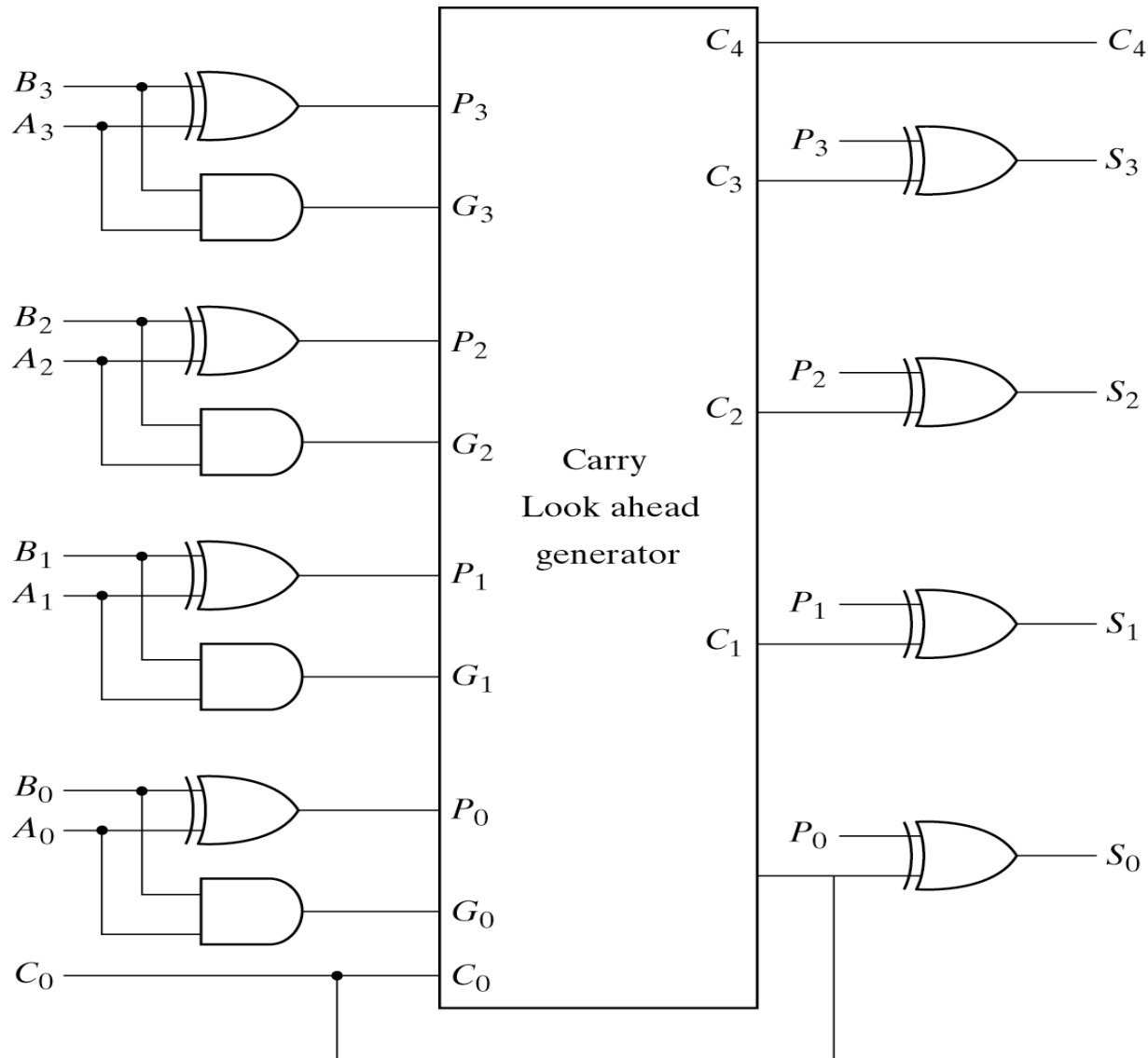- Delay time of n-bit CLAA = XOR + (AND + OR) + XOR



Binary Adder-Subtractor

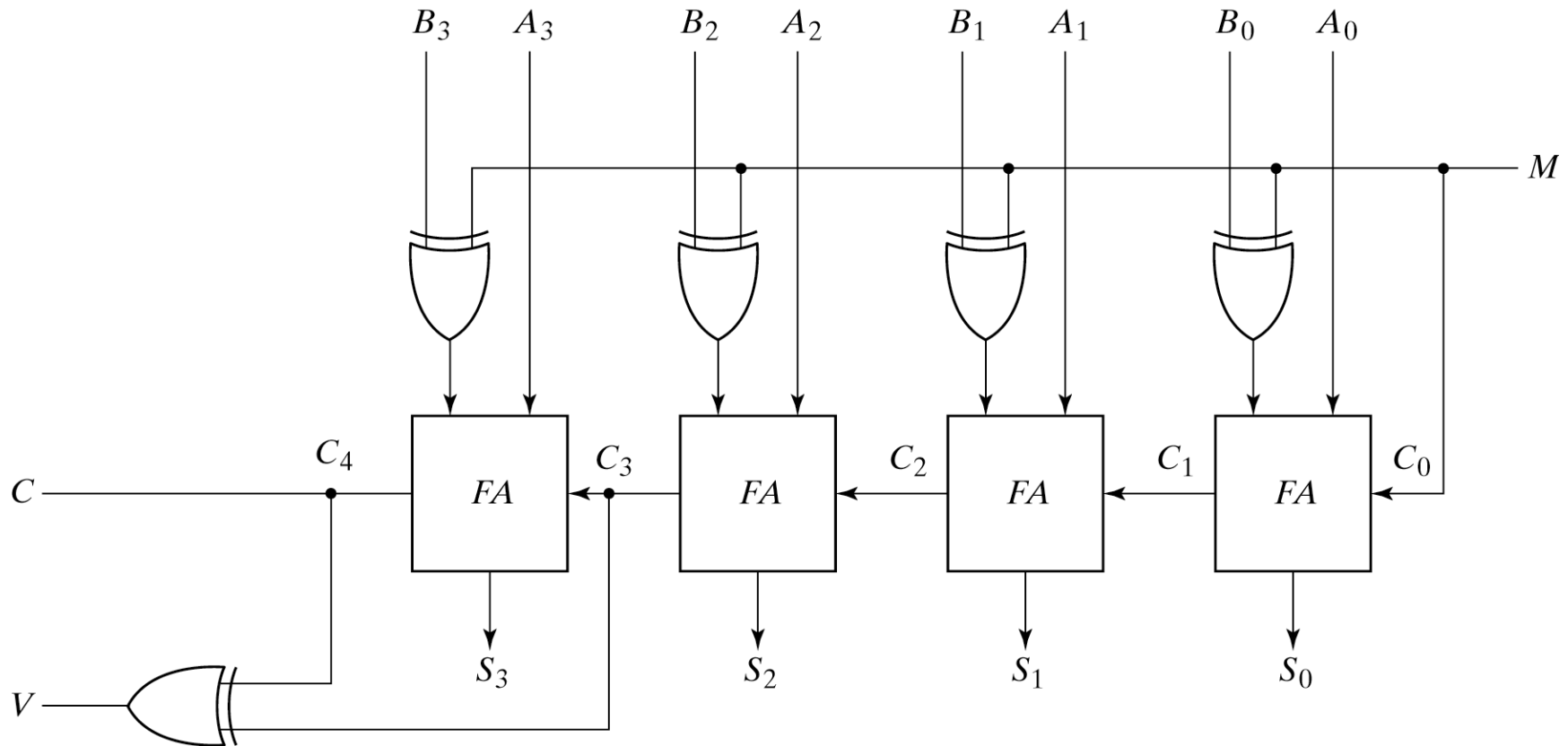$M = 1 \rightarrow$ subtractor ; $M = 0 \rightarrow$ adder



Overflow on signed and unsigned

- Binary numbers in the **signed-complement system** are added and subtracted by the same basic addition and subtraction rules as **unsigned numbers**.
- Overflow is a problem in digital computers because the number of bits that hold the number is finite and a result that contains $n+1$ bits cannot be accommodated.
- When two **unsigned** numbers are added, an overflow is detected from the **end carry out of the MSB position**.
- When two **signed** numbers are added, the sign bit is treated as part of the number and the end carry does not indicate an overflow.
- An **overflow can't occur** after an addition if one number is **positive** and the other is **negative**.
- An overflow may occur if the two numbers added are both positive or both negative.

Overflow indication.

- In 8-bit 2's complement notation the range that can be represented is -127 to +127.
- Then the operation to add +70 to +80 is

Carries	0	1		
+70	0	100	0110	
+80	0	101	0000	
+150	1	001	0110	


- Also look at the addition of -70 and -80

The other addition

- The addition of -70 and -80

Carries	1	0		
-70	1	011	1010	
-80	1	011	0000	
<hr/>				
-150	0	110	1010	

 - The rule – if the carry into the msb position differs from the carry out from the msb position then an overflow has occurred.



Decimal adder

BCD adder can't exceed 9 on each input digit. K is the carry.

Table 4-5
Derivation of BCD Adder

Binary Sum					BCD Sum					Decimal
K	Z ₈	Z ₄	Z ₂	Z ₁	C	S ₈	S ₄	S ₂	S ₁	
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	2
0	0	0	1	1	0	0	0	1	1	3
0	0	1	0	0	0	0	1	0	0	4
0	0	1	0	1	0	0	1	0	1	5
0	0	1	1	0	0	0	1	1	0	6
0	0	1	1	1	0	0	1	1	1	7
0	1	0	0	0	0	1	0	0	0	8
0	1	0	0	1	0	1	0	0	1	9
0	1	0	1	0	1	0	0	0	0	10
0	1	0	1	1	1	0	0	0	1	11
0	1	1	0	0	1	0	0	1	0	12
0	1	1	0	1	1	0	0	1	1	13
0	1	1	1	0	1	0	1	0	0	14
0	1	1	1	1	1	0	1	0	1	15
1	0	0	0	0	1	0	1	1	0	16
1	0	0	0	1	1	0	1	1	1	17
1	0	0	1	0	1	1	0	0	0	18
1	0	0	1	1	1	1	0	0	1	19


Rules of BCD adder

- When the binary sum is **greater than 1001**, we obtain a **non-valid BCD** representation.
- The **addition of binary 6(0110)** to the binary sum **converts it to the correct BCD** representation and also produces an output carry as required.
- To distinguish them from binary 1000 and 1001, which also have a 1 in position Z_8 , we specify further that either Z_4 or Z_2 must have a 1.

$$C = K + Z_8Z_4 + Z_8Z_2$$


Implementation of BCD adder

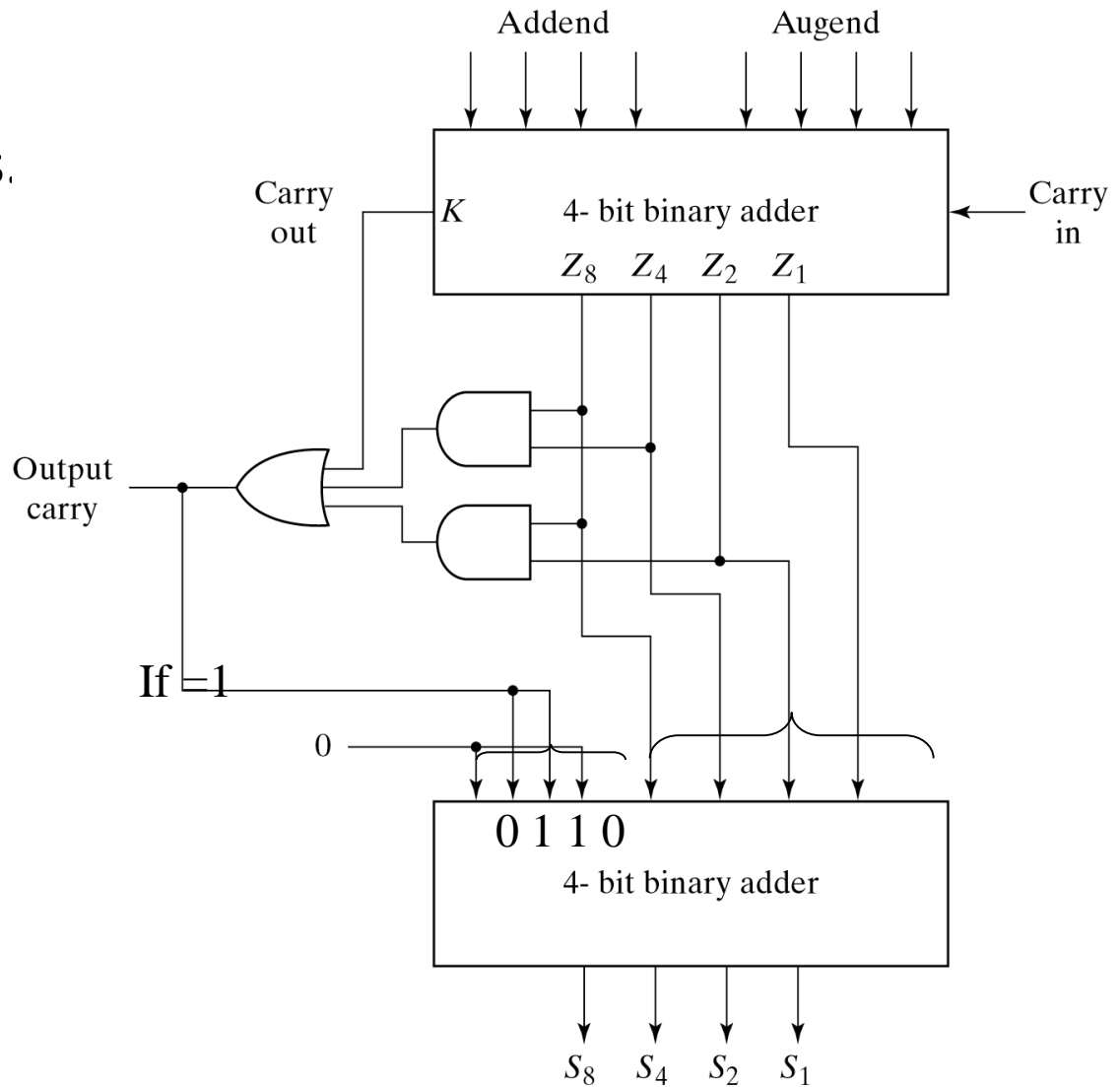- A decimal parallel adder that adds n decimal digits needs n BCD adder stages.
- The **output carry from one stage** must be **connected** to the input carry of the next higher-order stage.




Binary multiplier

 - Usually there are **more bits** in the partial products and it is necessary to use **full adders** to produce the sum of the partial products.



4-bit by 3-bit binary multiplier

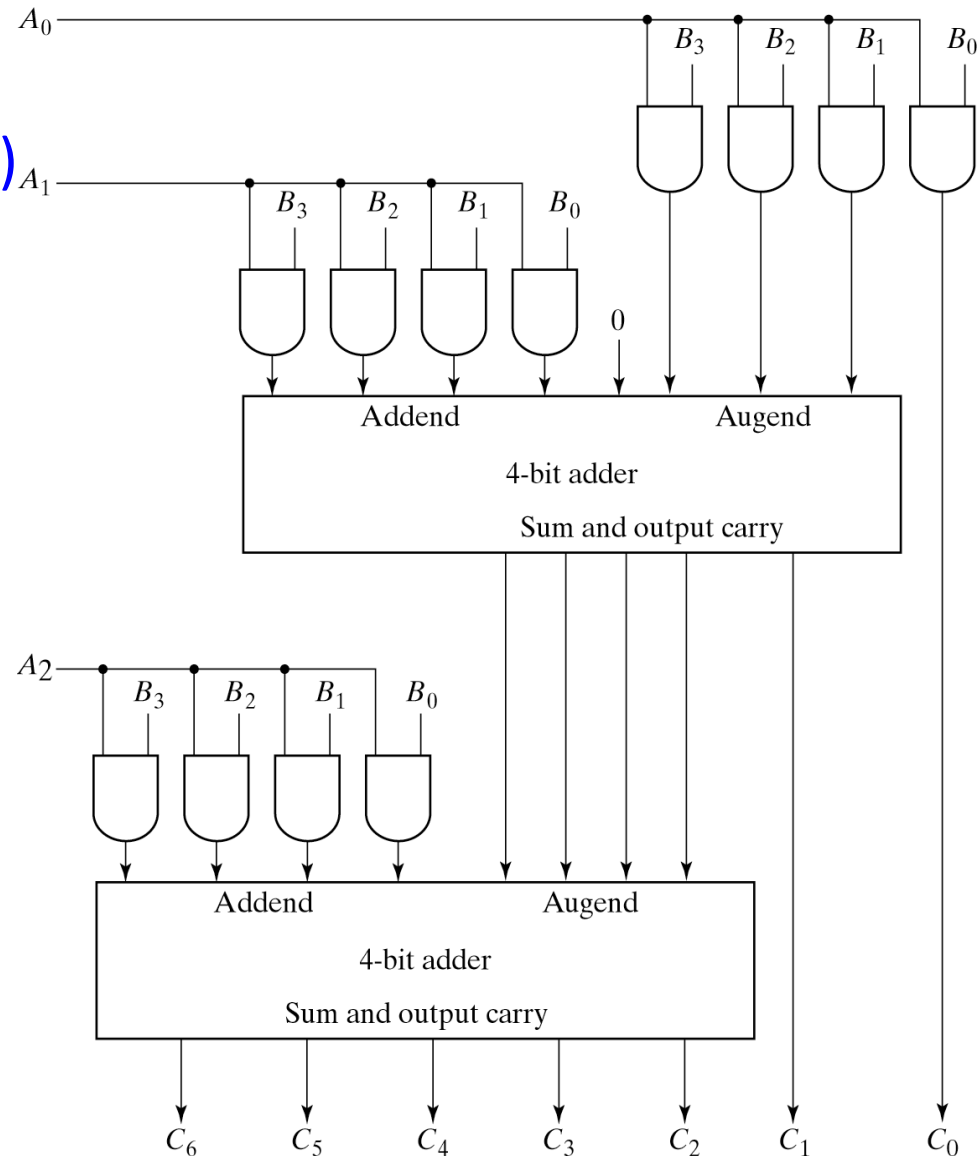- For J multiplier bits and K multiplicand bits we need $(J \times K)$ AND gates and $(J - 1)$ K -bit adders to produce a product of $J+K$ bits.
- $K=4$ and $J=3$, we need 12 AND gates and two 4-bit adders.




Magnitude comparator

- The equality relation of each pair of bits can be expressed logically with an exclusive-NOR function as:

$$A = A_3A_2A_1A_0 ; B = B_3B_2B_1B_0$$

$$x_i = A_iB_i + A_i'B_i' \quad \text{for } i = 0, 1, 2, 3$$

$$(A = B) = x_3x_2x_1x_0$$

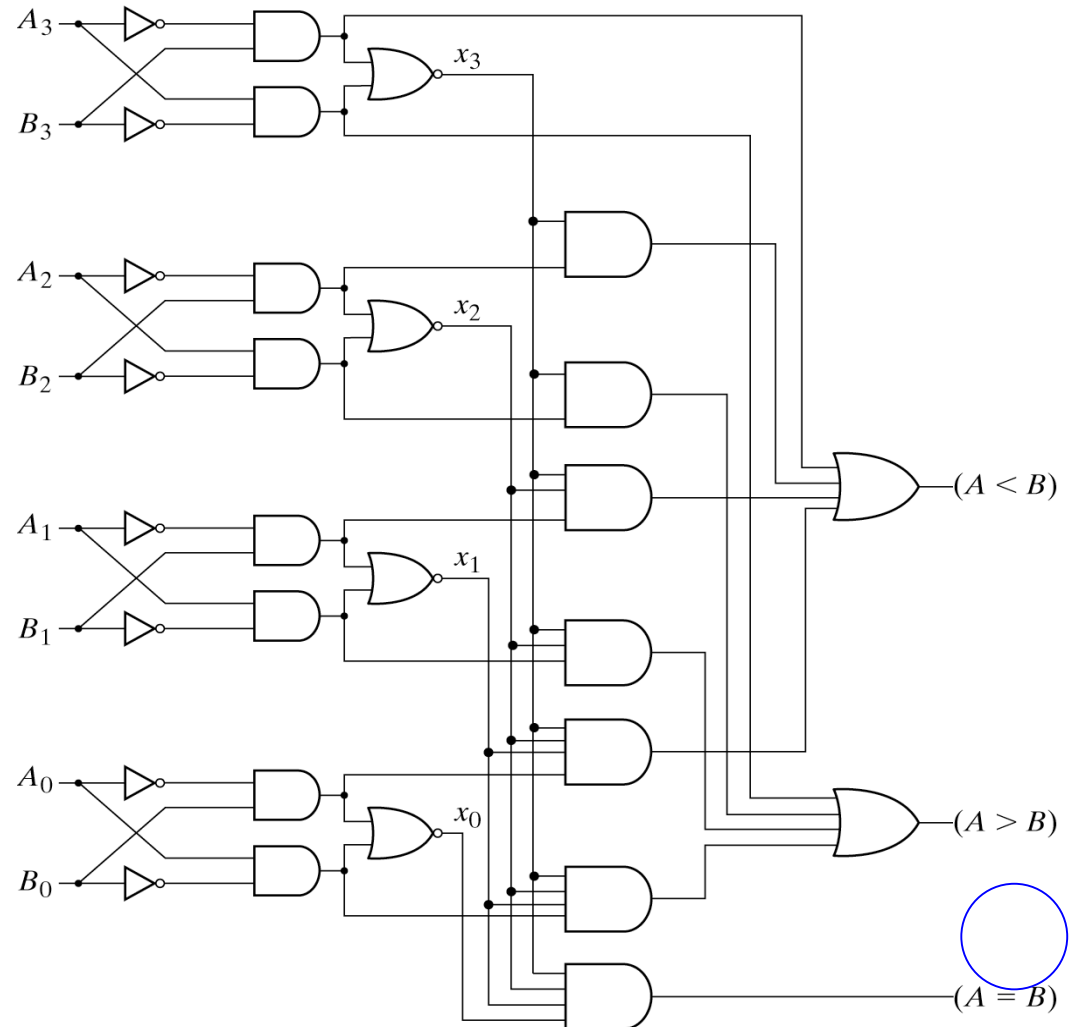

Magnitude comparator


- We inspect the relative magnitudes of pairs of MSB. If equal, we compare the next lower significant pair of digits until a pair of unequal digits is reached.
- If the corresponding digit of A is 1 and that of B is 0, we conclude that $A > B$.

$(A > B) =$

$$A_3B'_3 + x_3A_2B'_2 + x_3x_2A_1B'_1 + x_3x_2x_1A_0B'_0$$

$(A < B) =$
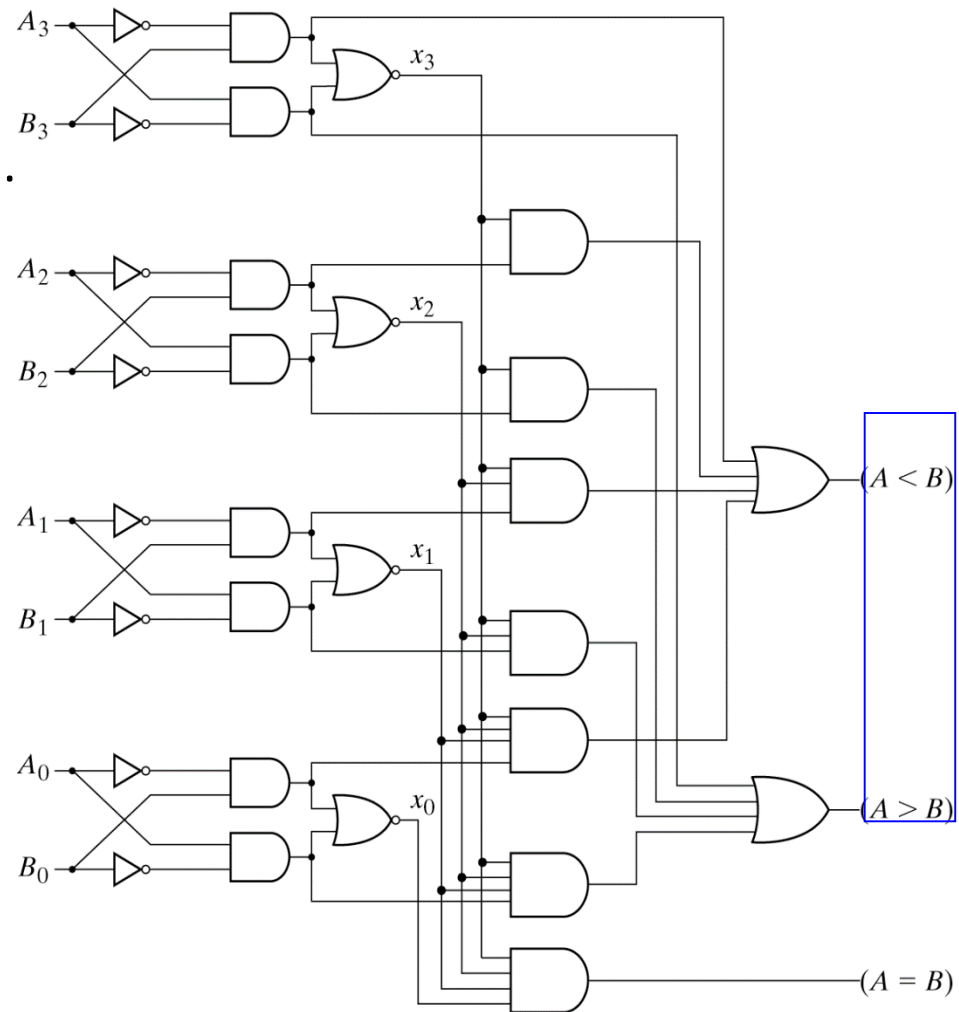
$$A'_3B_3 + x_3A'_2B_2 + x_3x_2A'_1B_1 + x_3x_2x_1A'_0B_0$$




Decoders

- The decoder is called n-to-m-line decoder, where $m \leq 2^n$.
- the decoder is also used in conjunction with other code converters such as a BCD-to-seven_segment decoder.
- 3-to-8 line decoder: For each possible input combination, there are seven outputs that are equal to 0 and only one that is equal to 1.


Inputs			Outputs							
<i>x</i>	<i>y</i>	<i>z</i>	<i>D</i> ₀	<i>D</i> ₁	<i>D</i> ₂	<i>D</i> ₃	<i>D</i> ₄	<i>D</i> ₅	<i>D</i> ₆	<i>D</i> ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Implementation of 3-to-8 Decoder

 

Decoder with enable input

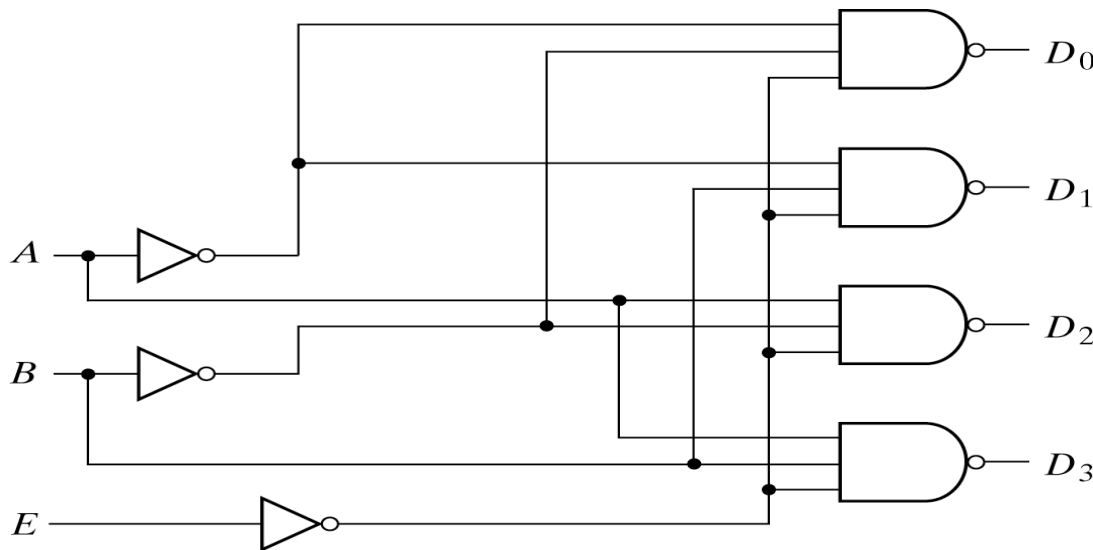- Some decoders are constructed with NAND gates, it becomes more economical to generate the decoder minterms in their complemented form.
- As indicated by the truth table, only one output can be equal to 0 at any given time, all other outputs are equal to 1.




(a) Logic diagram

<i>E</i>	<i>A</i>	<i>B</i>	<i>D</i> ₀	<i>D</i> ₁	<i>D</i> ₂	<i>D</i> ₃
1	<i>X</i>	<i>X</i>	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

 
(b) Truth table

Demultiplexer

- A decoder with an enable input is referred to as a decoder/demultiplexer.
- The truth table of demultiplexer is the same with decoder.



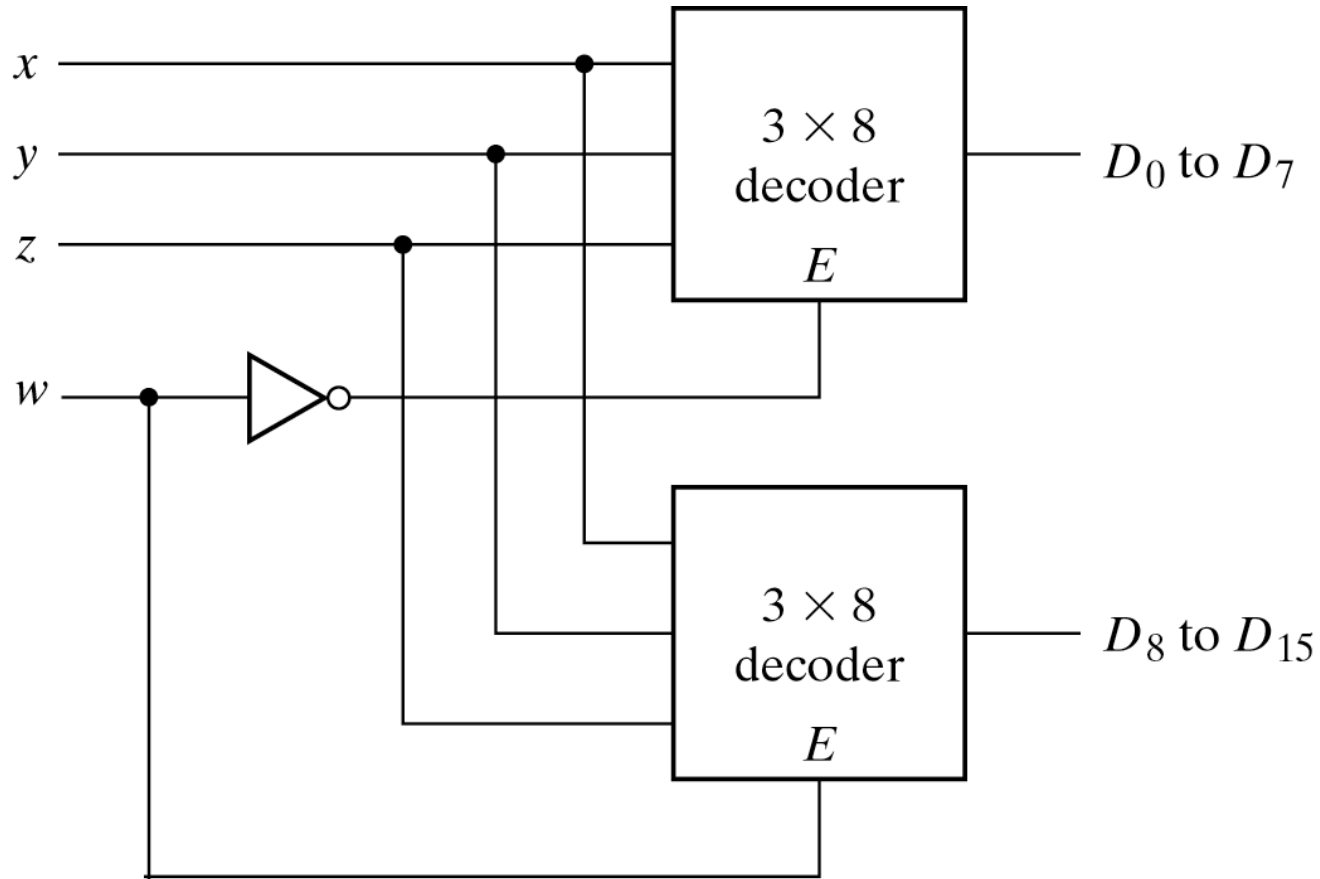3-to-8 decoder with enable implement the 4-to-16 decoder




Full Adder using Decoder

- From the truth table, we obtain the functions for the combinational circuit in sum of minterms:

$$S(x, y, z) = \sum(1, 2, 4, 7)$$

$$C(x, y, z) = \sum(3, 5, 6, 7)$$

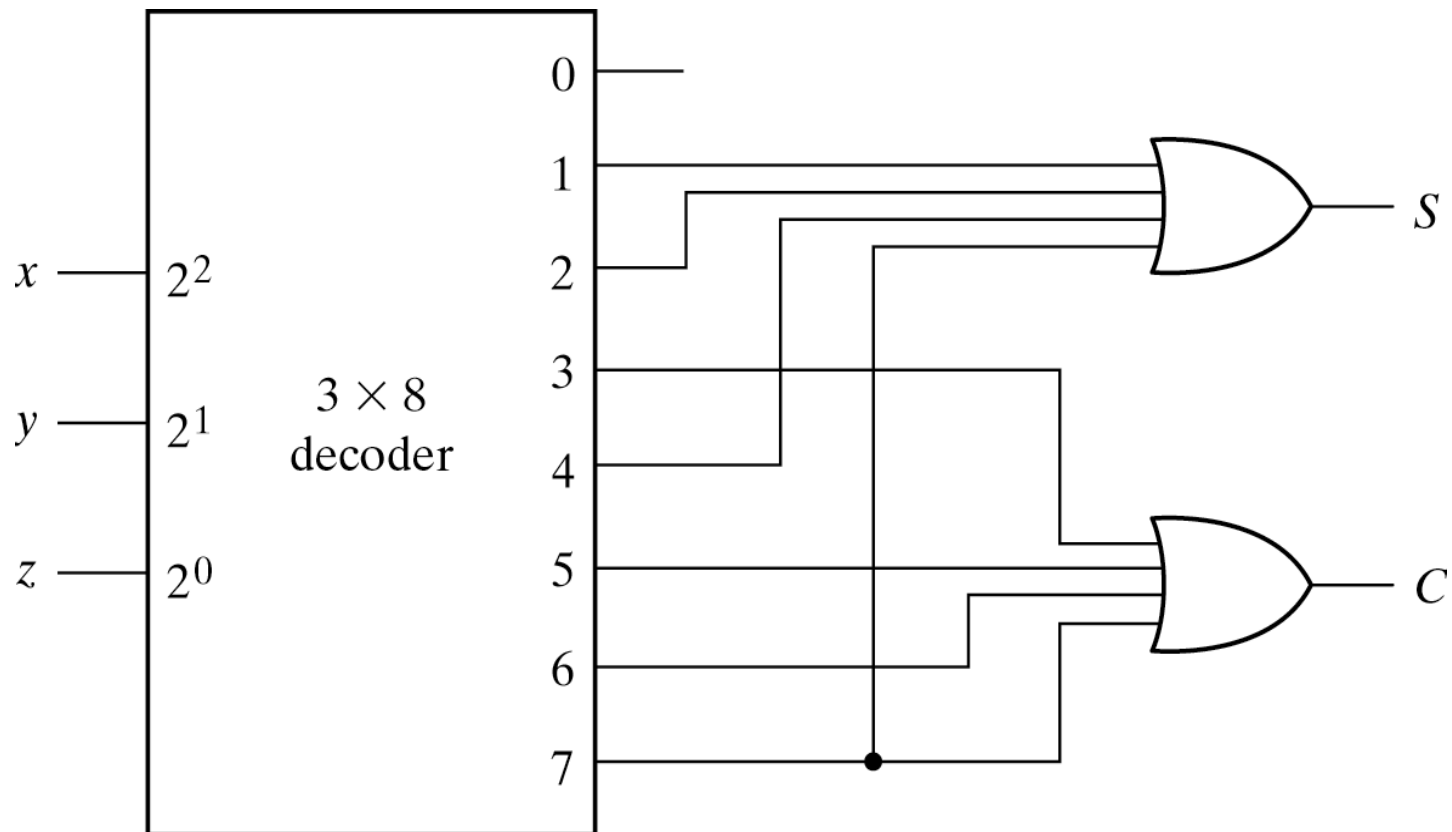

Encoders

- An **encoder** is the **inverse operation of a decoder**.
- We can derive the Boolean functions by table 4-7

$$z = D_1 + D_3 + D_5 + D_7$$

$$y = D_2 + D_3 + D_6 + D_7$$

$$x = D_4 + D_5 + D_6 + D_7$$

Inputs								Outputs		
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

Priority encoder

- If two **inputs** are **active simultaneously**, the **output** produces an **undefined combination**. We can establish an input **priority** to ensure that only one input is encoded.
- **Another ambiguity** in the octal-to-binary encoder is that an **output with all 0's** is generated when **all the inputs are 0**; the output is the same as when D_0 is equal to 1.
- The discrepancy tables can **resolve aforesaid condition by providing one more output** to indicate that at least one input is equal to 1.

Priority encoder

$V=0 \rightarrow$ no valid inputs

$V=1 \rightarrow$ valid inputs

X 's in output columns represent
don't-care conditions

X 's in the input columns are
useful for representing a truth
table in condensed form.

Instead of listing all 16
minterms of four variables.

Table 4-8

Truth Table of a Priority Encoder

Inputs				Outputs		
D_0	D_1	D_2	D_3	x	y	V
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

4-input priority encoder


$$x = D_2 + D_3$$

$$y = D_3 + D_1 D'_2$$

$$V = D_0 + D_1 + D_2 + D_3$$

		D_2				
		00	01	11	10	
D_0	00	X	1	1	1	D_1
	01		1	1	1	
	11		1	1	1	
	10		1	1	1	
		D_3				
		$x = D_2 + D_3$				

		D_2				
		00	01	11	10	
D_0	00	X	1	1	1	D_1
	01	1	1	1	0	
	11	1	1	1	0	
	10		1	1	0	
		D_3				
		$y = D_3 + D_1 D'_2$				

 

Multiplexers

- Select from one of many Inputs and directs it to a single Output
- N selectors $\rightarrow 2^N$ Input lines


$$S = 0, Y = I_0$$

$$S = 1, Y = I_1$$


Truth Table \rightarrow

S	Y
0	I_0
1	I_1

$$Y = S'I_0 + SI_1$$

 


(a) Logic diagram

 

(b) Block diagram

4-to-1 Line Multiplexer

 


(a) Logic diagram

s_1	s_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

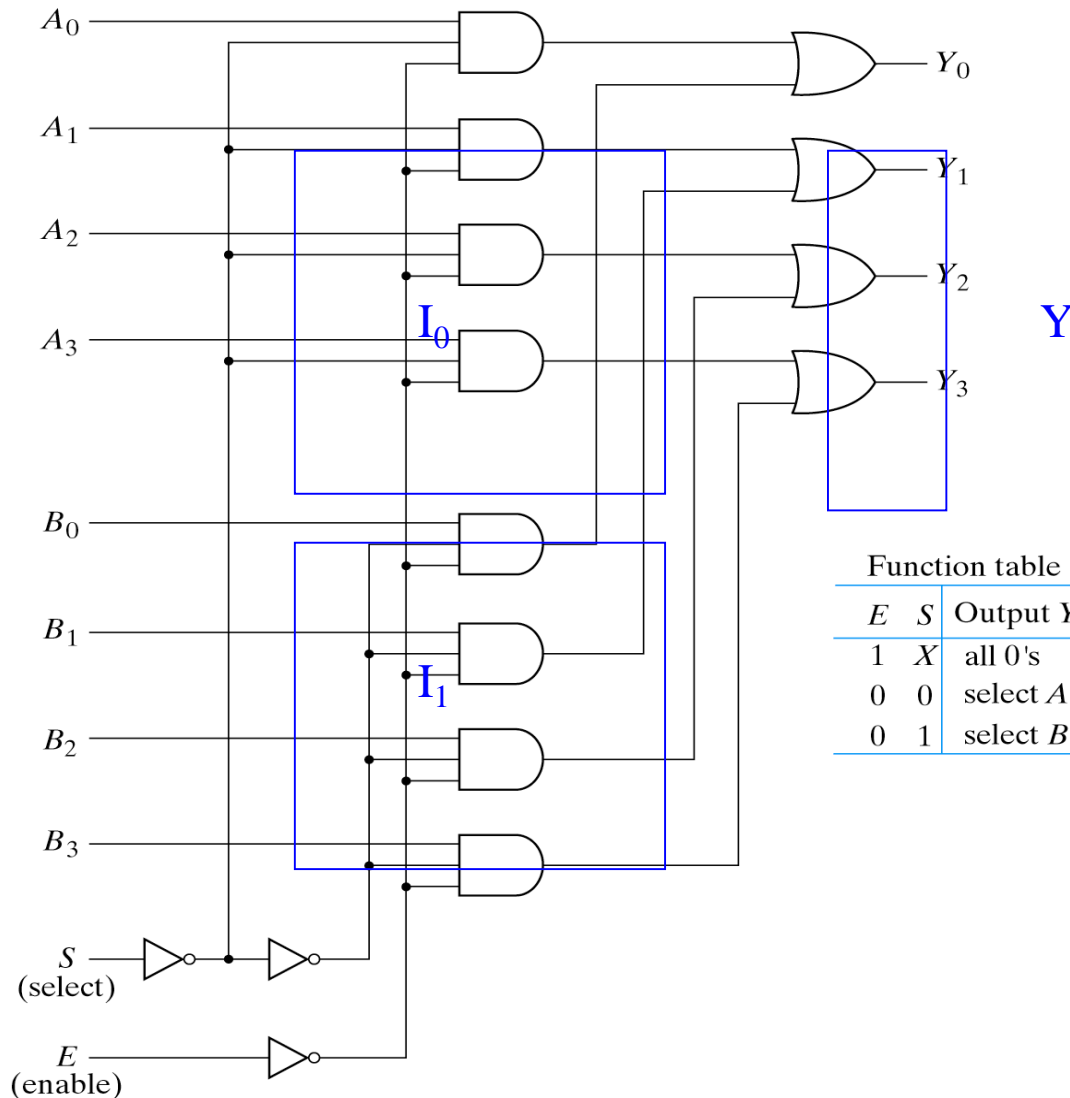(b) Function table

Quadruple 2-to-1 Line Multiplexer

- Multiplexer circuits can be combined with common selection inputs to provide multiple-bit selection logic.




Boolean function implementation

- A more efficient method for implementing a Boolean function of n variables with a multiplexer that has $n-1$ selection inputs.

$$F(x, y, z) = \Sigma(1,2,6,7)$$

x	y	z	F	
0	0	0	0	$F = z$
0	0	1	1	
0	1	0	1	$F = z'$
0	1	1	0	
1	0	0	0	$F = 0$
1	0	1	0	
1	1	0	1	$F = 1$
1	1	1	1	

(a) Truth table

 


(b) Multiplexer implementation

4-input function with a multiplexer



$$F(A, B, C, D) = \Sigma(1, 3, 4, 11, 12, 13, 14, 15)$$

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>F</i>	
0	0	0	0	0	$F = D$
0	0	0	1	1	
0	0	1	0	0	$F = D$
0	0	1	1	1	
0	1	0	0	1	$F = D'$
0	1	0	1	0	
0	1	1	0	0	$F = 0$
0	1	1	1	0	
1	0	0	0	0	$F = 0$
1	0	0	1	0	
1	0	1	0	0	$F = D$
1	0	1	1	1	
1	1	0	0	1	$F = 1$
1	1	0	1	1	
1	1	1	0	1	$F = 1$
1	1	1	1	1	

 


Multiplexer with Three-State Gates

  - A multiplexer can be constructed with three-state gates.



(a) 2-to-1- line mux

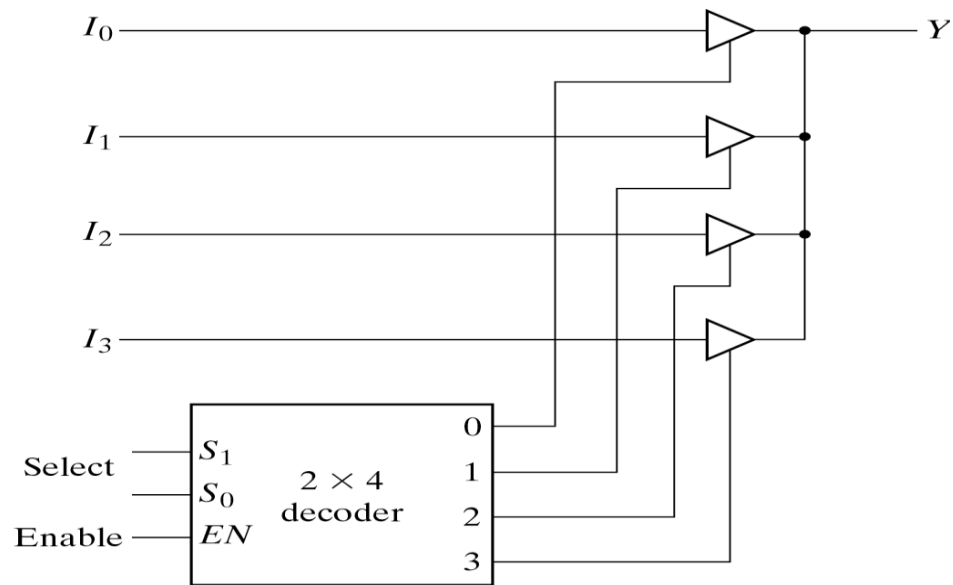

(b) 4 - to - 1 line mux