

## Assignment 3

1. Design a Full Subtractor. Show all the necessary steps.
2. Design a combinational circuit that can convert a BCD number into an Excess-3 number.  
Show all the necessary steps.