

# Digital Logic Design :

## Lecture 15

### The Edge-Triggered J-K Flip-Flop :

The functioning of the J-K flip-flop is identical to that of the S-R flip-flop in the SET, RESET and No change conditions of operation. The difference is that the J-K flip-flop has no invalid states as does the S-R flip-flop.


 
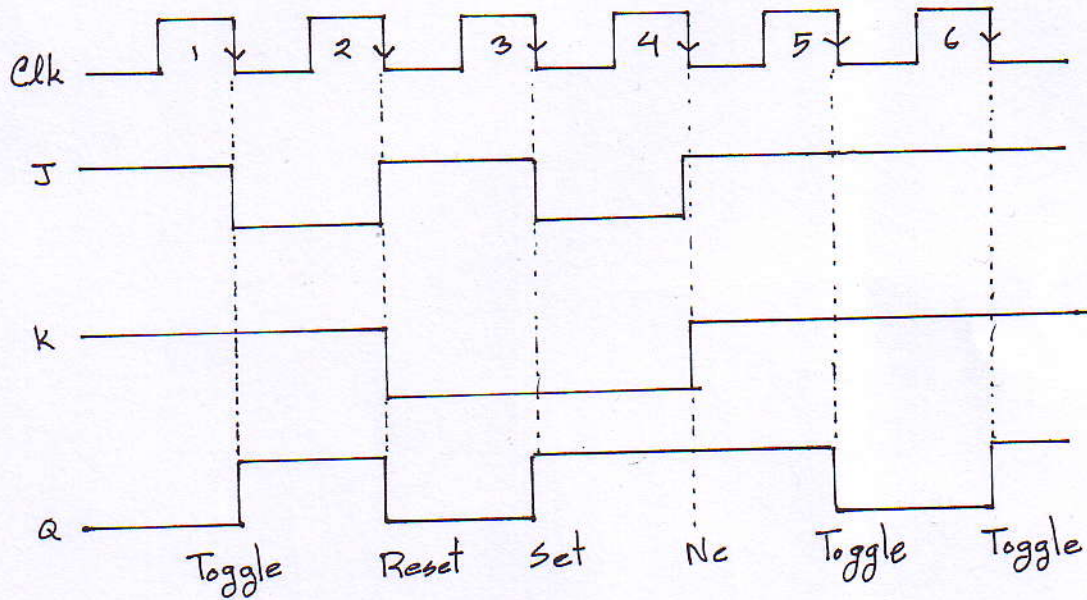


Fig : Logic diagram for a positive edge triggered J-K flip-flop


Inputs			Outputs		Comments
J	K	clk	Q	$\bar{Q}$	
0	0	↑	$Q_0$	$\bar{Q}_0$	No change
0	1	↑	0	1	RESET
1	0	↑	1	0	SET
1	1	↑	$\bar{Q}_0$	$Q_0$	Toggle

 Determine  $Q$  output if the J-K flip-flop is initially RESET



T flip-flop :

 A J-K flip-flop connected for toggle operation is sometimes called a T flip-flop.





Inputs		Outputs		Comments
T	Clk	Q	$\bar{Q}$	
0	↑	$Q_0$	$\bar{Q}_0$	No Change
1	↑	$\bar{Q}_0$	$Q_0$	Toggle mode

The Edge-Triggered D Flip-Flop :

 


Fig : A positive edge triggered D flip-flop formed with an S-R flip-flop and an inverter

Truth table for positive edge triggered D flip-flop


Inputs		Outputs		Comments
D	Clk	Q	$\bar{Q}_0$	
1	↑	1	0	SET
0	↑	0	1	RESET

The D flip-flop is used to store a single data bit, positive edge triggered flip-flop stores data at the



leading edge of the clock.

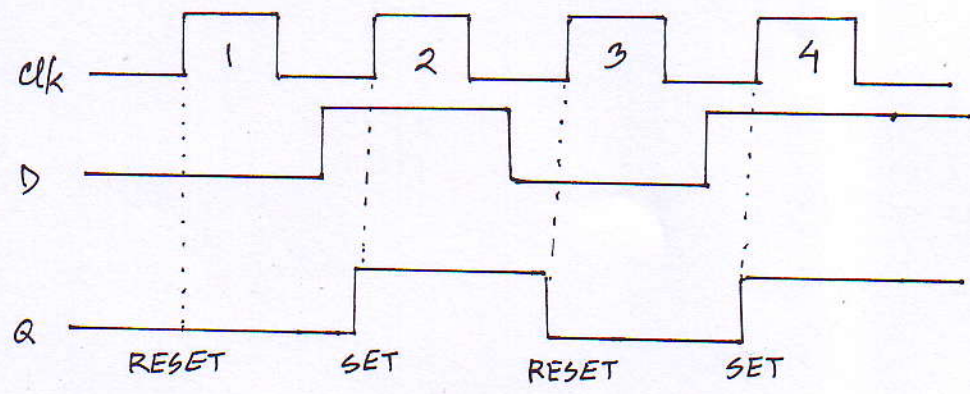Determine Q if the D flip-flop is initially RESET



flip-flop with Asynchronous Inputs


 


Fig : Logic symbol for a J-K flip-flop with active Low preset and clear inputs.

\* Determine Q for the following inputs

 



# MASTER SLAVE J-K FLIP-FLOPS


 



Fig : Logic diagram for a master slave J-K flip-flop

Truth table

Inputs			Outputs		Comments
J	K	clk	Q	$\bar{Q}$	
0	0		$Q_0$	$\bar{Q}_0$	No Change
0	1		0	1	RESET
1	0		1	0	SET
1	1		$\bar{Q}_0$	$Q_0$	Toggle

 

 
a) Data transferred to the output at the negative edge of the clock pulse



b) Data transferred to the output at the positive edge of the clock pulse

Fig : Pulse triggered / Master Slave flip-flop



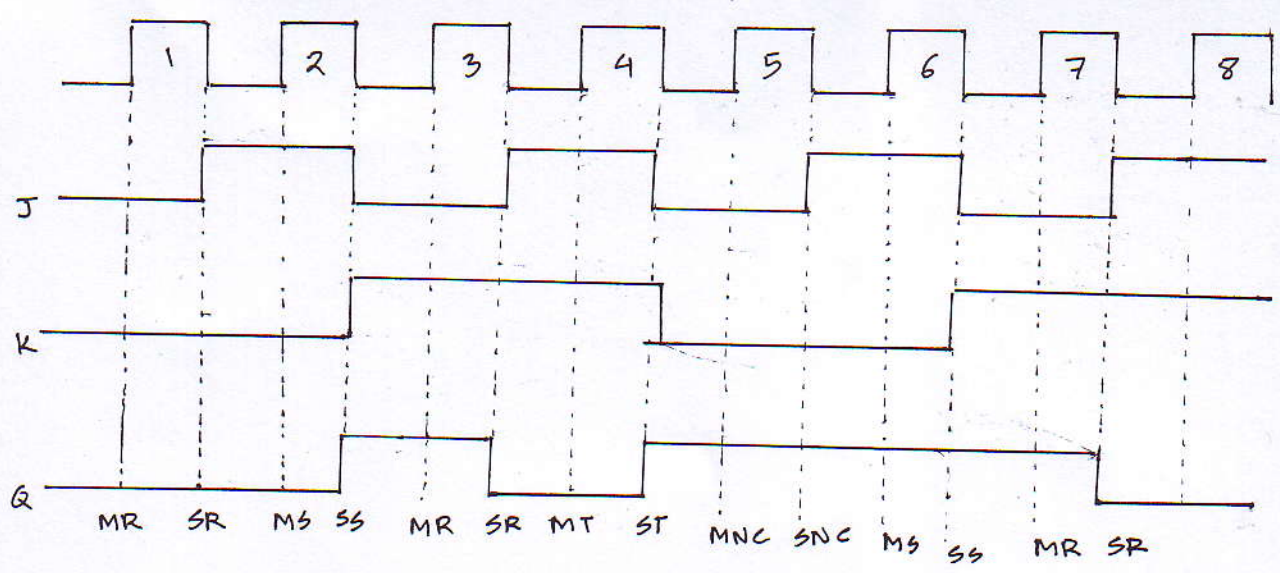

Determine Q if the flip-flop is initially RESET

D type Edge triggered flip-flop without pulse transition detector

 


Fig : D type positive edge-triggered flip-flop.

Truth table of  $\bar{S}\bar{R}$  latch

$\bar{S}$	$\bar{R}$	Q
0	1	1
1	0	0
0	0	Invalid
1	1	NC

CP	D	$\bar{S}$	$\bar{R}$	Q1	Q4
0	0	1	1	0	1
1	0 → 1	1	0	0	1
0	1	1	1	1	0
1	1 → 0	0	1	1	0 → 1