



North South University

Department of Electrical and Computer Engineering LAB REPORT-08

Course name: Digital Logic Design Lab

Course Code: 231.L

Experiment Number: 08

Experiment name: Synchronous Sequential Circuits

Experiment Date: 27th April, 2021

Report Submission Date: 4th May, 2021

Section: 06

Group no: 04

Student Name	ID
Khalid Bin Shafiq	1911342642
Rafidul Islam	1912152642
Rashiqur Rahman Rifat	1911445652
Towsif Muhtadi Khan	1911576642
Remarks:	Score:

OBJECTIVES:

- Gain a practical understanding of State Diagrams and State Tables.
- Understand the concept of designing Sequential Circuits using Flip-Flops.
- Design and implement a Synchronous Sequential Circuit given a State Diagram.

THEORY:

Synchronous Sequential Circuits:

Sequential Circuit is made of combinational circuits and memory storage where circuits conduct the operation of present output based on present inputs and past outputs stored in memory storage. In a sequential circuit, the values of the outputs depend on the past behavior of the circuit, as well as the present values of its inputs. A sequential circuit has states, which in conjunction with the present values of inputs determine its behavior. Sequential circuits can be Synchronous where flip-flops are used to implement the states, and a clock signal is used to control the operation.

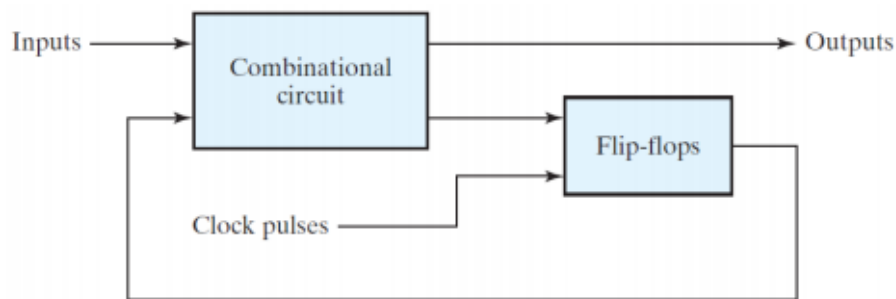


Figure: The general form of a synchronous sequential circuit.

State Table:

The state table representation of a sequential circuit consists of three sections labeled present state, next state and output. The present state designates the state of flip-flops before the occurrence of a clock pulse. The next state shows the states of flip-flops after the clock pulse, and the output section lists the value of the output variables during the present state.

State Diagram:

In addition to graphical symbols, tables or equations, flip-flops can also be represented graphically by a state diagram. In this diagram, a state is represented by a circle, and the transition between states is indicated by directed lines (or arcs) connecting the circles.

EQUIPMENT LIST:

- Trainer board
- 1 x IC 74107 JK Flip-Flop
- 1 x IC 7408 2-input AND gates
- 1 x IC 7404 Hex inverters (NOT gates)
- IC 7474 (Dual D Flip-Flops)
- IC 74107 (Dual JK Flip-Flops)

CIRCUIT DIAGRAM:

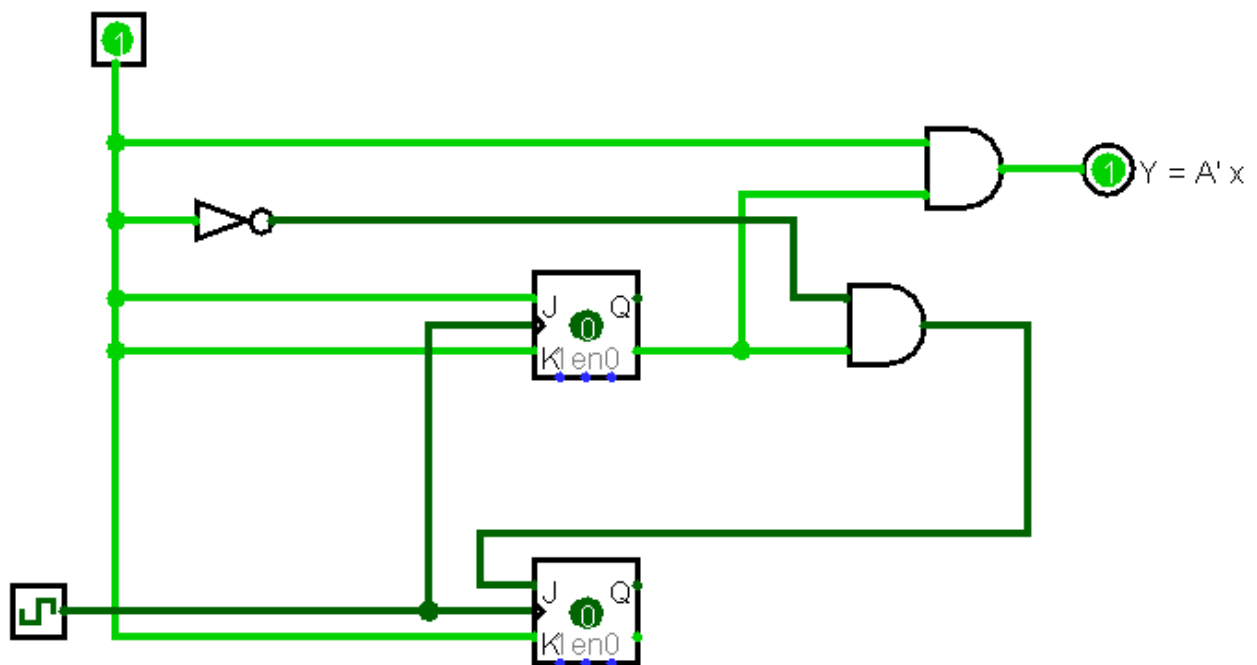


Figure F..1.1: Sequential Circuit simulation using JK Flip flop

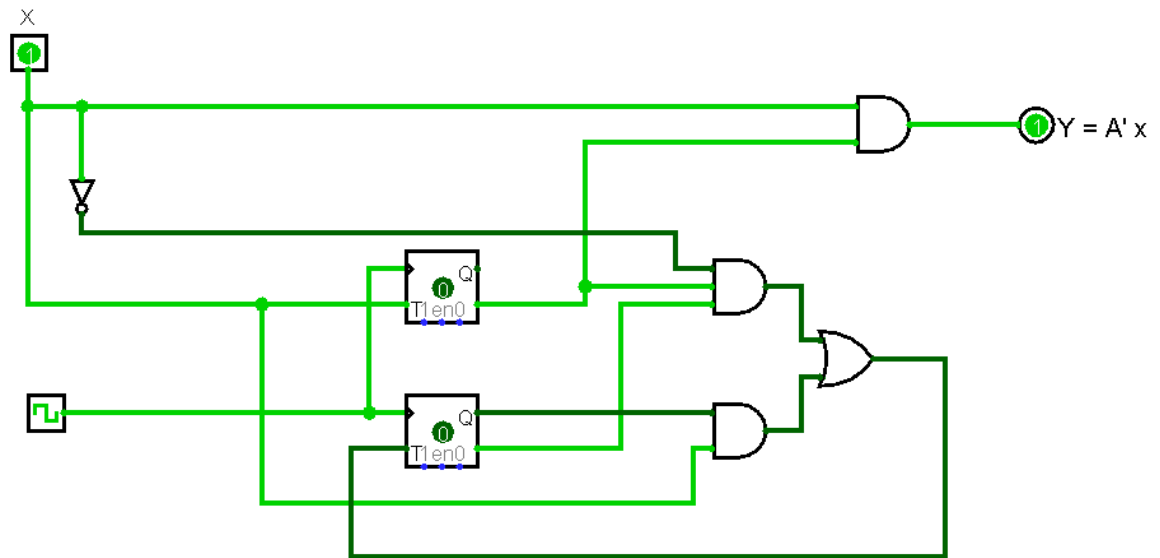


Figure F.2.1: Sequential Circuit simulation using T Flip flop

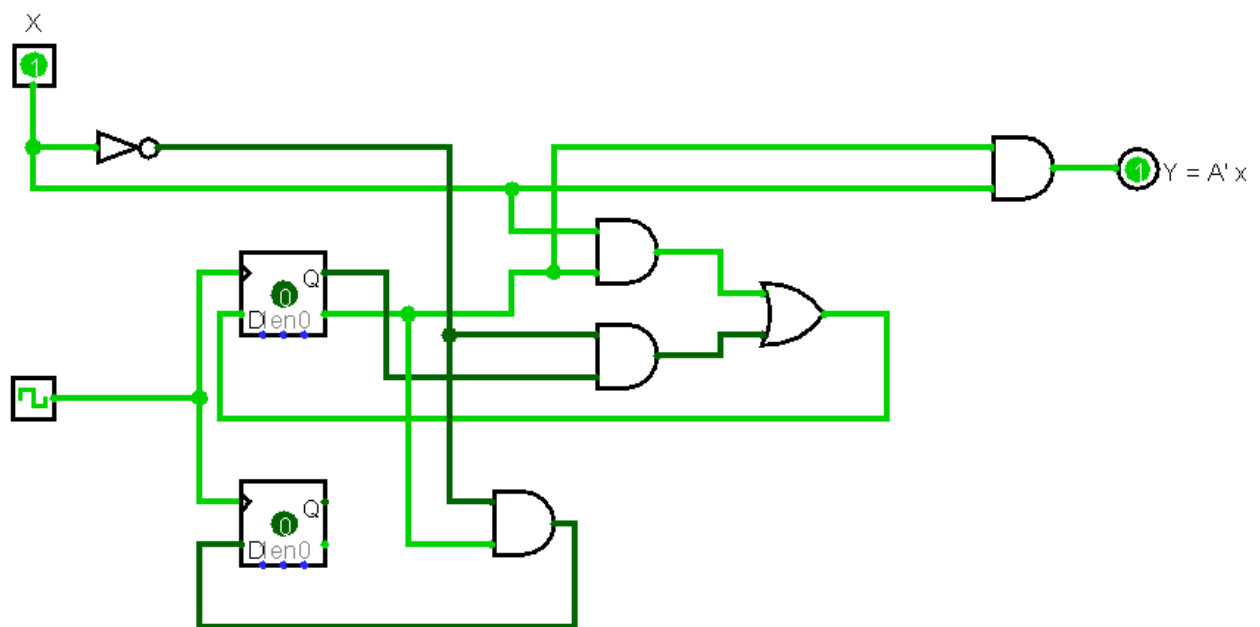


Figure F.3.1: Sequential Circuit simulation using D Flip flop

KMAP:

A \ B _x	B _x				
	00	01	11	10	
0	0	1	1	0	$J_A = x$
1	x	x	x	x	

A \ B _x	B _x				
	00	01	11	10	
0	x	x	x	x	$= K_A = x$
1	0	1	x	x	

A \ B _x	B _x				
	00	01	11	10	
0	1	0	x	x	$J_B = \bar{A}\bar{x}$
1	0	0	x	x	

A \ B _x	B _x				
	00	01	11	10	
0	x	x	1	0	$K_B = x$
1	x	x	x	x	

A \ B _x	B _x				
	00	01	11	10	
0	0	1	1	0	$Y = \bar{A}x$
1	0	0	x	x	

Figure: K Map for JK Flip-Flops

A \ Bx	00	01	11	10
0	0	1	1	0
1	0	1	x	x

$T_A = x$




A \ Bx	00	01	11	10
0	1	0	1	0
1	0	0	x	x

$T_B = \bar{A}\bar{B}\bar{x} + Bx$

A \ Bx	00	01	11	10
0	0	1	1	0
1	0	0	x	x

$Y = \bar{A}x$

Figure: K Map for T Flip-Flops

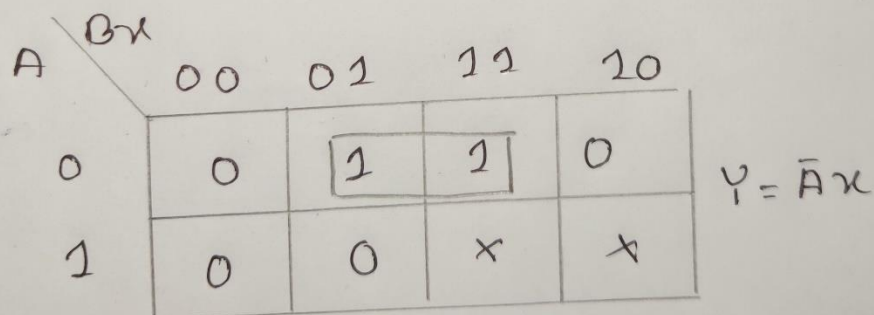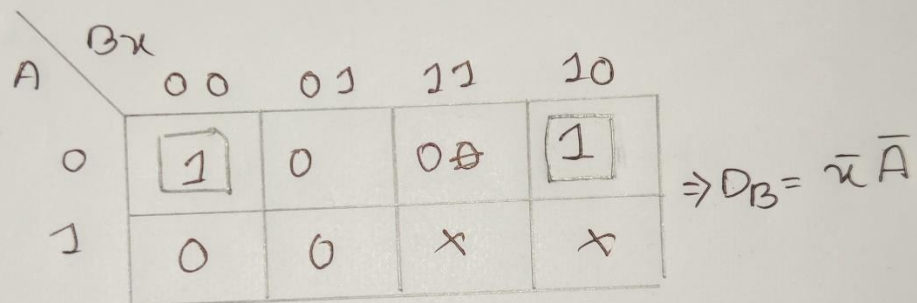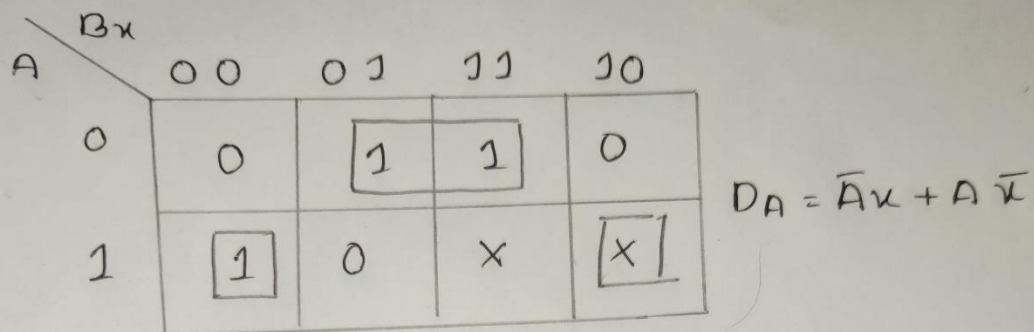

K Map for D Flip flop

Figure: K Map for D Flip-Flops

DATA & TABLE:

Present state		Input	Next state		Output	Flip-flop input functions			
A	B	X	A	B	Y	J _A	K _A	J _B	K _B
0	0	0	0	1	0	0	X	1	X
0	0	1	1	0	1	1	X	0	X
0	1	0	0	1	0	0	X	X	0
0	1	1	1	0	1	1	X	X	1
1	0	0	1	0	0	X	0	0	X
1	0	1	0	0	0	X	1	0	X
1	1	0	X	X	X	X	X	X	X
1	1	1	X	X	X	X	X	X	X

Table F.1.1: State Table for circuit using JK Flip-Flops

Present state		Input	Next state		Output	Flip-flop input functions	
A	B	X	A	B	Y	T _A	T _B
0	0	0	0	1	0	0	1
0	0	1	1	0	1	1	0
0	1	0	0	1	0	0	0
0	1	1	1	0	1	1	1
1	0	0	1	0	0	0	0
1	0	1	0	0	0	1	0
1	1	0	X	X	X	X	X
1	1	1	X	X	X	X	X

Table F.2.1: Constructing a Sequential Circuit using T Flip-Flops

Present state		Input	Next state		Output	Flip-flop input functions	
A	B	X	A	B	Y	D _A	D _B
0	0	0	0	1	0	0	1
0	0	1	1	0	1	1	0
0	1	0	0	1	0	0	1
0	1	1	1	0	1	1	0
1	0	0	1	0	0	1	0
1	0	1	0	0	0	0	0
1	1	0	X	X	X	X	X
1	1	1	X	X	X	X	X

Table F.3.1: State Table for circuit using D Flip-Flops

QUESTIONS:

Ques-01: Is the output equation (Y) of this circuit the same as the equation in the JK Flip-Flop circuit? Explain why.

ANS: From given state diagram, the obtained output values of y depend on the flip-flop output and external input for both JK flip-flop and T flip-flop. As the values of external output y is same for JK flip-flop and T flip-flop, the output equation obtained from k-map will also be same.

RESULT ANALYSIS AND DISCUSSION:

The overall lab experiment was about the implementation of synchronous sequential circuit using different types of flip-flops. At the beginning of the experiment, we implemented the synchronous sequential circuit using JK flip-flop.

At first, from given state diagram, we had to complete the state table with next state values and external output values. Then using Karnaugh map built from state table, we got required state equations. Using these state equations, we constructed the sequential circuit.

Then we constructed synchronous sequential circuit using D flip-flop and T flip-flop as same as did for JK flip-flop. Additionally, we did the implementation with basic logic gate ICs and T flip-flop. During experiment, Logisim worked properly. Above all, from the experiment, we learned how to implement the synchronous sequential circuit using JK, D, T flip-flops.

CONTRIBUTION

NAME	CONTRIBUTION IN
Khalid Bin Shafiq	CIRCUIT DIAGRAM ,QUESTION ANSWER
Rafidul Islam	RESULT ANALYSIS AND DISCUSSION
Rashiqur Rahman Rifat	THEORY
Towsif Muhtadi Khan	DATA & TABLE,KMAP COORDINATOR

Class Assignment 08

Complete the class work and attach the screenshots/images at the end.

F.1 Experimental Data: Constructing a Sequential Circuit using T Flip-Flops

Present state		Input	Next state		Output	Flip-flop input functions	
A	B	X	A	B	Y	T _A	T _B
0	0	0	0	1	0	0	1
0	0	1	1	0	1	1	0
0	1	0	0	1	0	0	0
0	1	1	1	0	1	1	1
1	0	0	1	0	0	0	0
1	0	1	0	0	0	1	0
1	1	0	X	X	X	X	X
1	1	1	X	X	X	X	X

Table F.2.1: State Table for circuit using T Flip-Flops

0	1	1	0
1	0	0	X

T_A =

1	0	1	0
0	0	X	X

T_B =

0	1	1	0
0	0	X	X

Y =

A \ Bx				
	00	01	11	10
0	0	1	1	0
1	0	1	x	x

$T_A = x$


A \ Bx				
	00	01	11	10
0	1	0	1	0
1	0	0	x	x

$T_B = \bar{A}\bar{B}\bar{x} + Bx$

A \ Bx				
	00	01	11	10
0	0	1	1	0
1	0	0	x	x

$Y = \bar{A}x$

K Map

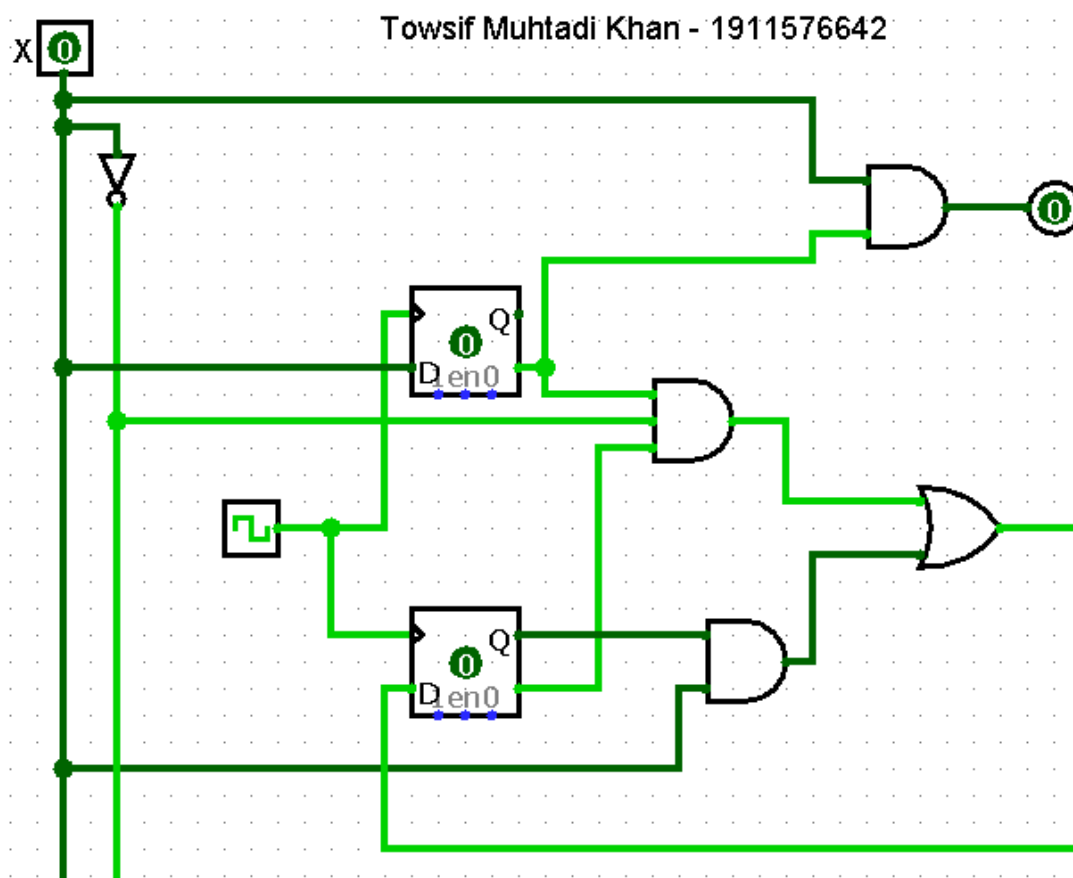

Sequential Circuit Using T Flip; Flops

Figure F.2.1: Circuit Diagram

F.2 Experimental Data: Constructing a Sequential Circuit using D Flip-Flops

Present state		Input	Next state		Output	Flip-flop input functions	
A	B	X	A	B	Y	D _A	D _B
0	0	0	0	1	0	0	1
0	0	1	1	0	1	1	0
0	1	0					
0	1	1					
1	0	0					
1	0	1					
1	1	0					
1	1	1					

Table F.3.1: State Table for circuit using D Flip-Flops

D_A =

D_B =

Y =

 


Figure F.3.1: Circuit Diagram

F.1 Experimental Data: Constructing a Sequential Circuit using D Flip-Flops

Present state		Input	Next state		Output	Flip-flop input functions	
A	B	X	A	B	Y	D _A	D _B
0	0	0	1	1	0	1	1
0	0	1	0	1	0	0	1
0	1	0	1	1	0	1	1
0	1	1	0	0	0	0	0
1	0	0	1	0	0	1	0
1	0	1	1	1	1	1	1
1	1	0	1	0	0	1	0
1	1	1	1	0	1	1	0

Table F.3.1: State Table for circuit using D Flip-Flops

1	0	0	1
1	1	1	1

D_A =

1	1	0	1
0	1	0	0

D_B =

0	0	0	0
0	1	1	0

Y =

K map:

Handwritten: A/Bx

1	0	0	1
1	1	1	1

$$D_A = \bar{B} + A$$

Handwritten: A/Bx

1	1	0	1
0	1	0	0

$$D_B = \bar{B}x + \bar{A}x$$

Handwritten: A/Bx

0	0	0	0
0	1	1	0

$$Y = Ax$$

