

Lab 1: Digital Logic Gates and Boolean Functions

F. Data Sheet

F.1 Introduction to Basic Logic Gates

 


Figure F.1.1: Pin configurations of gates in ICs

Input	AND	OR	NAND	XOR	NOR
0 0	0	0	1	0	1
0 1	0	1	1	1	0
1 0	0	1	1	1	0
1 1	1	1	0	0	0

Input	NOT
0	1
1	0

Table F.1.1: Truth Table of Logic Gates

F.2 Constructing 3-input AND & OR gates from 2-input AND & OR gates

A B C	$F = ABC$	$F = A+B+C$
0 0 0	0	0
0 0 1	0	1
0 1 0	0	1
0 1 1	0	1
1 0 0	0	1
1 0 1	0	1
1 1 0	0	1
1 1 1	1	1

Table F.2.1: Truth Tables for 3-input AND and OR

$F = ABC = A(BC) = (AB)C$
$F = A+B+C = A+(B+C) = (A+B)+C$

Table F.2.2: Expressing 3-input gates as 2-input gates using associative law.

 


Figure F.2.1: Extension of inputs of AND and OR gates

F.3 Implementation of Boolean Functions

A B C	$I_1 = A'C$	$I_2 = AB'$	$I_3 = BC$	$F = I_1 + I_2 + I_3$
0 0 0	0	0	0	0
0 0 1	1	0	0	1
0 1 0	0	0	0	0
0 1 1	1	0	1	1
1 0 0	0	1	0	1
1 0 1	0	1	0	1
1 1 0	0	0	0	0
1 1 1	0	0	1	1

Figure F.3.1: Truth Table for the given Boolean Function

 


Figure F.3.1: Logic Diagram for the given Boolean Function

Attachment:

1. Attach the screenshots /image of the simulations below
2. Attach the required logic Diagrams with proper figure name and labeling below.

Logisim: main of lab 1

File Edit Project Simulate Window Help

lab 1

- main
- Wiring
- Gates
 - NOT Gate
 - Buffer
 - AND Gate
 - OR Gate
 - NAND Gate
 - NOR Gate
 - XOR Gate
 - XNOR Gate
 - Odd Parity
 - Even Parity
 - Controlled Buffer
 - Controlled Inverter
- Plexers
- Arithmetic

Circuit: main

Circuit Name	main
Shared Label	
Shared Label Facing	East
Shared Label Font	SansSerif Plain 12

Name: Rafidul Islam, ID: 1912152642

100%

Type here to search

12:56 PM 3/2/2021

Activate Windows
Go to Settings to activate Windows.

F.1.1

Logisim: main of lab 1

File Edit Project Simulate Window Help

lab 1

- main
- Wiring
- Gates
 - NOT Gate
 - Buffer
 - AND Gate
 - OR Gate
 - NAND Gate
 - NOR Gate
 - XOR Gate
 - XNOR Gate
 - Odd Parity
 - Even Parity
 - Controlled Buffer
 - Controlled Inverter
- Plexers
- Arithmetic

Pin

Facing	East
Output?	No
Data Bits	1
Three-state?	No
Pull Behavior	Unchanged
Label	
Label Location	West
Label Font	SansSerif Plain 12

Name: Rafidul Islam, ID: 1912152642

100%

Type here to search

1:10 PM 3/2/2021

Activate Windows
Go to Settings to activate Windows.

F.2.1



4