

# Digital Logic Design :

## Lecture 19

### Counter Applications :

#### The Digital Clock


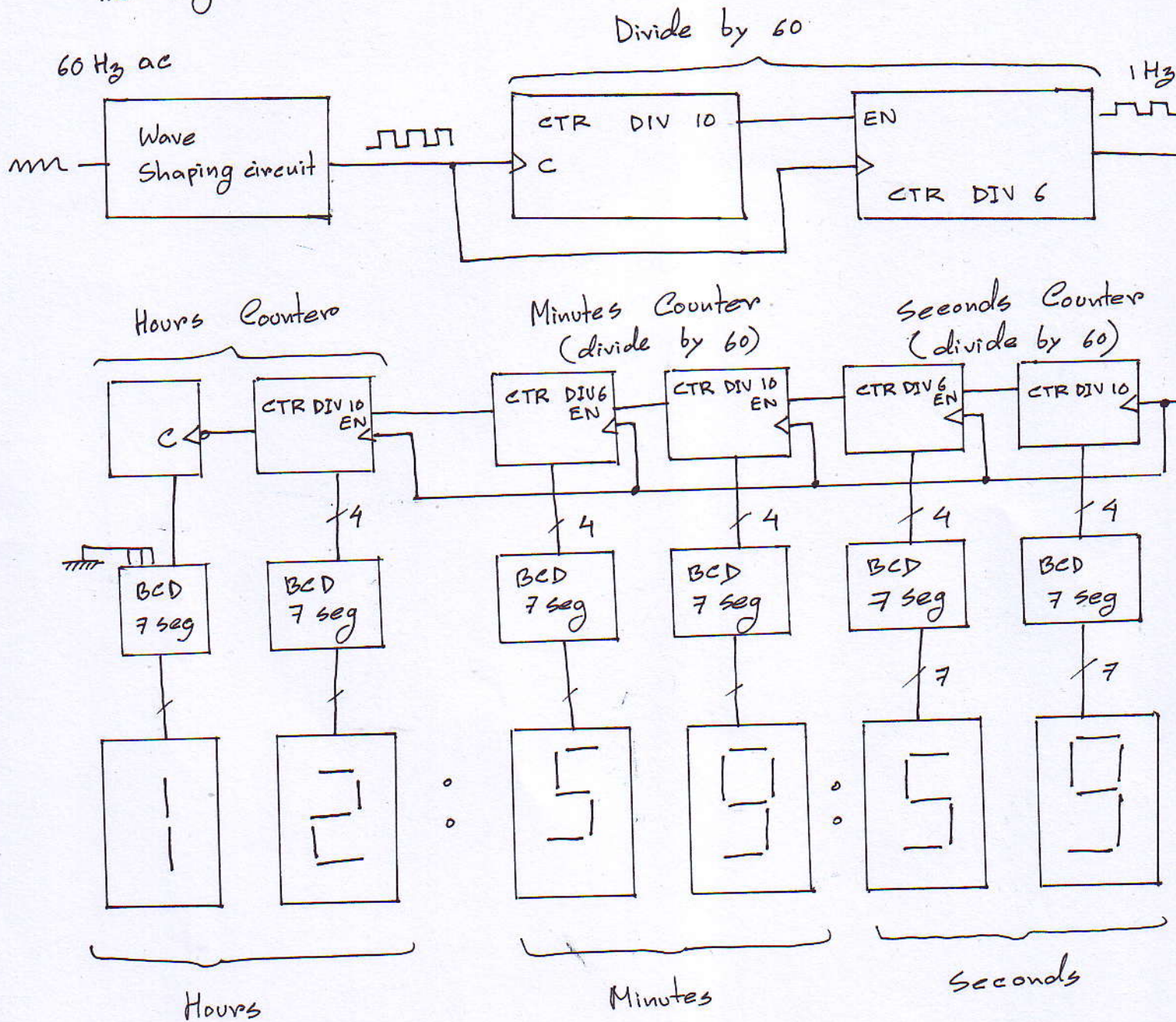



Fig : Simplified logic diagram for a 12-hour digital clock

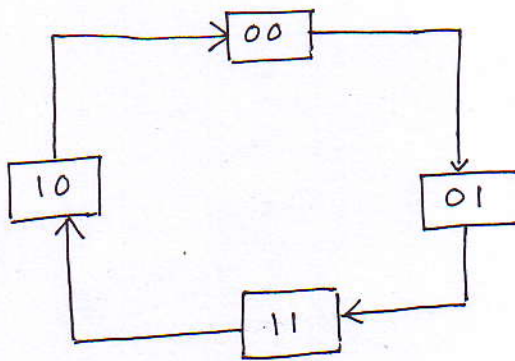


Design a counter that will count in 2-bit Gray code sequence :




Present State		Next State	
$Q_1$	$Q_0$	$Q_1$	$Q_0$
0	0	0	1
0	1	1	1
1	1	1	0
1	0	0	0

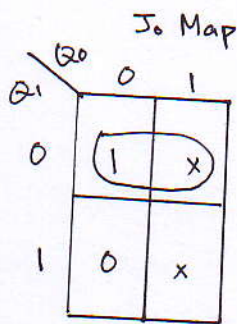


$$J_0 = \overline{Q_1}$$

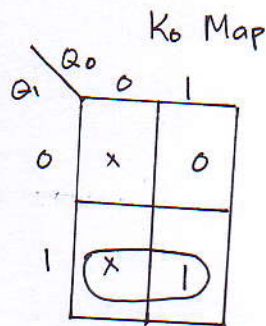


$$K_0 = Q_1$$

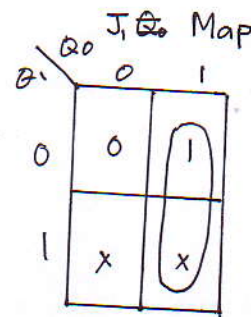

$$J_1 = Q_0$$

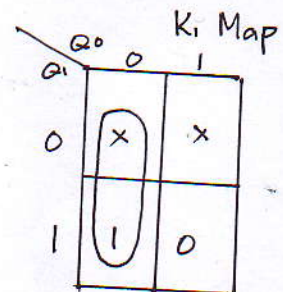

$$K_1 = \overline{Q_0}$$

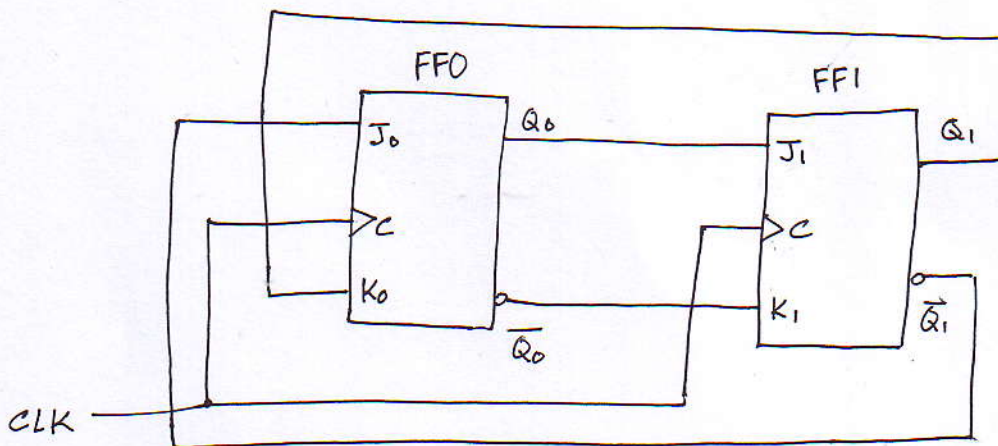


Output Transitions

$Q_N$	$Q_{N+1}$
0	→ 0
0	→ 1
1	→ 0
1	→ 1

Flip-flop inputs

J	K
0	x
1	x
x	1
x	0

## SHIFT REGISTERS

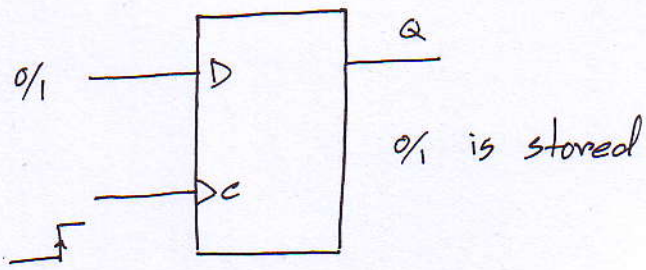

Serial In / Serial Out shift register :


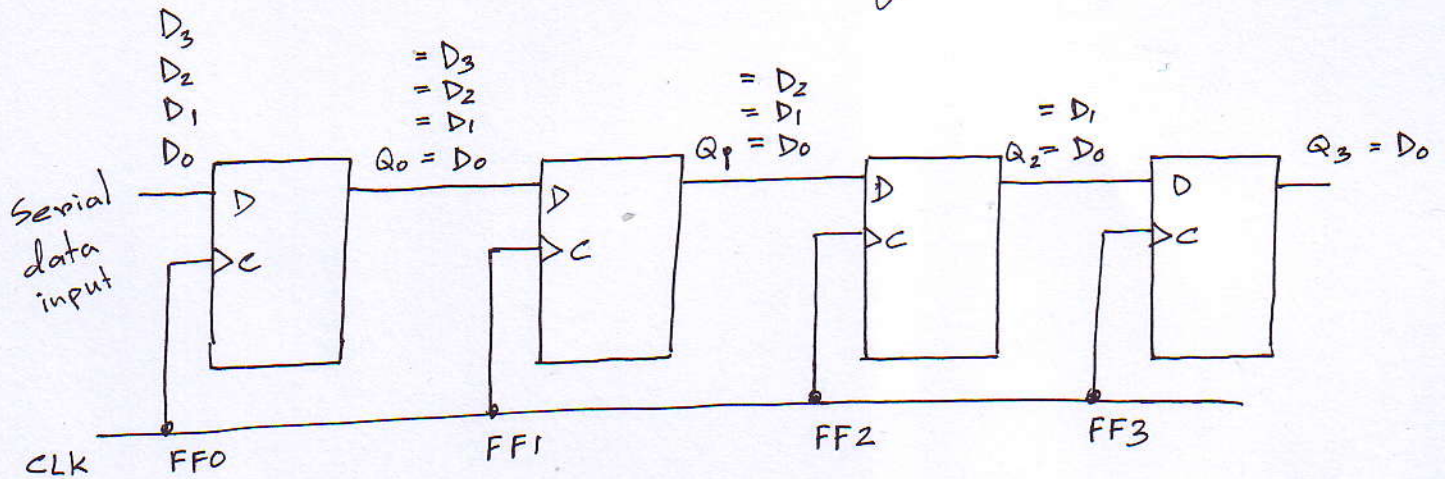


Fig : 4-bit serial in / serial out Shift register

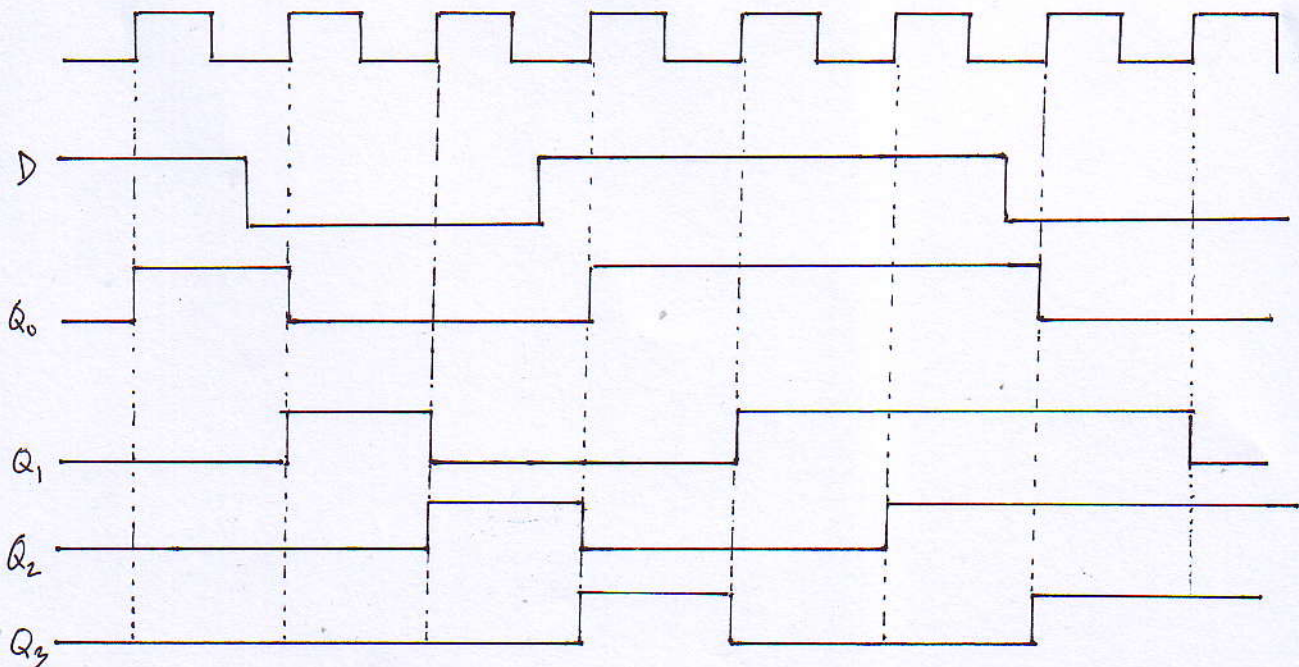Determine  $Q_0, Q_1, Q_2$  and  $Q_3$  for the following clock and D input :





# Serial In/Parallel Out Shift Register :

19-4

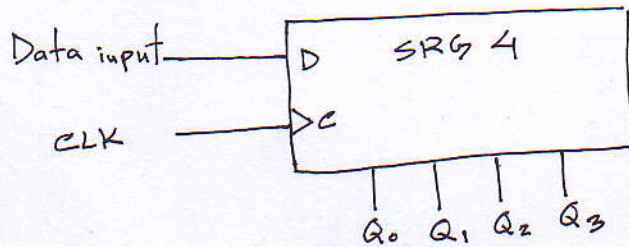
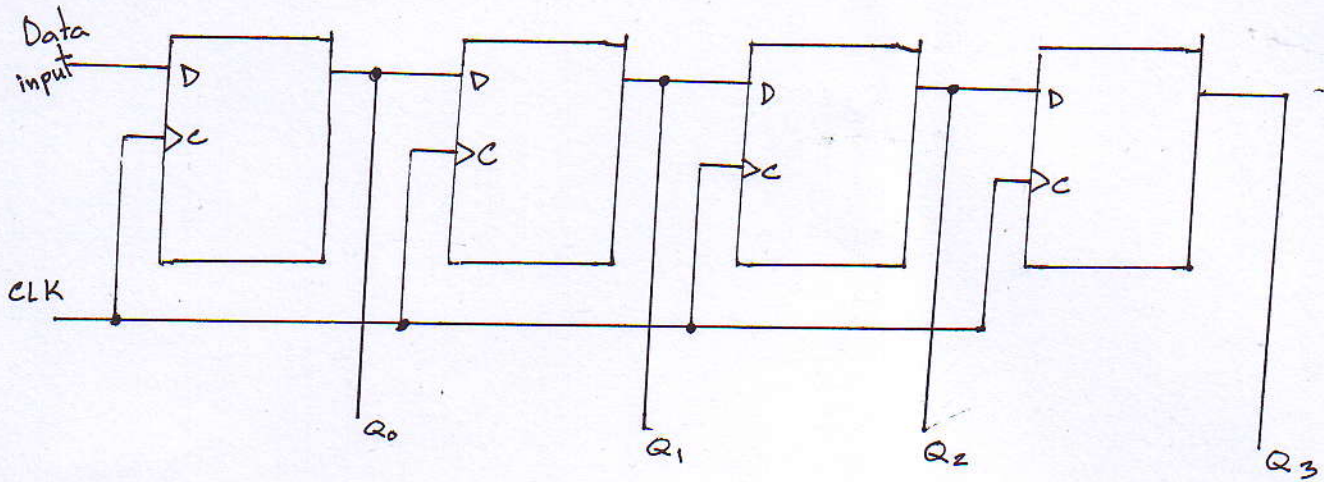


Fig: Logic symbol

Fig : A serial in/parallel out shift register

## Parallel In/Serial Out Shift Register :

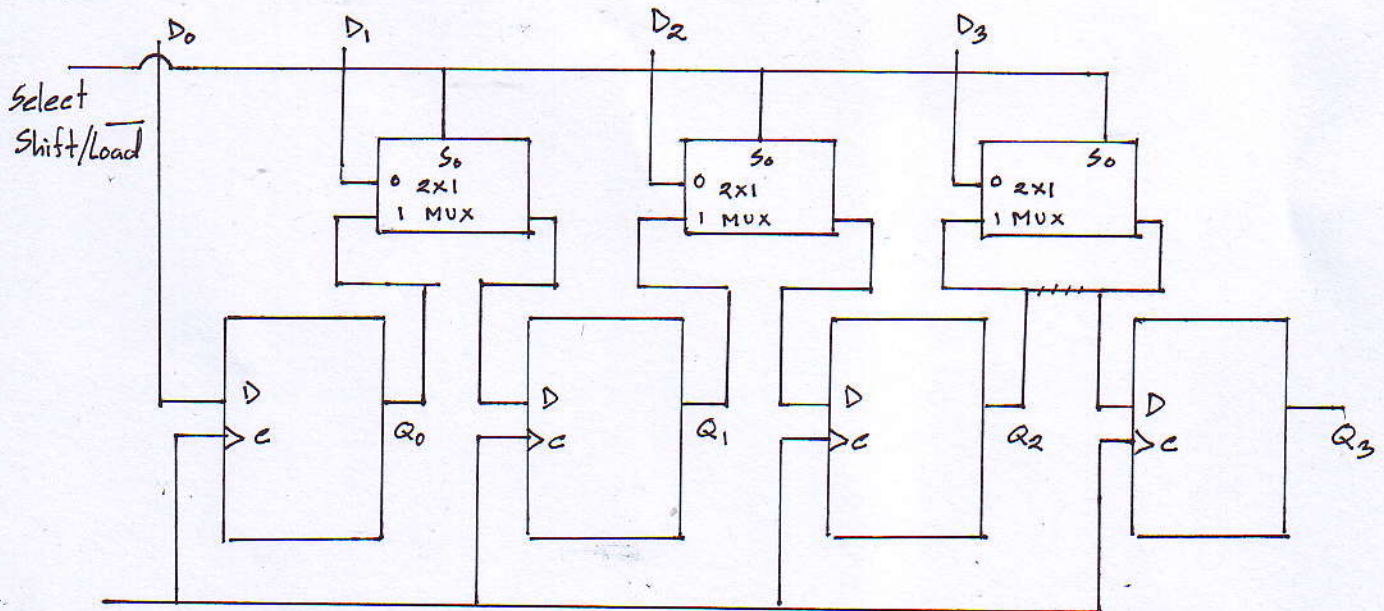


Fig : Four Bit Parallel In Serial Out Shift Register



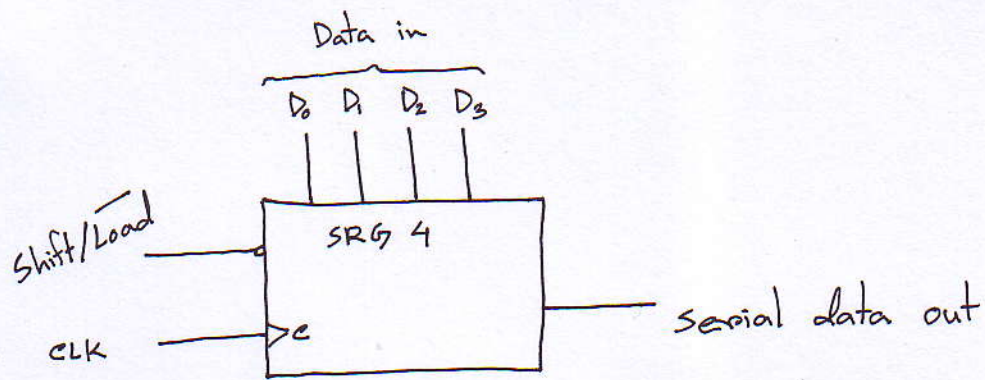


Fig : Logic symbol

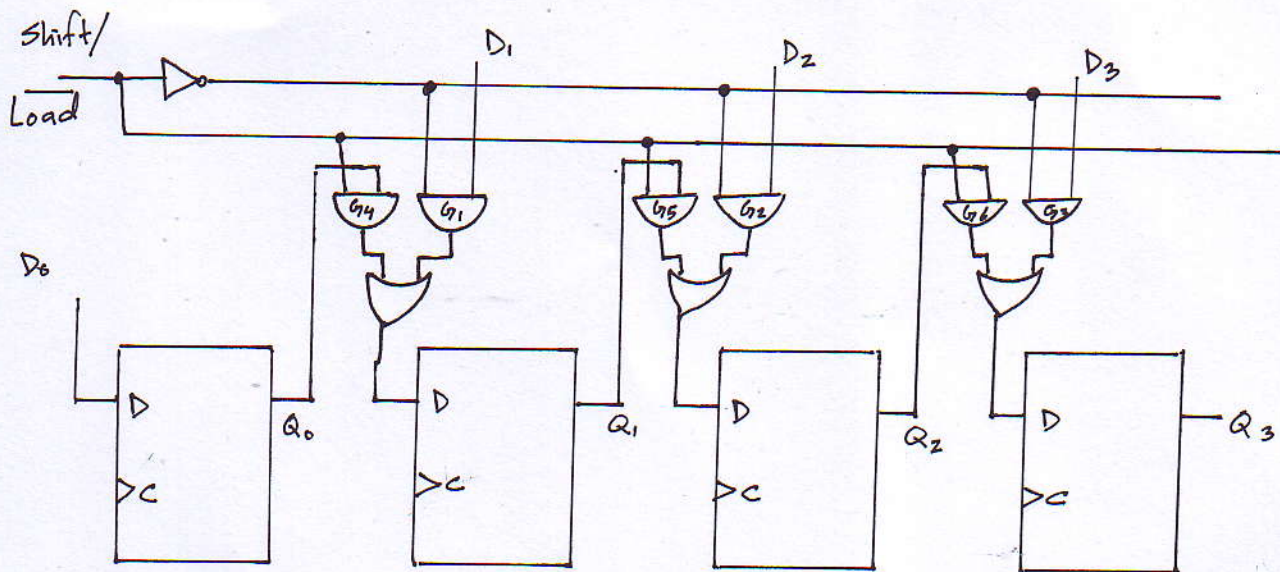
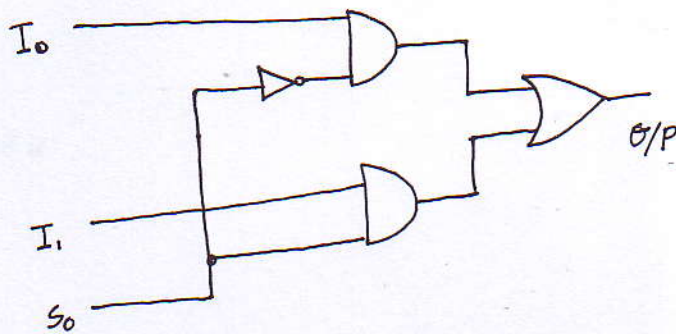


Fig : Four bit Parallel In/Serial Out Shift Register

# Parallel In/Parallel Out Shift Register :

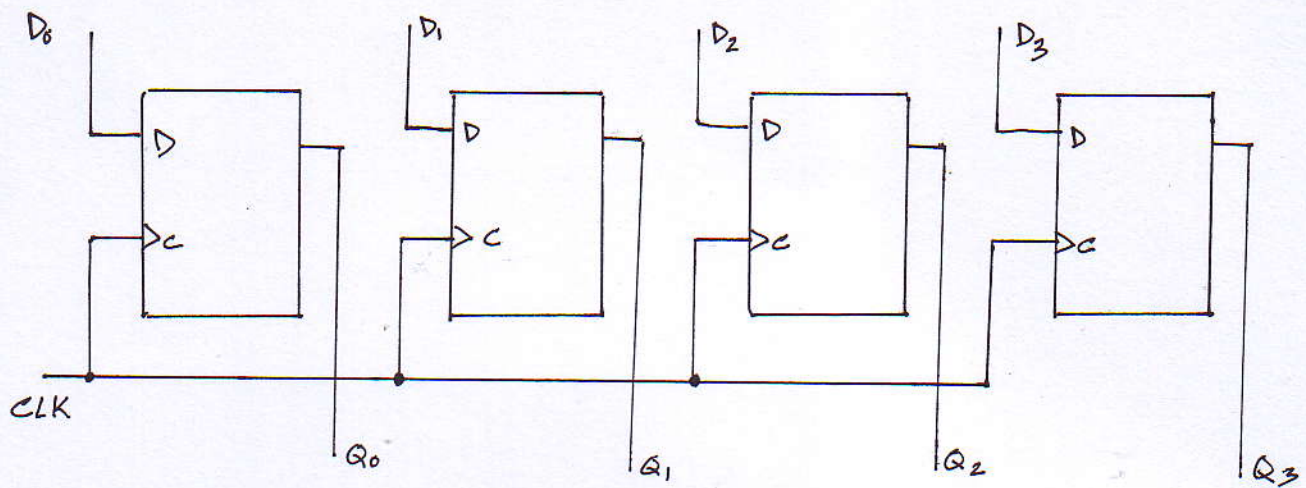


Fig : Four Bit Parallel In/Parallel Out shift Register