



## Lecture – 1

# Introductory Concepts of Digital Logic

### Lesson Outcomes

After completing this lecture, students will be able to

- *Explain the basic differences between digital and analog quantities*
- *Show how voltage levels are used to represent digital quantities*
- *Describe various parameters of a pulse waveform such as rise time, fall time, pulse width, frequency, period, and duty cycle*
- *Explain the basic logic functions of NOT, AND, and OR*
- *Describe several types of logic operations and explain their application in an example system*




# Key Terms


- Analog
- Digital
- Binary
- Bit
- Pulse
- Duty cycle
- Clock
- Timing diagram
- NOT
- Inverter
- AND
- OR
- Programmable logic
- SPLD
- CPLD
- FPGA
- Data
- Serial
- Parallel
- Logic
- Input
- Output
- Gate
- Microcontroller
- Embedded system
- Compiler
- Integrated circuit (IC)
- Fixed-function logic
- Troubleshooting

# Analog vs digital

- ❑ An **analog** quantity is one having continuous values.
- ❑ A **digital** quantity is one having a discrete set of values.

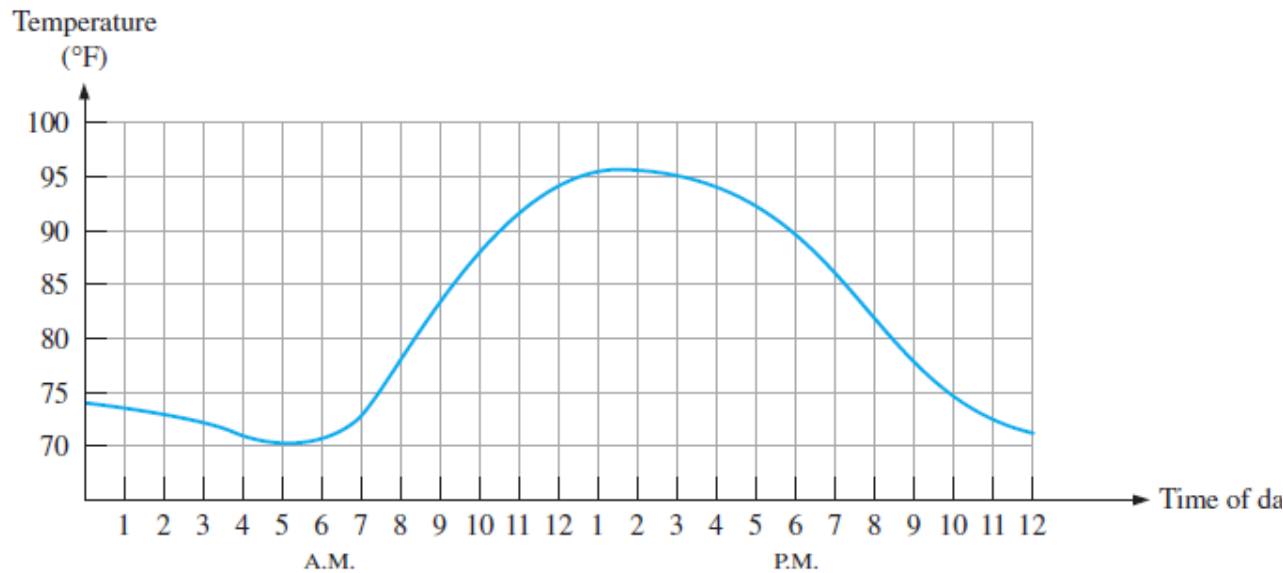



**FIGURE 1-1** Graph of an analog quantity (temperature versus time).

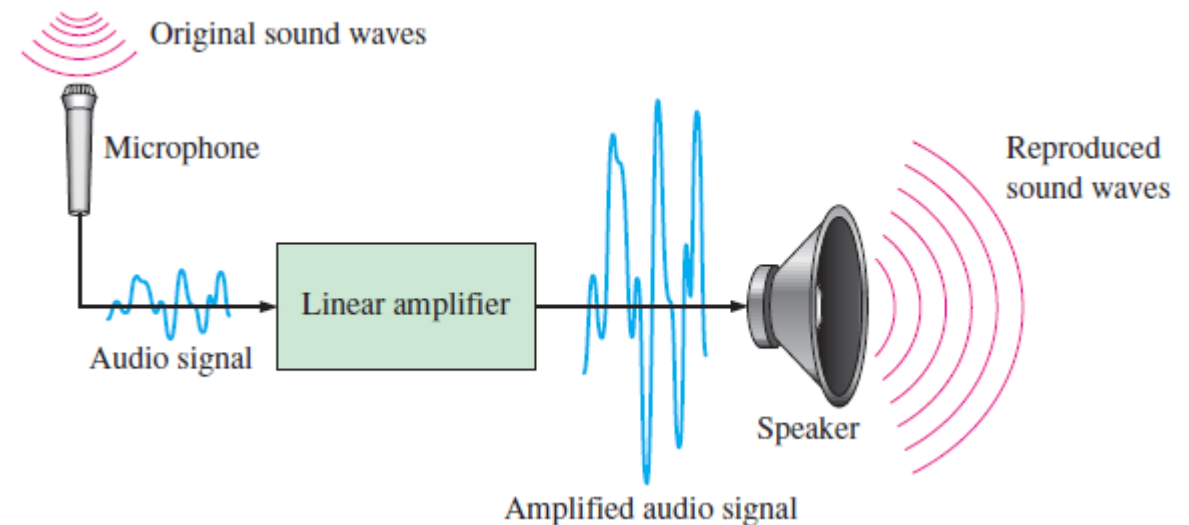

# Analog vs digital

## Advantage of digital over analog:


- ❑ Digital data can be processed and transmitted more efficiently and reliably than analog data.
- ❑ Digital data has a great advantage when storage is necessary.
- ❑ Noise does not affect digital data nearly as much as it does analog signals.

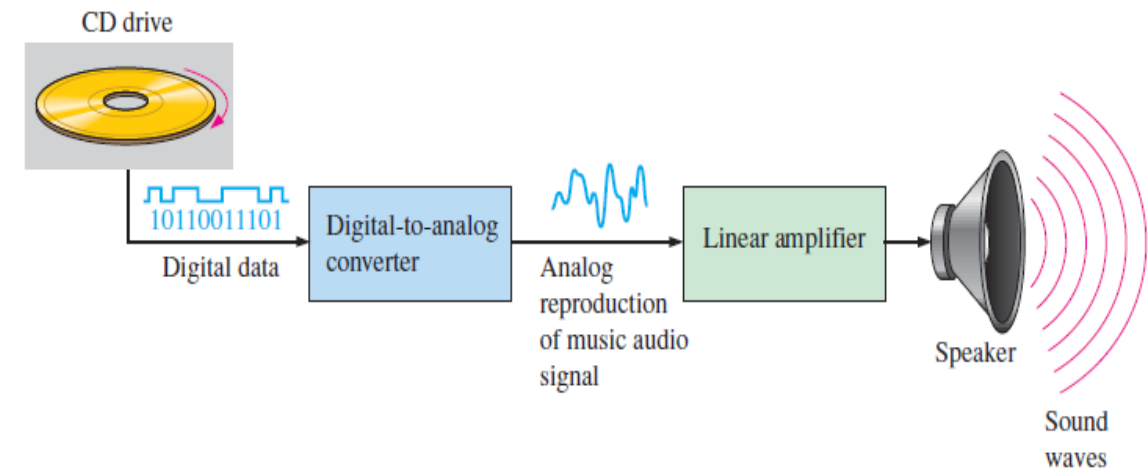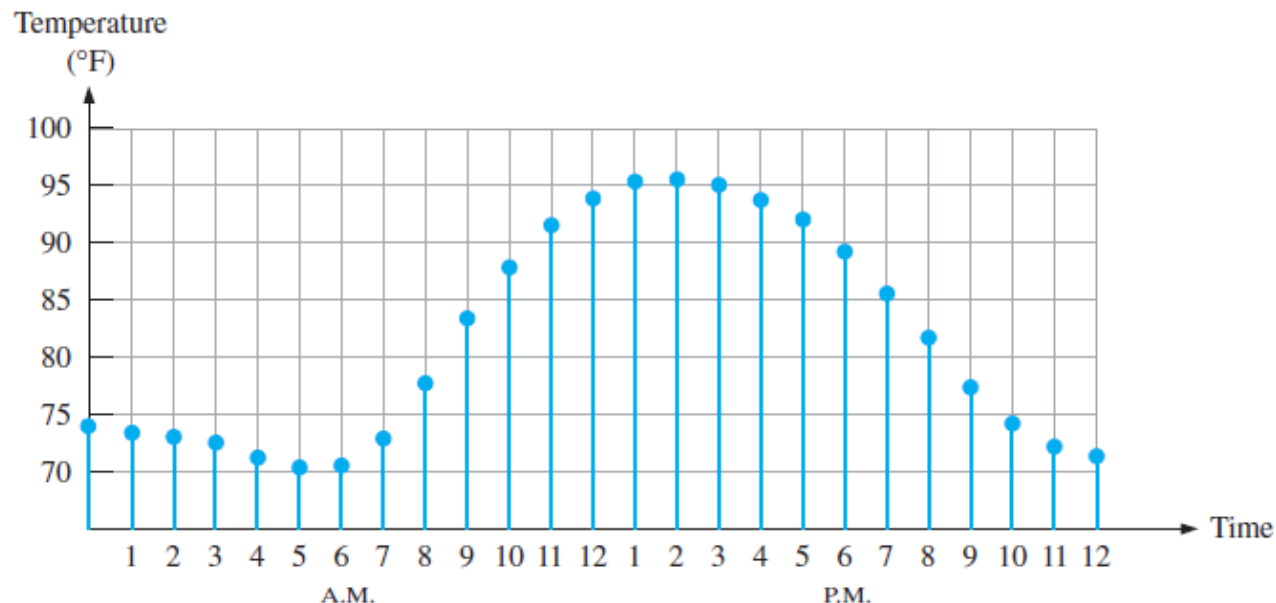


**FIGURE 1-4** Basic block diagram of a CD player. Only one channel is shown.

# Binary digits, logic levels and digital waveform


- Each of the two digits in the **binary** system, 1 and 0, is called a **binary digit** or **bit**.
- In positive logic, 1 represents **HIGH** voltage and 0 represents **LOW** voltage.

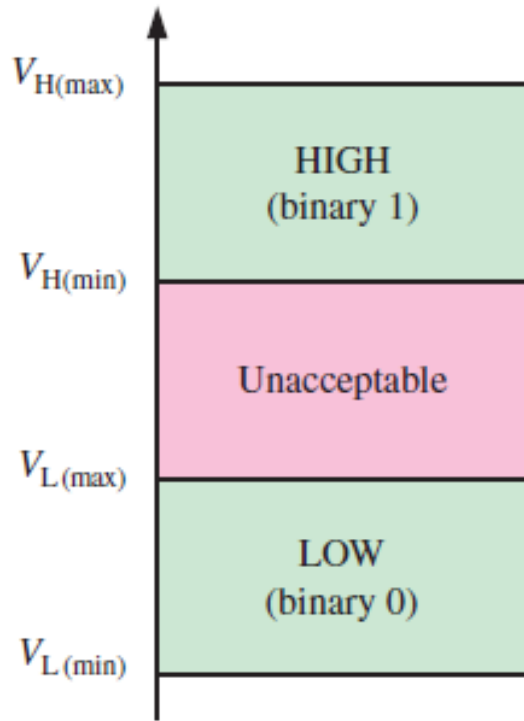

**FIGURE 1-6** Logic level ranges of voltage for a digital circuit.

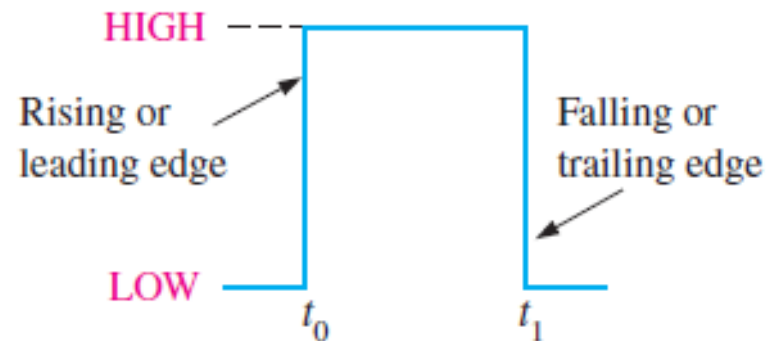


(a) Positive-going pulse

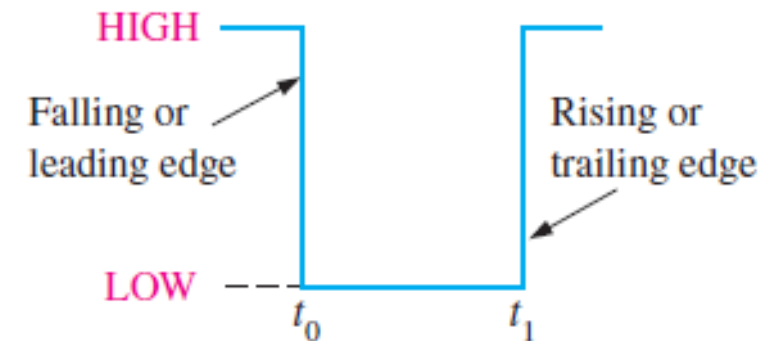


(b) Negative-going pulse

**FIGURE 1-7** Ideal pulses.

# Non ideal pulse

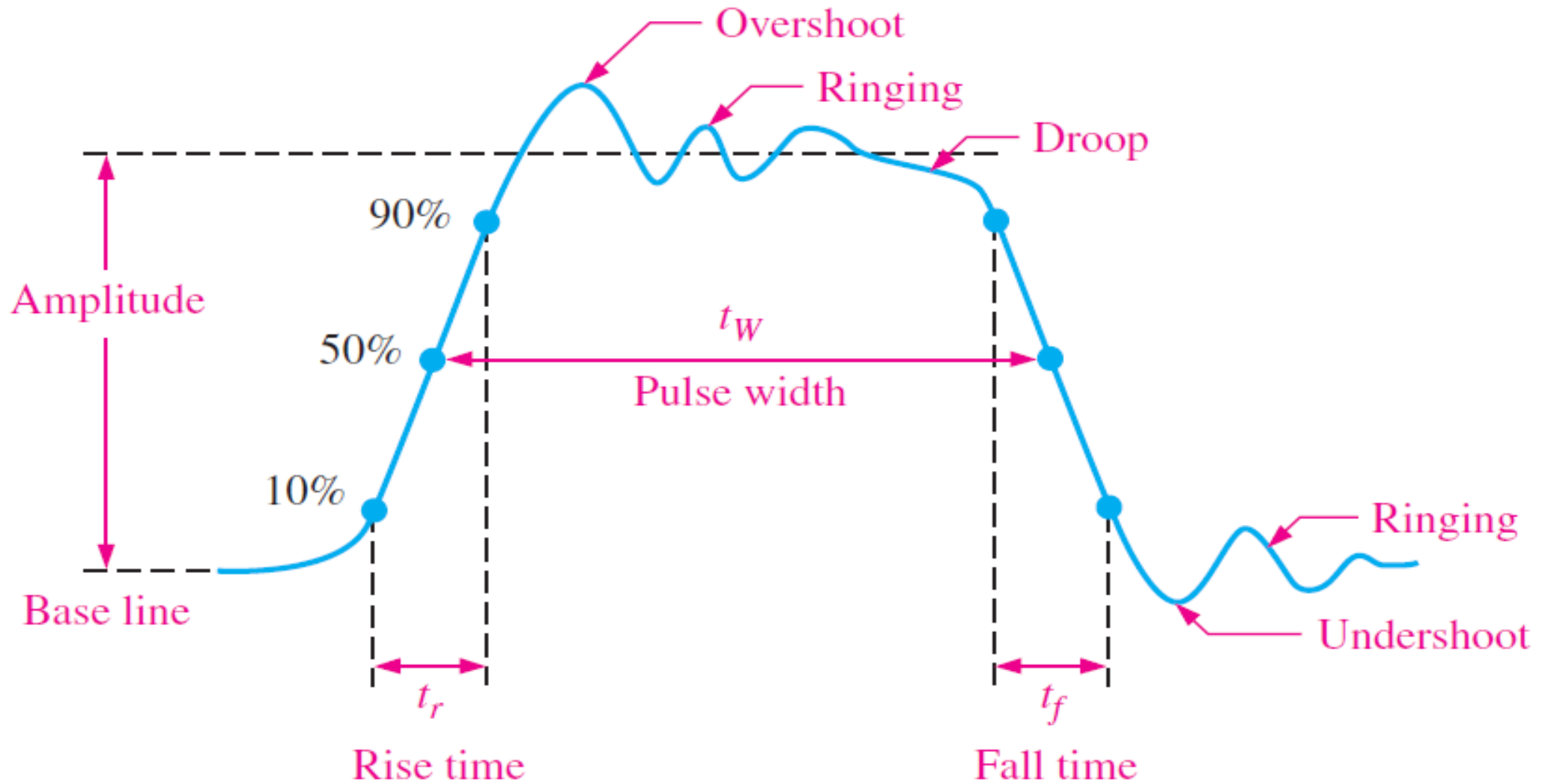


# Digital waveform characteristics

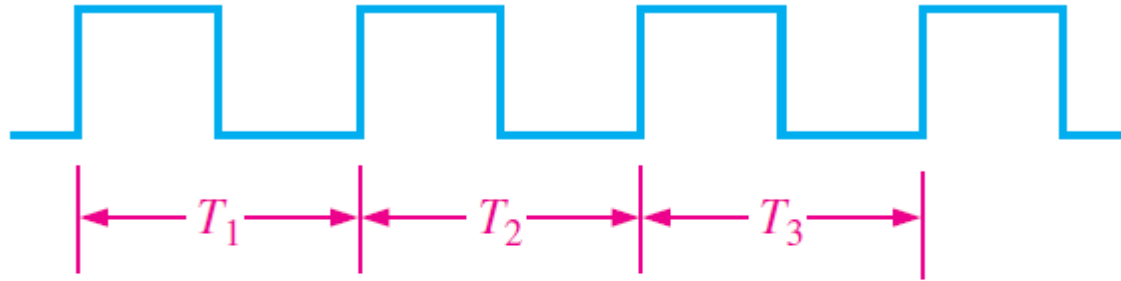

Period =  $T_1 = T_2 = T_3 = \dots = T_n$


Frequency =  $\frac{1}{T}$

(a) Periodic (square wave)

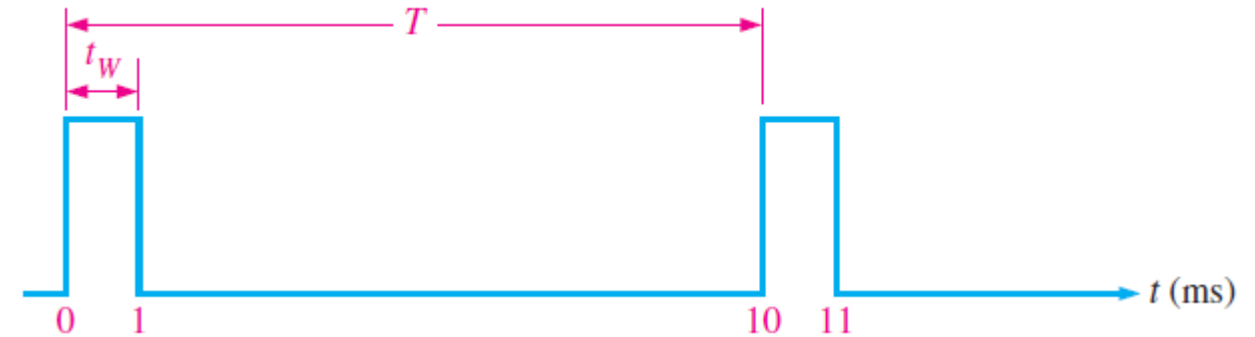

(b) Nonperiodic

$$\text{Duty cycle} = \left( \frac{t_w}{T} \right) 100\%$$

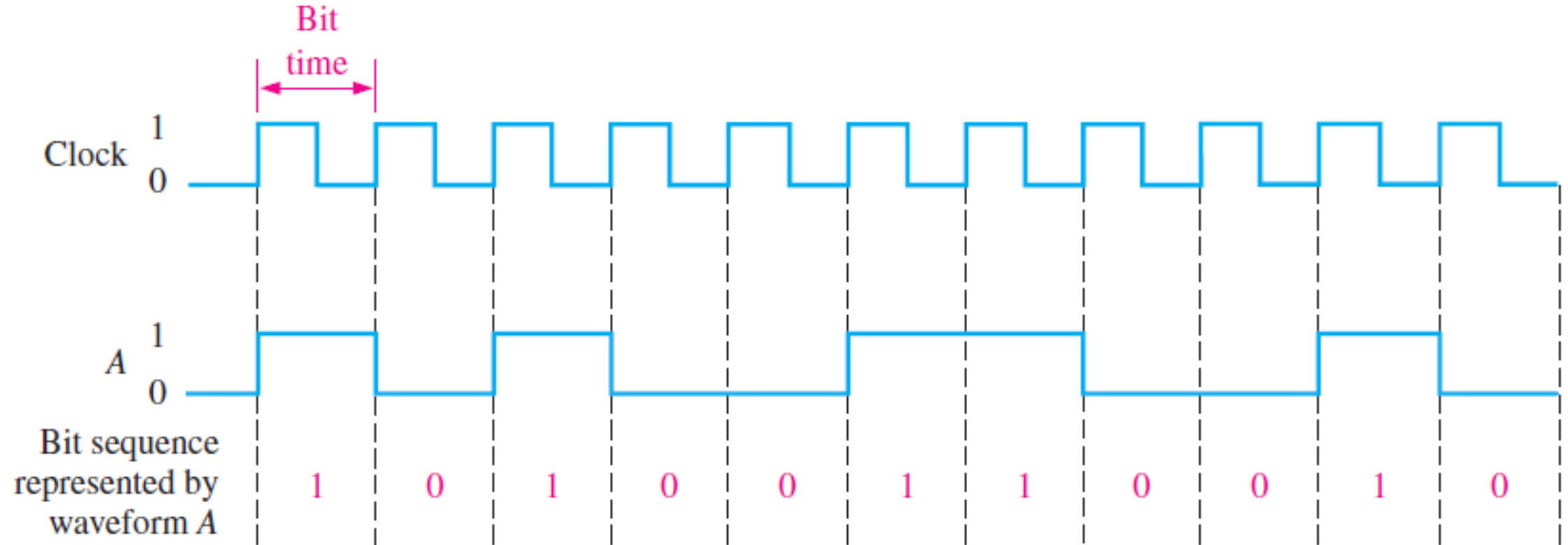


**FIGURE 1-11** Example of a clock waveform synchronized with a waveform representation of a sequence of bits.



# Timing diagram


- ❑ A *timing diagram* is basically a graph that accurately displays the relationship of two or more waveforms with respect to each other on a time basis.

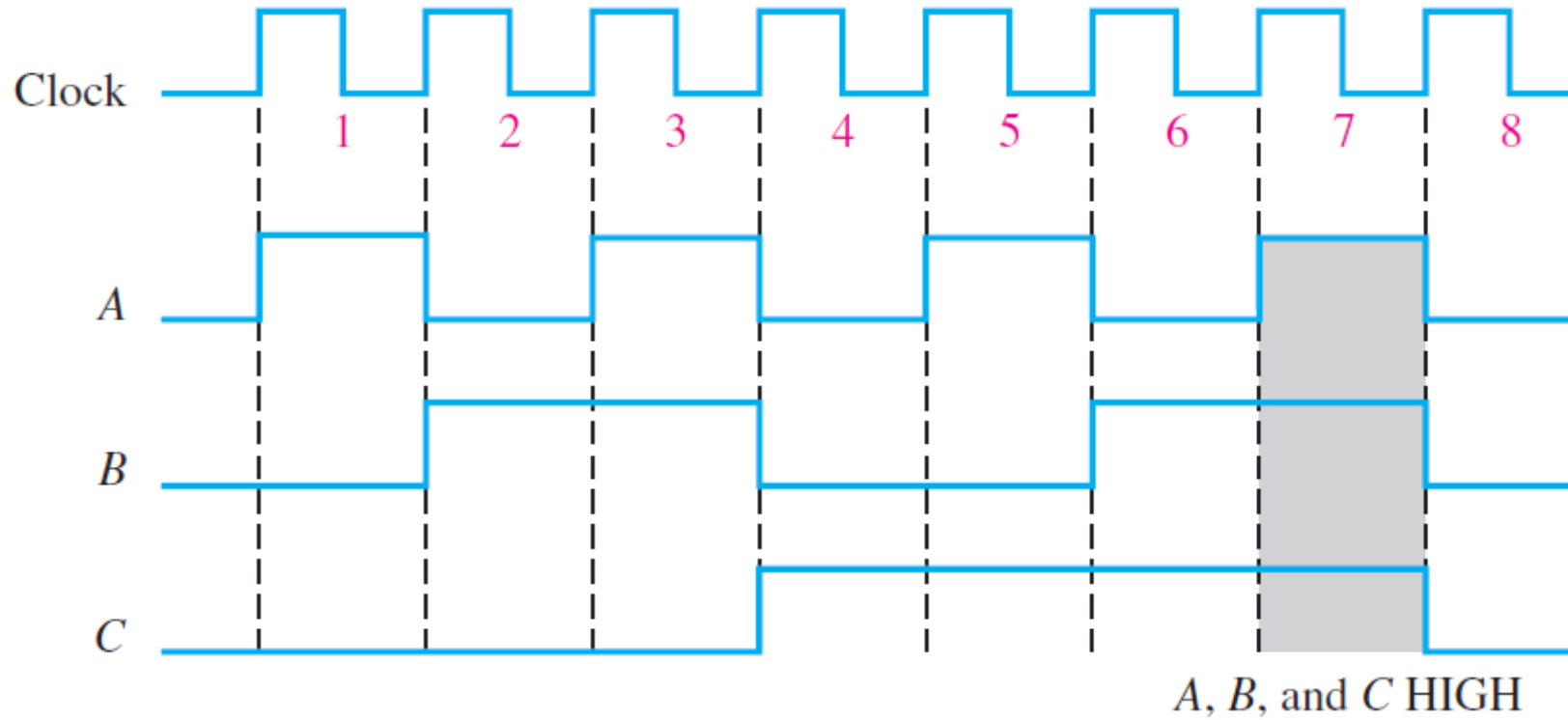


**FIGURE 1-12** Example of a timing diagram.

❑ Binary data are transferred in two ways: **serial** and **parallel**.

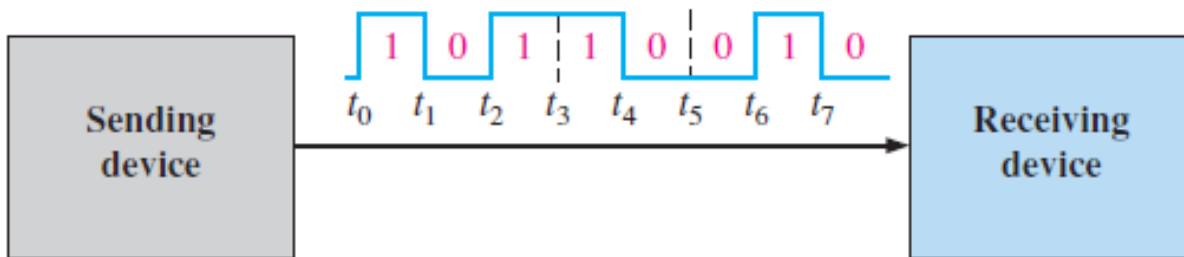- ✓ When bits are transferred in **serial** form from one point to another, they are sent one bit at a time along a single line.
- ✓ When bits are transferred in **parallel** form, all the bits in a group are sent out on separate lines at the same time.



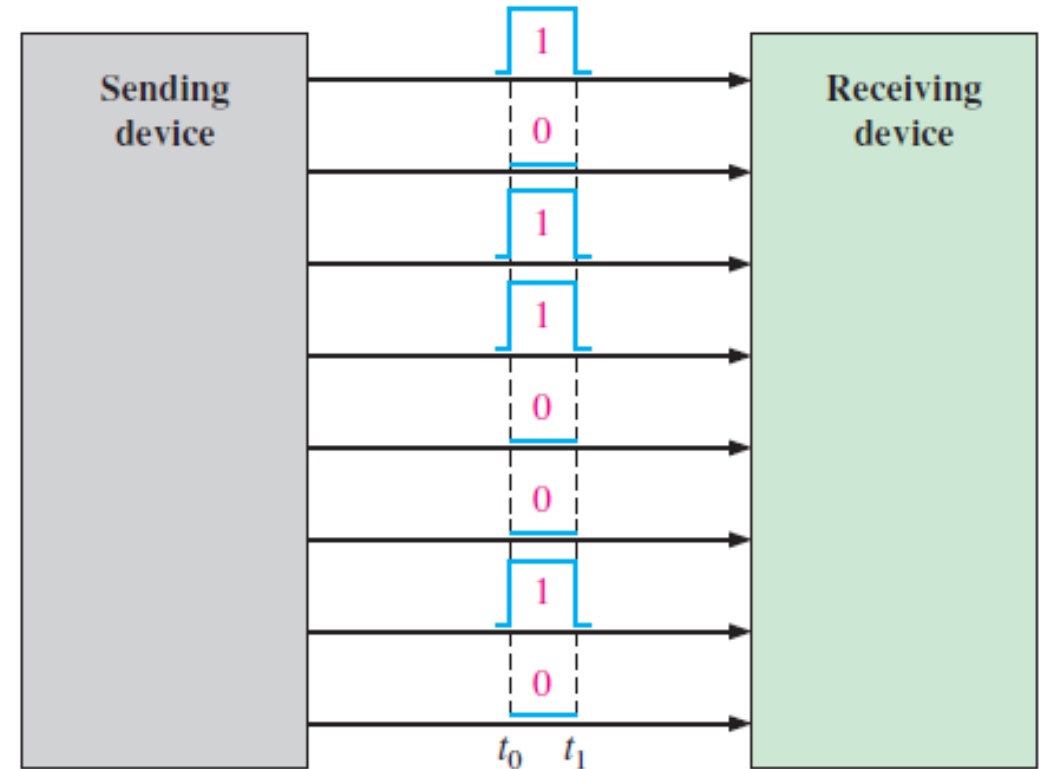(a) Serial transfer of 8 bits of binary data. Interval  $t_0$  to  $t_1$  is first.



(b) Parallel transfer of 8 bits of binary data. The beginning time is  $t_0$ .



# Example 1-1

- a) Determine the total time required to serially transfer the eight bits contained in waveform *A*, and indicate the sequence of bits. The left-most bit is the first to be transferred. The 1 MHz clock is used as reference.
- b) What is the total time to transfer the same eight bits in parallel?

## SOLUTION:

- (a) Since the frequency of the clock is 1 MHz,


$$\text{the period is } T = \frac{1}{f} = \frac{1}{1 \text{ MHz}} = 1 \mu\text{s}$$

It takes  $1 \mu\text{s}$  to transfer each bit in the waveform.

The total transfer time for 8 bits is

$$8 \times 1 \mu\text{s} = 8 \mu\text{s}$$

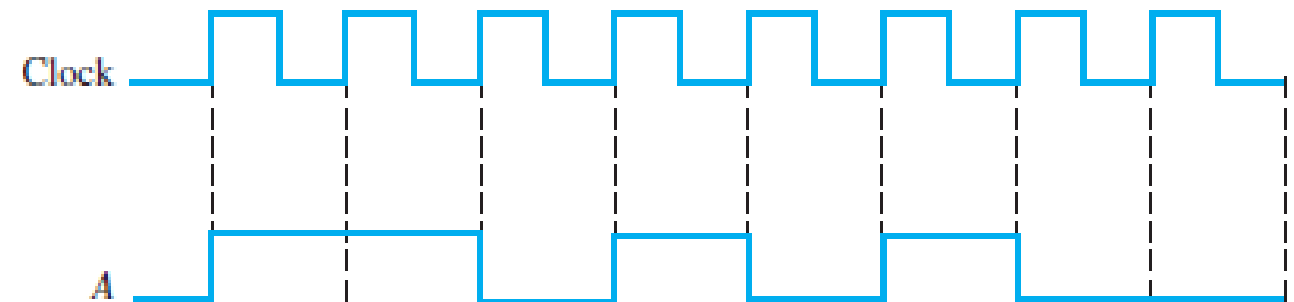
- (b) A parallel transfer would take  $1 \mu\text{s}$  for all eight bits.




Sequence of bits:




# Basic logic functions

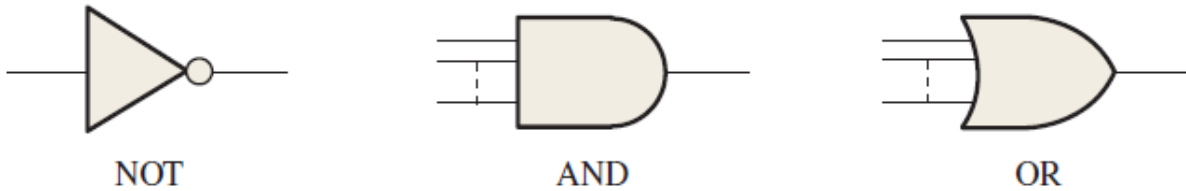


**FIGURE 1-16** The basic logic functions and symbols.

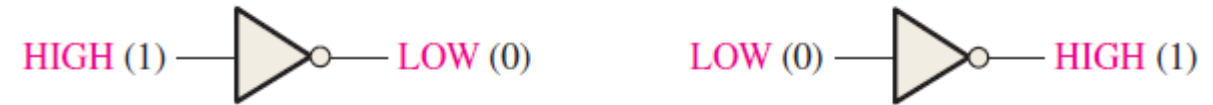

**FIGURE 1-17** The NOT function.

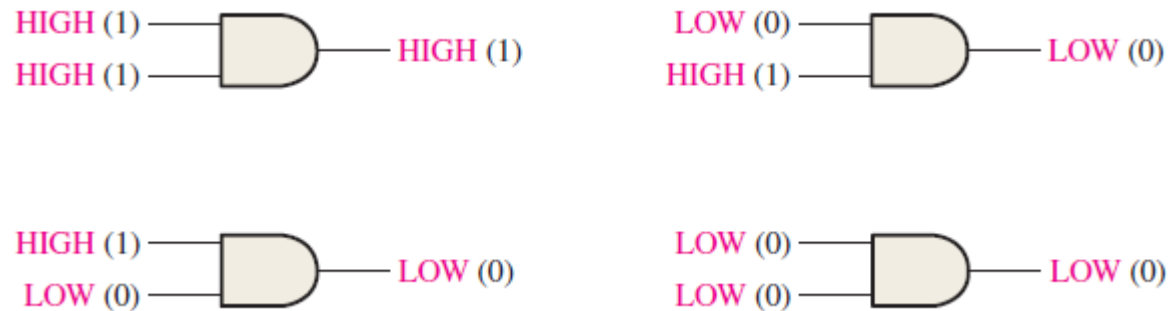


**FIGURE 1-18** The AND function.

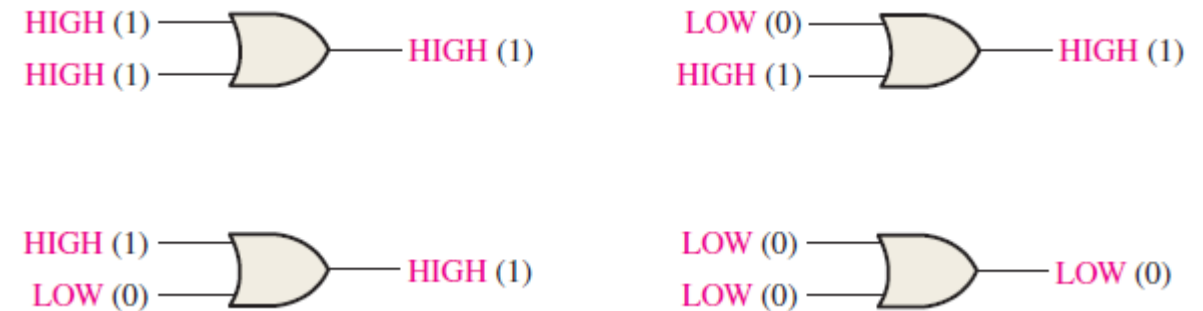


**FIGURE 1-19** The OR function.
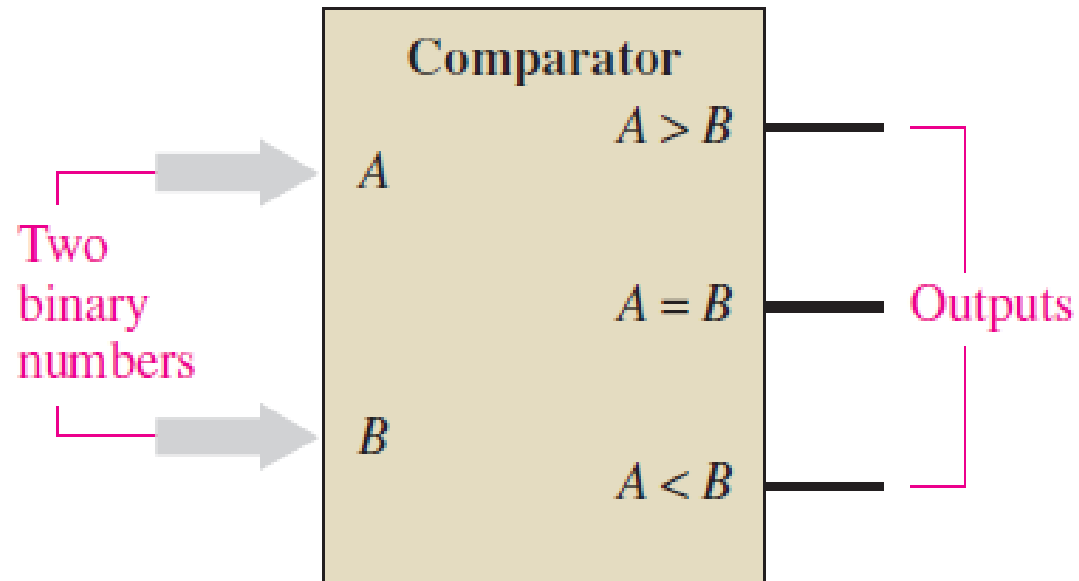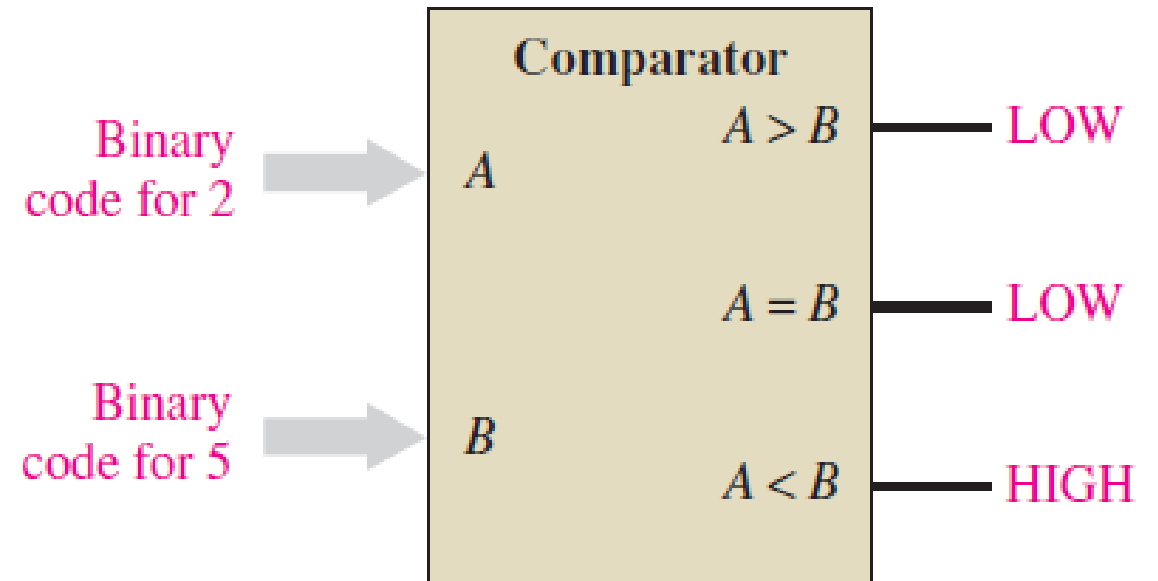
# Combinational and sequential logic functions




(a) Basic magnitude comparator




(b) Example:  $A$  is less than  $B$  ( $2 < 5$ ) as indicated by the HIGH output ( $A < B$ )

**FIGURE 1-20** The comparison function.
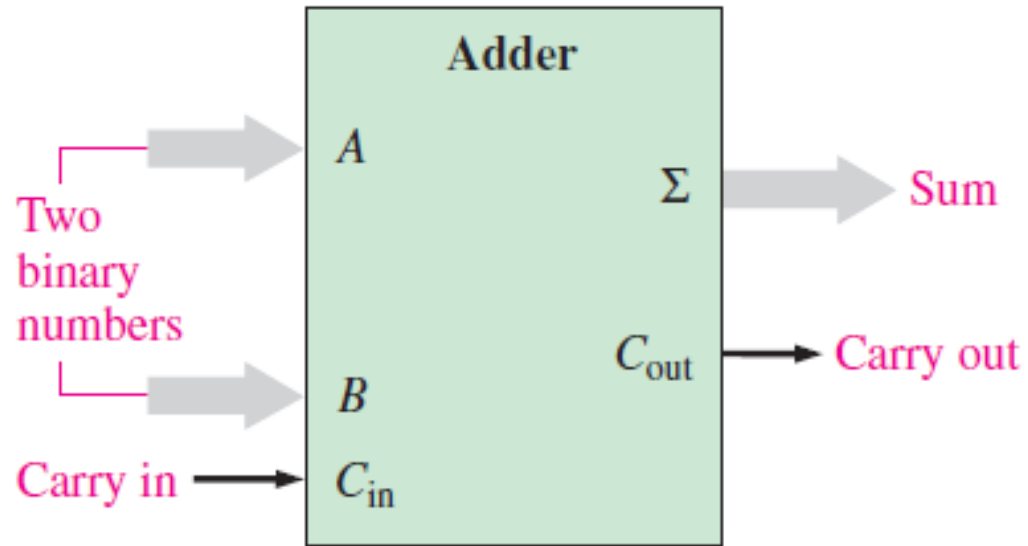
# Combinational and sequential logic functions




(a) Basic adder

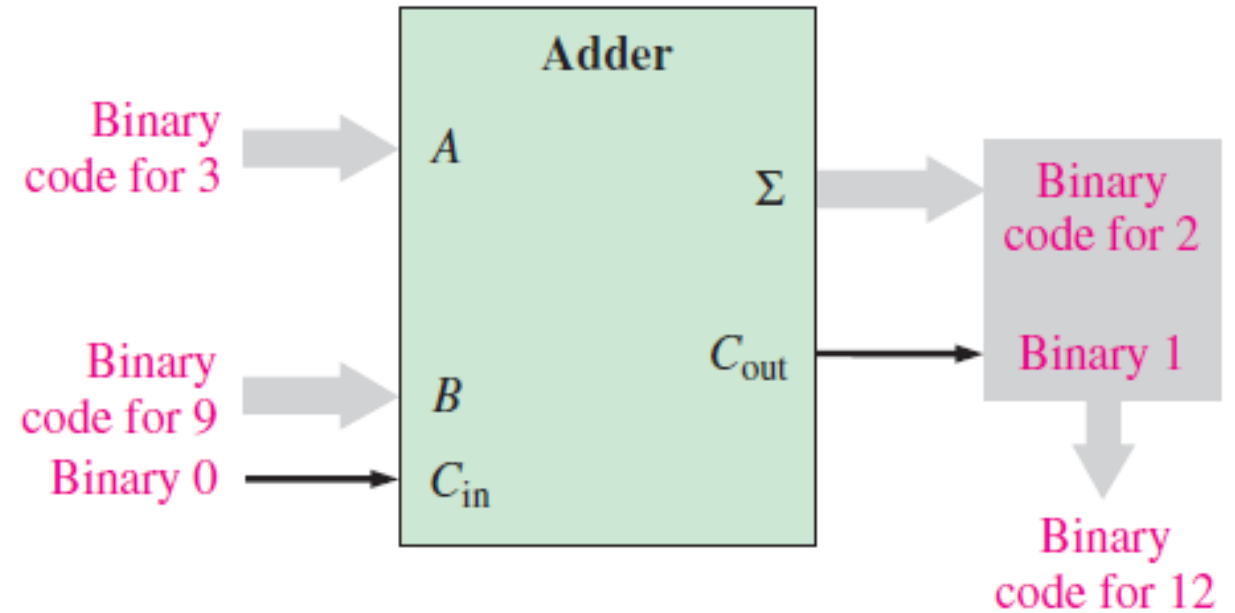

(b) Example:  $A$  plus  $B$  ( $3 + 9 = 12$ )

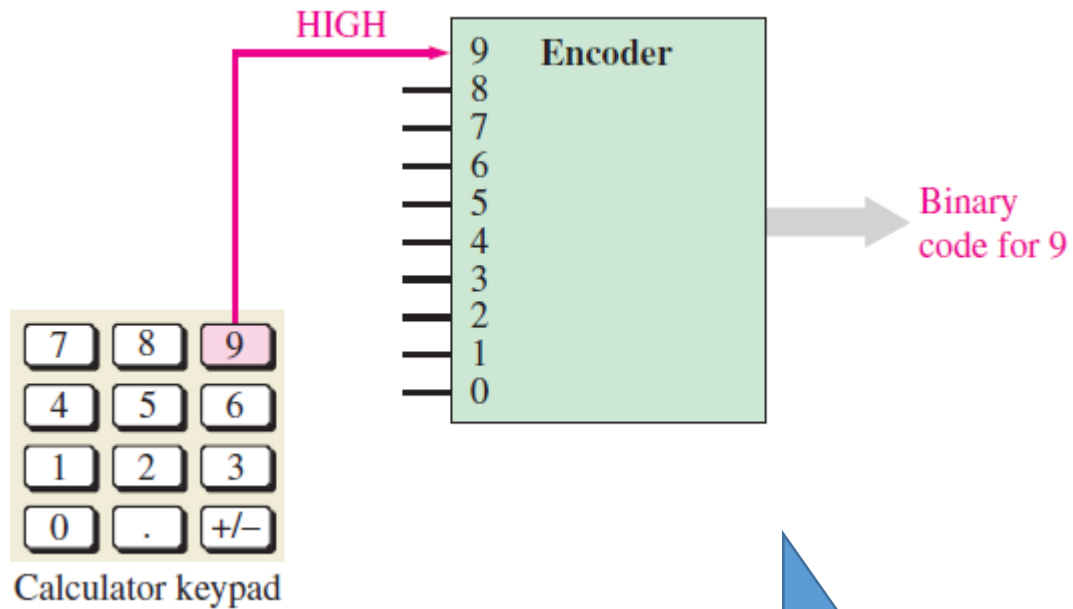
# Combinational and sequential logic functions




An **encoder** used to encode a calculator keystroke into a binary code for storage or for calculation.

A **decoder** used to convert a special binary code into a 7-segment decimal readout.

Binary-coded input

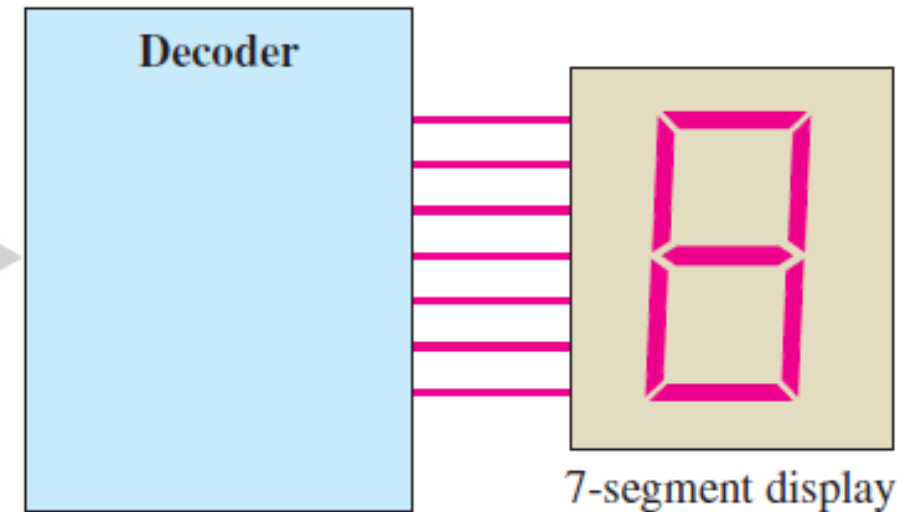

# Data selection functions (multiplexing-demultiplexing)

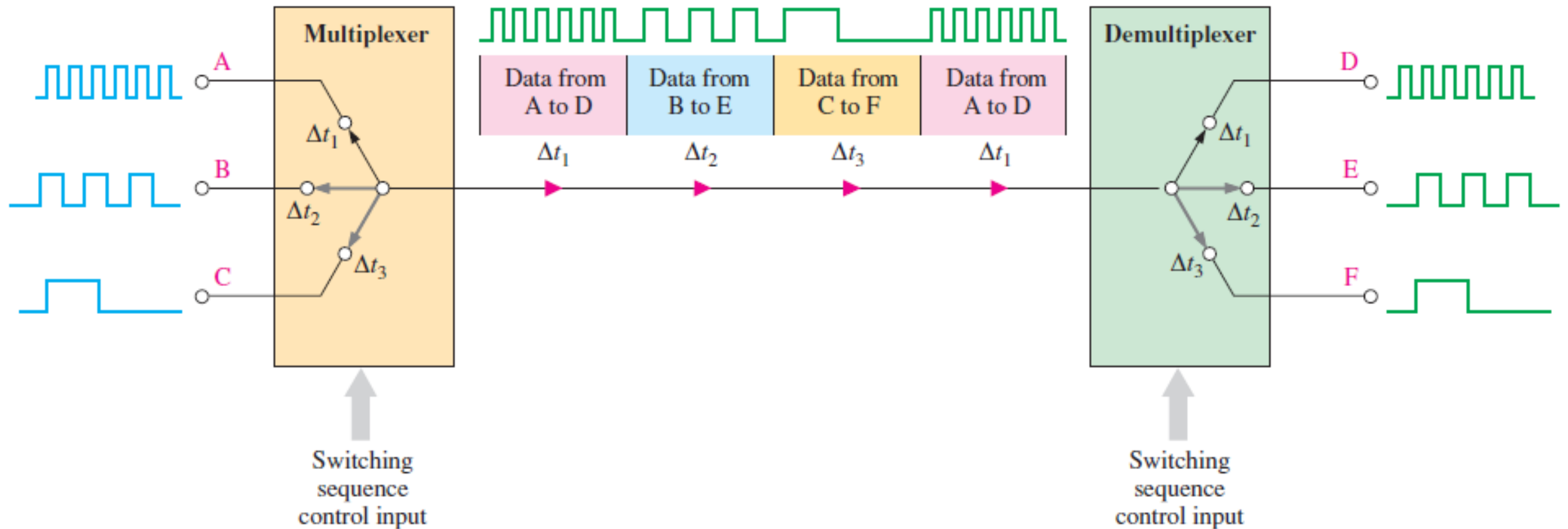


**FIGURE 1-24** Illustration of a basic multiplexing/demultiplexing application.

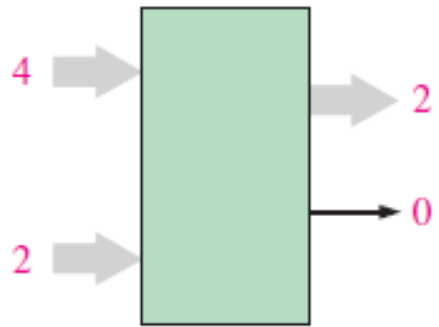


# Example 1-2


**Problems:** Based on your observation of the inputs and outputs, name the logic function of each block shown in Figures.




(a)

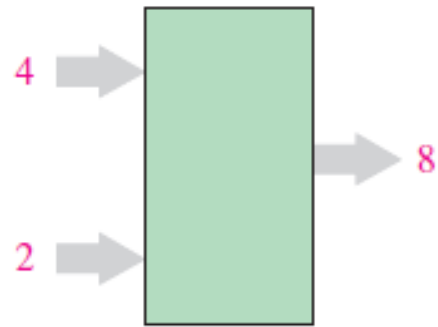

(b)

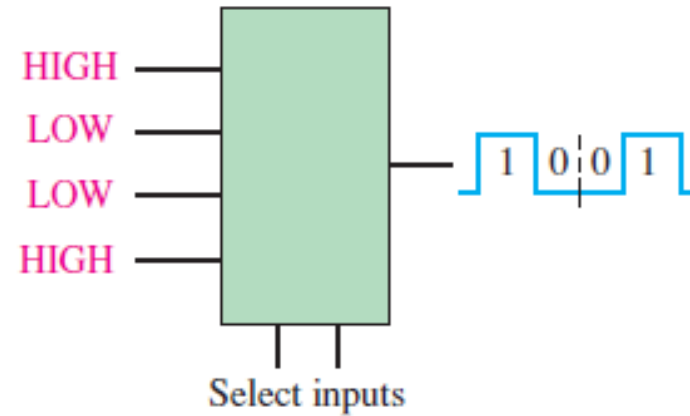

(c)

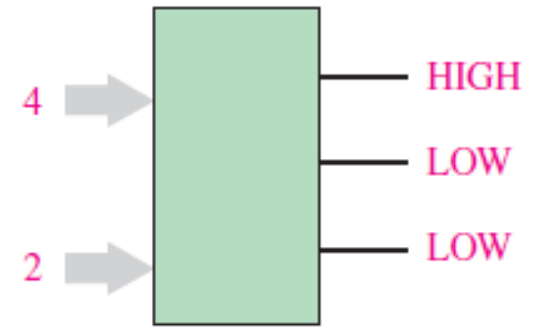

(d)

**ANSWER:**


(a) Subtractor

(b) Multiplier


(c) Multiplexure

(d) Comparator

# Data storage function (register)

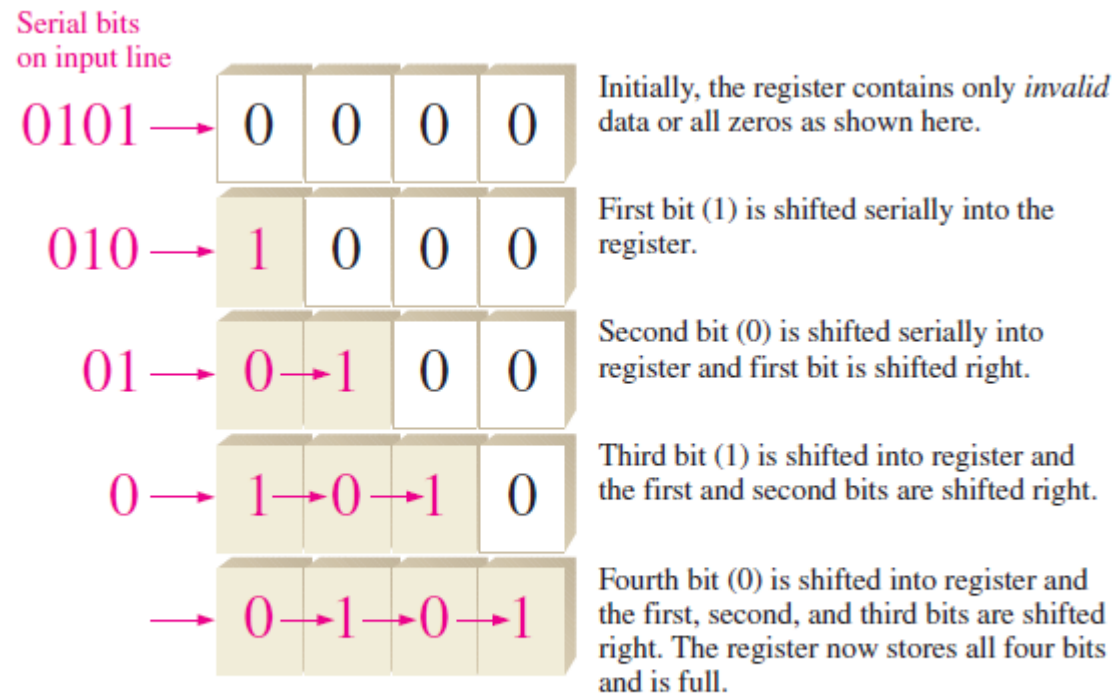


**FIGURE 1-25** Example of the operation of a 4-bit serial shift register. Each block represents one storage “cell” or flip-flop.

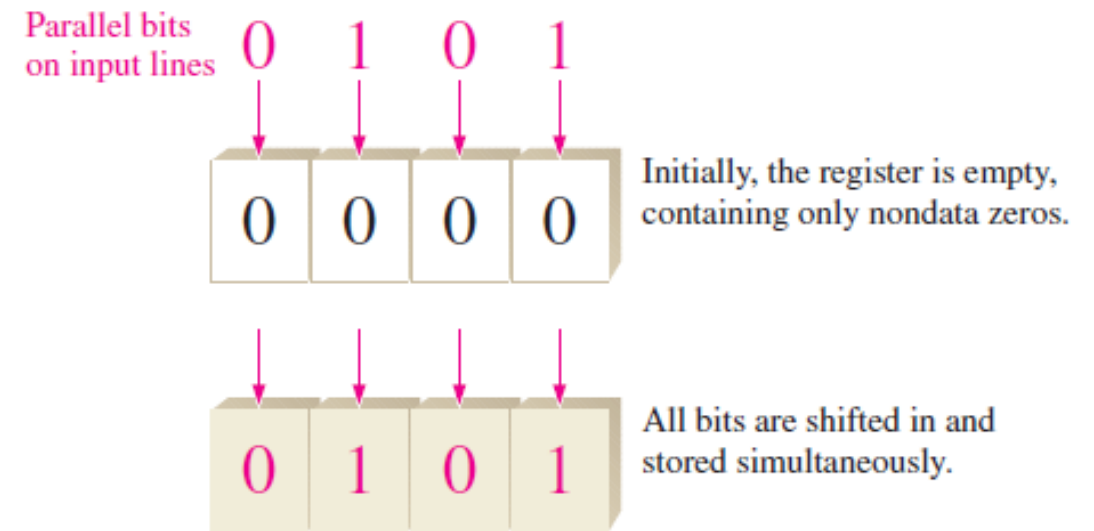


**6** Example of the operation of a 4-bit parallel shift register.

# Counting function

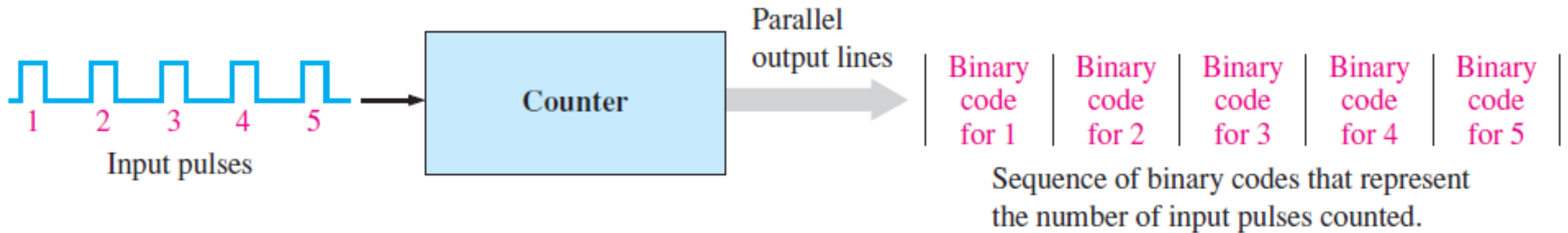

**FIGURE 1-27** Illustration of basic counter operation.
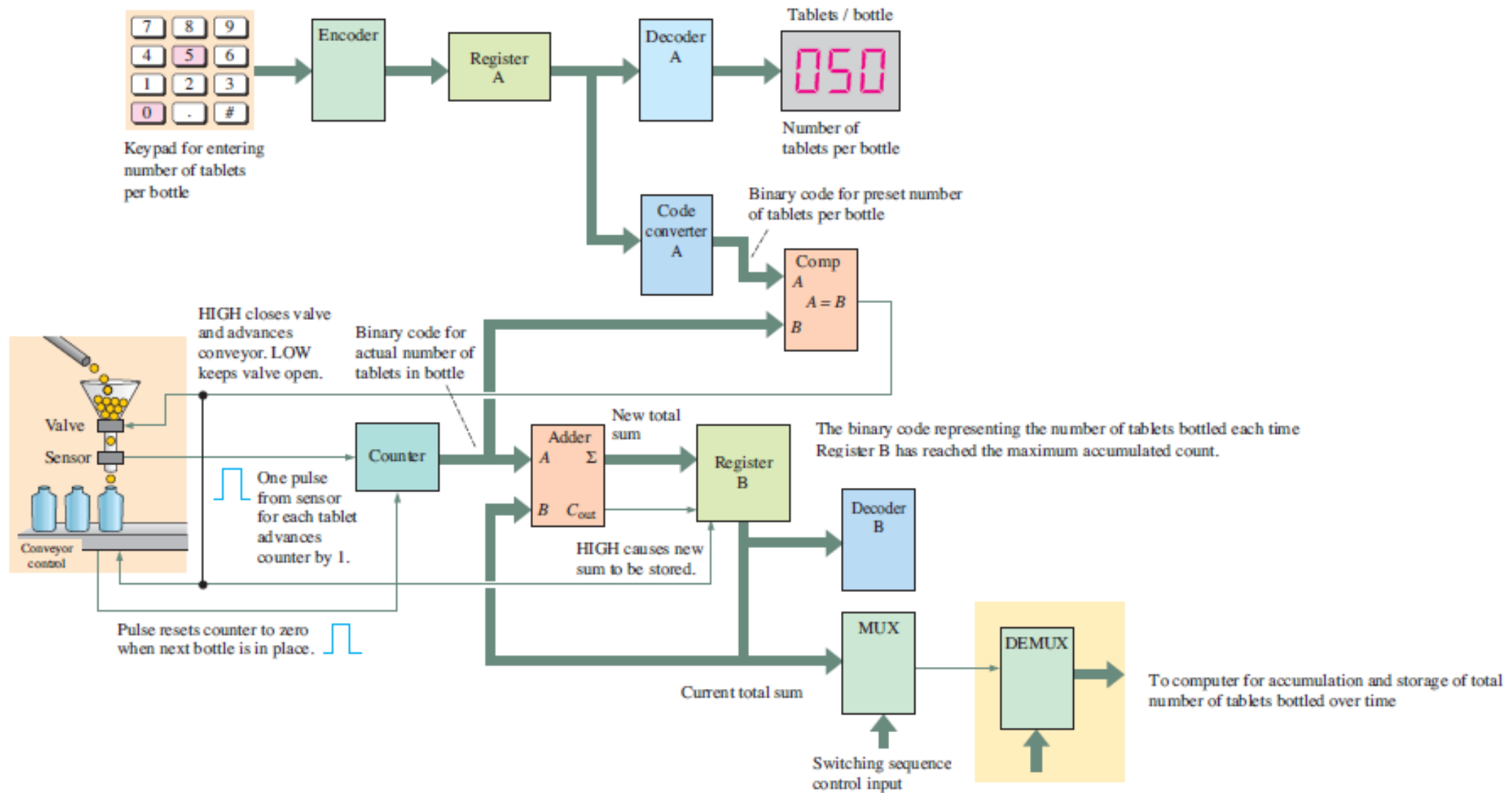
# Process control (tablet bottling system)



Digital integrated circuits (ICs) are two types:

(1) Fixed Function Logic Devices (FLDs)


(2) Programmable Logic Devices (PLDs)

❑ Many types of programmable logic are available, two major categories of user-programmable logic are:


- **PLD** (programmable logic device)
- **FPGA** (field-programmable gate array)

❑ PLDs are two types:

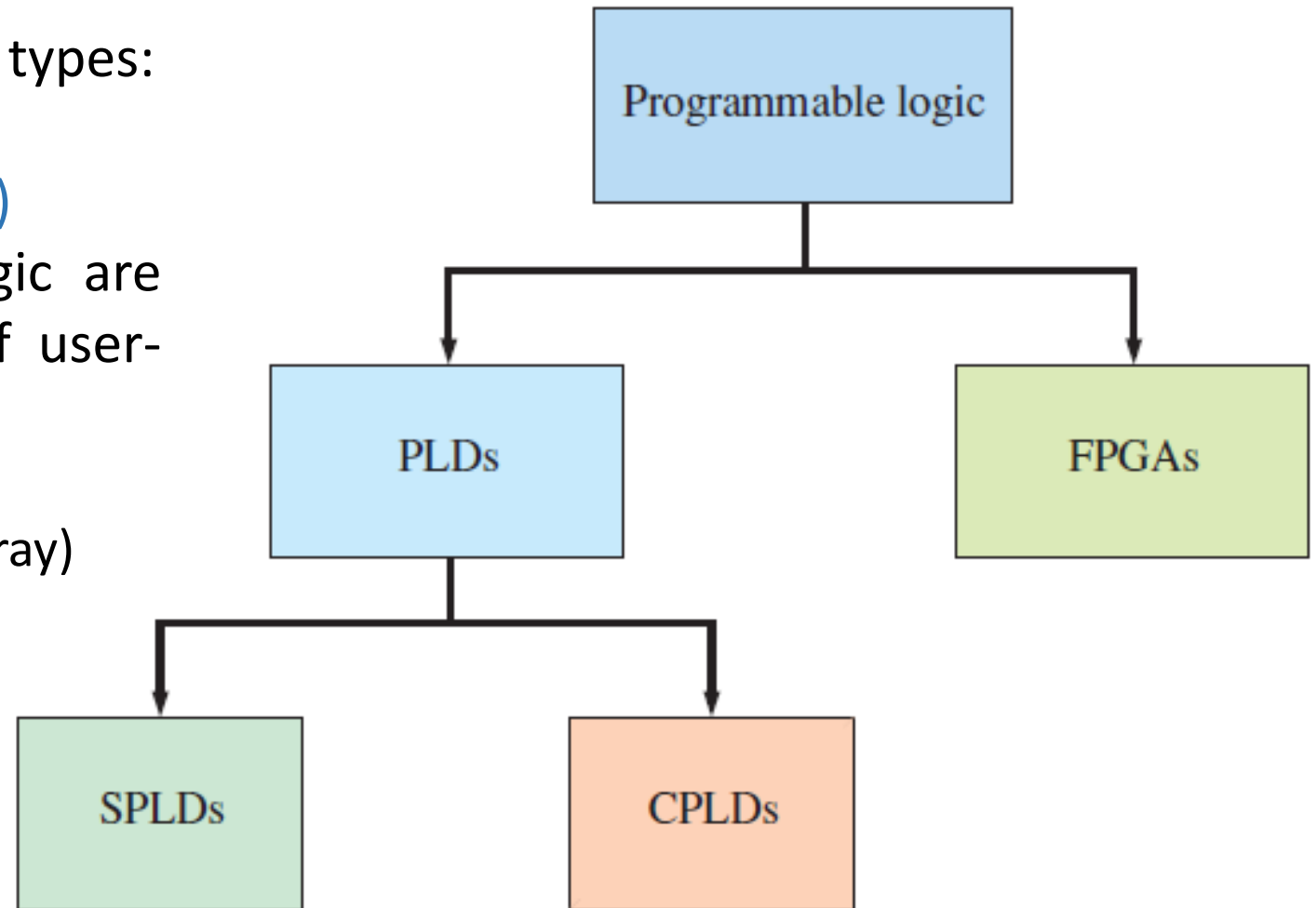- ✓ SPLDs (simple PLDs)
- ✓ CPLDs (complex PLDs)




# Simple programmable logic devices

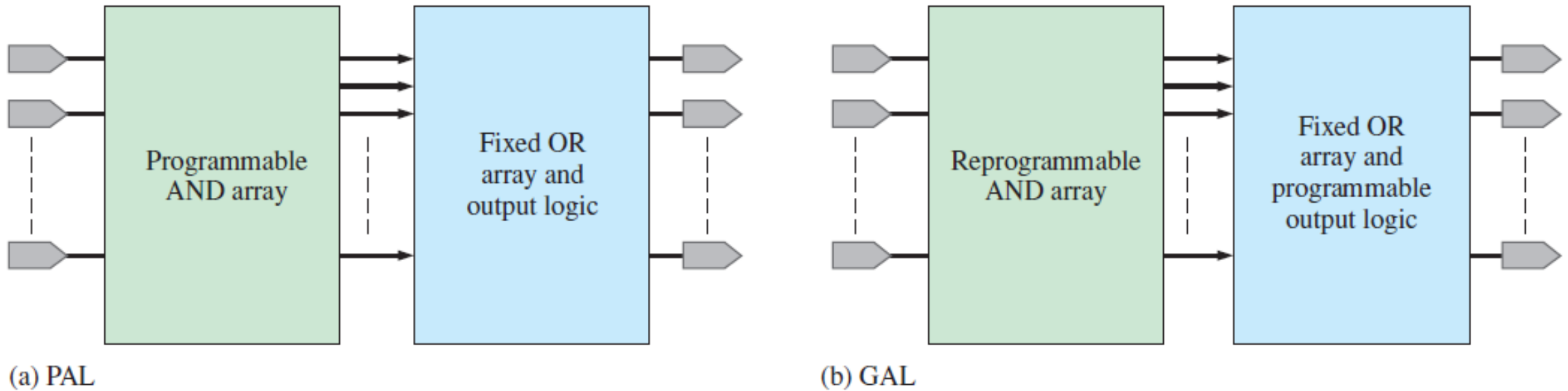

**FIGURE 1-30** Block diagrams of simple programmable logic devices (SPLDs).

# Complex programmable logic devices

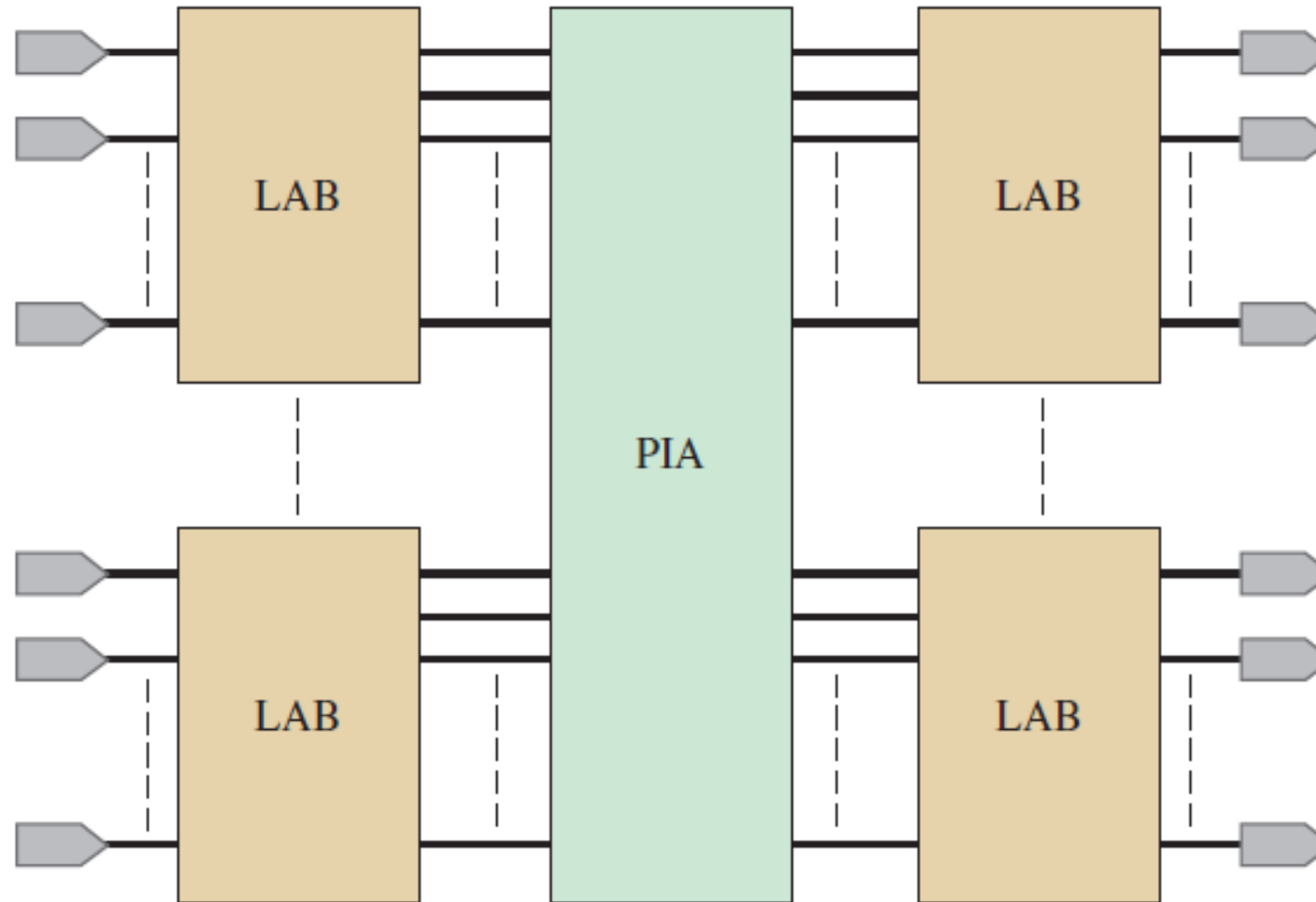

**FIGURE 1-32** General block diagram of a CPLD.

# Field programmable gate array


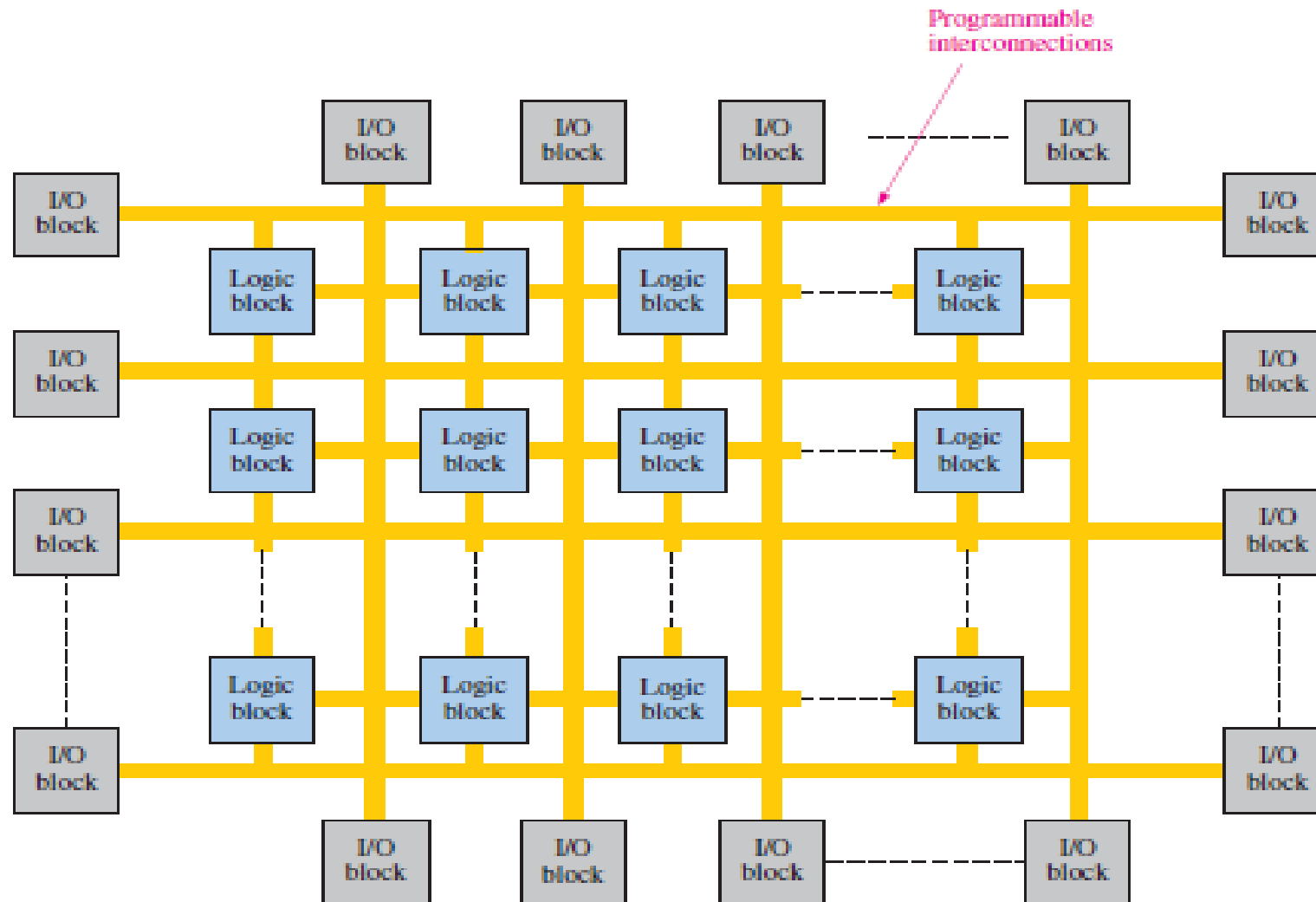



FIGURE 1-34 Basic structure of an FPGA.

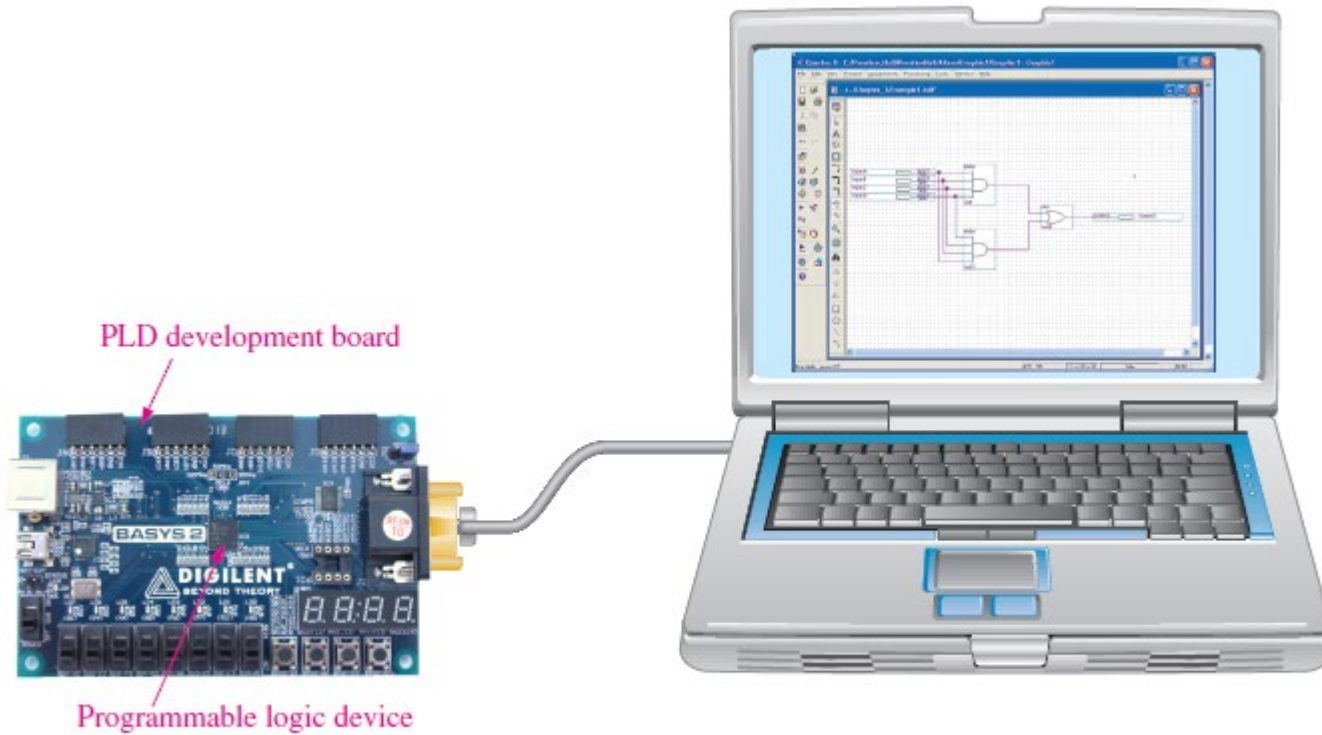

# Programming process




**FIGURE 1-36** Basic setup for programming a PLD or FPGA. Graphic entry of a logic circuit is shown for illustration. Text entry such as VHDL can also be used. (Photo courtesy of Digilent, Inc.)

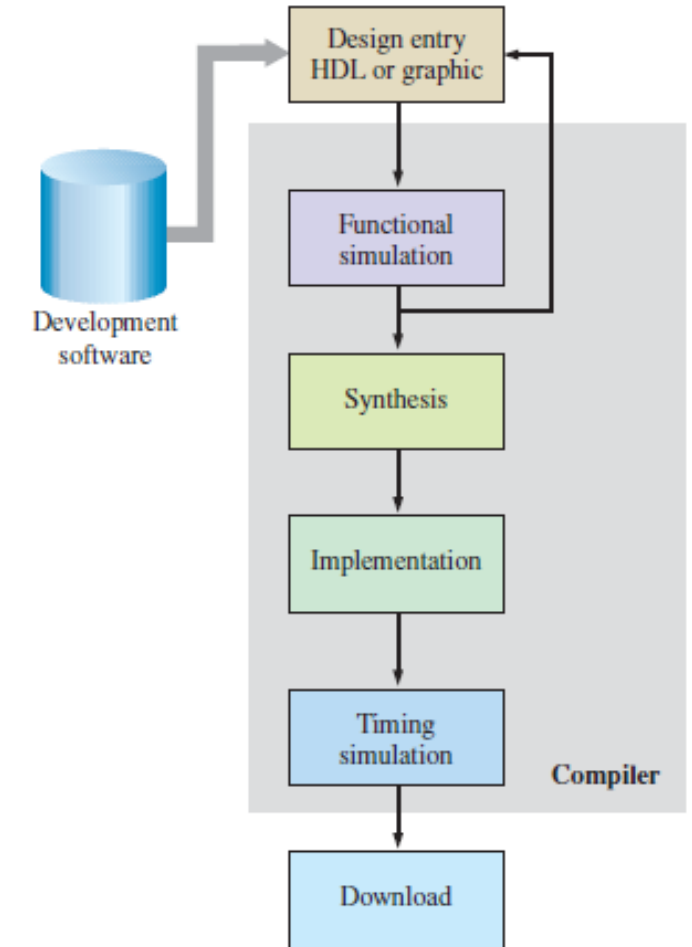

**FIGURE 1-37** Basic programmable logic design flow block diagram.

# Fixed function logic devices


- ❑ An **integrated circuit (IC)** is an electronic circuit that is constructed entirely on a single small chip of silicon.
- ❑ All the components that make up the circuit—transistors, diodes, resistors, and capacitors—are an integral part of that single chip.
- ❑ Fixed-function logic and programmable logic are two broad categories of digital ICs.
- ❑ In **fixed-function logic** devices, the logic functions are set by the manufacturer and cannot be altered.

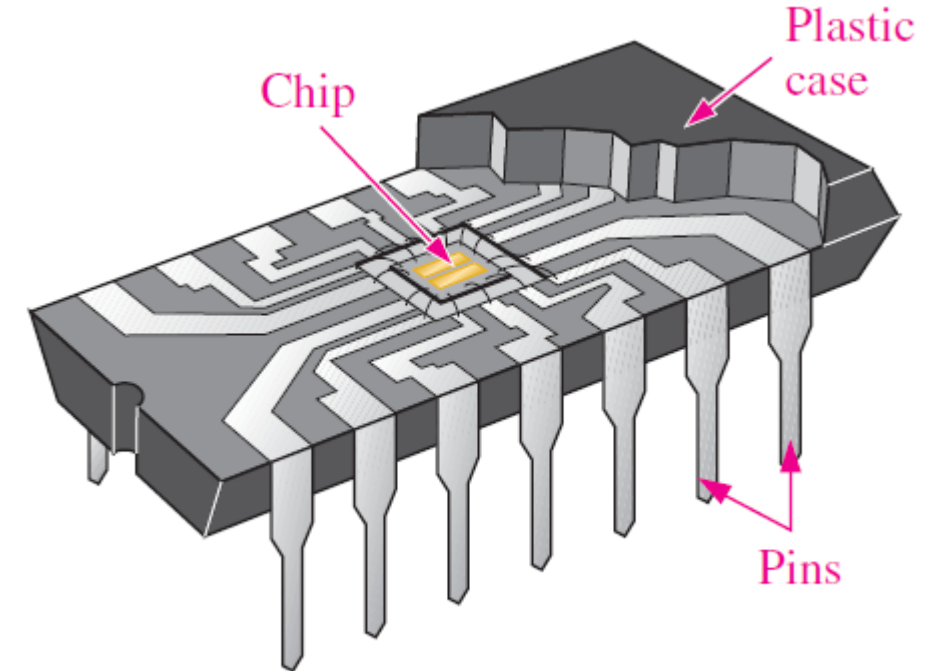


**FIGURE** Cutaway view of one type of fixed-function IC package (dual in-line package) showing the chip mounted inside, with connections to input and output pins
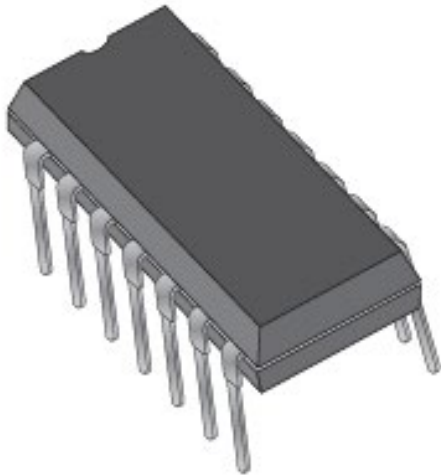
# Fixed function logic devices

- ❑ Integrated circuit (IC) packages are classified according to the way they are mounted on printed circuit boards (PCBs) as either through-hole mounted or surface mounted
- ✓ Dual in-line packages (DIP)
- ✓ Small-outline integrated circuit packages (SOIC)
- ✓ Plastic leaded chip carrier packages (PLCC)
- ✓ Leadless ceramic chip carrier packages (LCC)




(a) Dual in-line package (DIP)

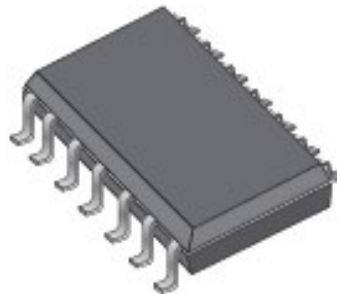

(b) Small-outline IC (SOIC)



(b) PLCC (350 × 350 mils)

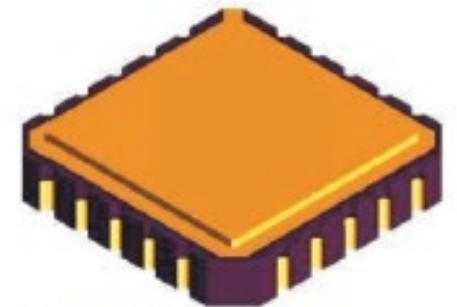


(c) LCC (350 × 350 mils)



# Fixed function logic devices

- ❑ **Fixed-function digital ICs are classified according to their complexity.**
  - ✓ **Small-scale integration (SSI)** describes fixed-function ICs that have up to ten equivalent gate circuits on a single chip, and they include basic gates and flip-flops.
  - ✓ **Medium-scale integration (MSI)** describes integrated circuits that have from 10 to 100 equivalent gates on a chip. They include logic functions such as encoders, decoders, counters, registers, multiplexers, arithmetic circuits, small memories, and others.
  - ✓ **Large-scale integration (LSI)** is a classification of ICs with complexities of from more than 100 to 10,000 equivalent gates per chip, including memories.
  - ✓ **Very large-scale integration (VLSI)** describes integrated circuits with complexities of from more than 10,000 to 100,000 equivalent gates per chip.
  - ✓ **Ultra large-scale integration (ULSI)** describes very large memories, larger **microprocessors**, and larger single-chip computers. Complexities of more than 100,000 equivalent gates per chip are classified as ULS.

# Measurement instruments - digital oscilloscope

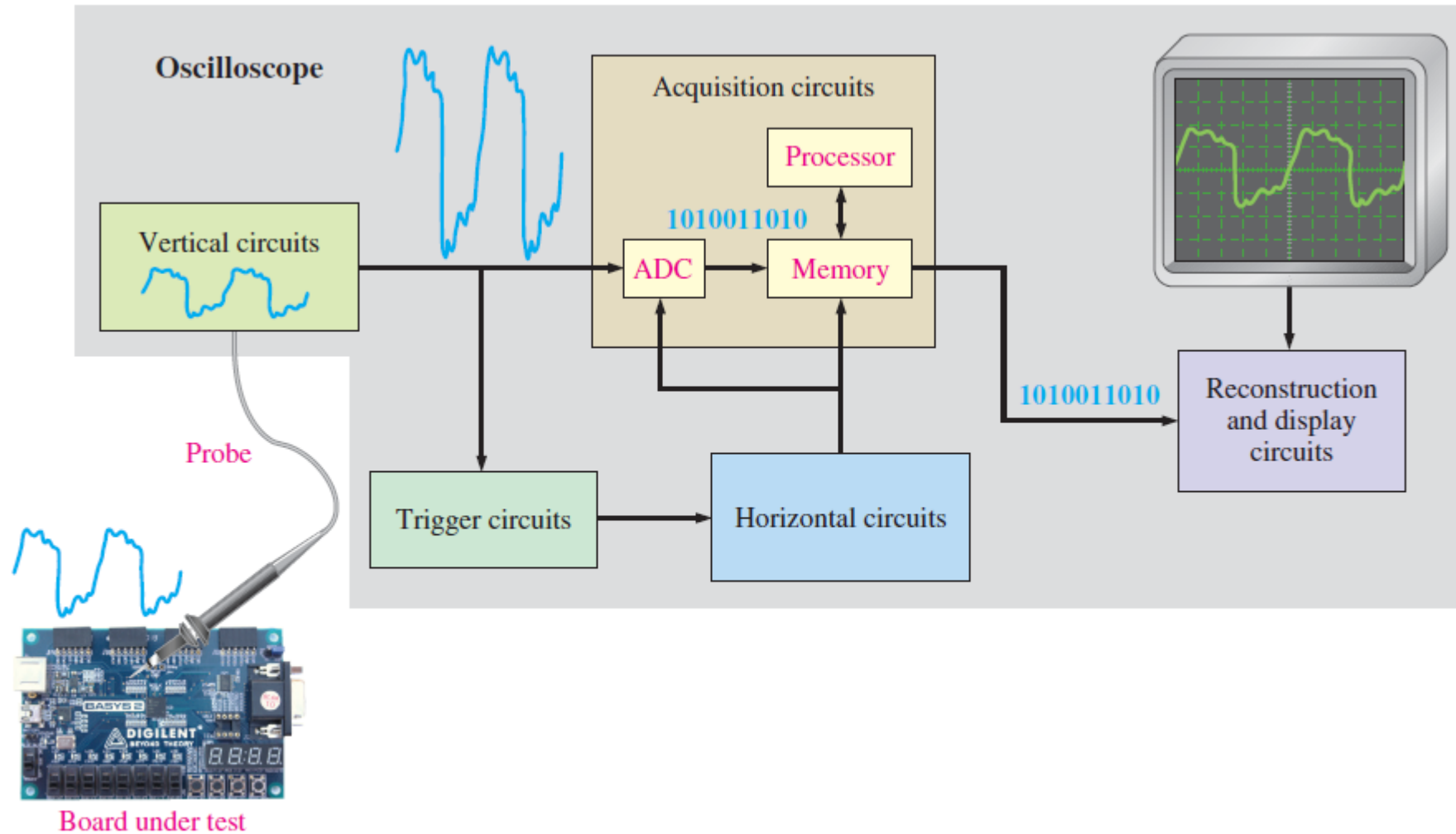

**FIGURE 1-43** Block diagram of a digital oscilloscope. (Photo courtesy of Digilent, Inc.)



# References

1. ***Digital Fundamentals*** by Thomas Floyd, Pearson International Edition, 11<sup>th</sup> Edition, Chapter 1, Page 16-54.





## Next class



# Number Systems and Operations