

CSE231L  
Class Assignment 04

**Task-1: Complete the data tables.**

**Task -2: Do the K-mapping for the required design in your notebook and attach their pictures here.**

**Task -3: Design the required BCD to Excess-3 converters in the logisim and attach their screenshots below.**

**Experimental Data**

Decimal Digit	Binary Coded Decimal (BCD)				Excess-3			
	W	X	Y	Z	A	B	C	D
<b>0</b>	0	0	0	0	0	0	1	1
<b>1</b>	0	0	0	1	0	1	0	0
<b>2</b>	0	0	1	0	0	1	0	1
<b>3</b>	0	0	1	1	0	1	1	0
<b>4</b>	0	1	0	0	0	1	1	1
<b>5</b>	0	1	0	1	1	0	0	0
<b>6</b>	0	1	1	0	1	0	0	1
<b>7</b>	0	1	1	1	1	0	1	0
<b>8</b>	1	0	0	0	1	0	1	1
<b>9</b>	1	0	0	1	1	1	0	0

**Table F1: Truth table - BCD to Excess-3**

<b>Number of inputs bits:</b>	4	<b>Input variables:</b>	W,X,Y,Z
<b>Number of outputs bits:</b>	4	<b>Output variables:</b>	A,B,C,D

**Table F2: System analysis**

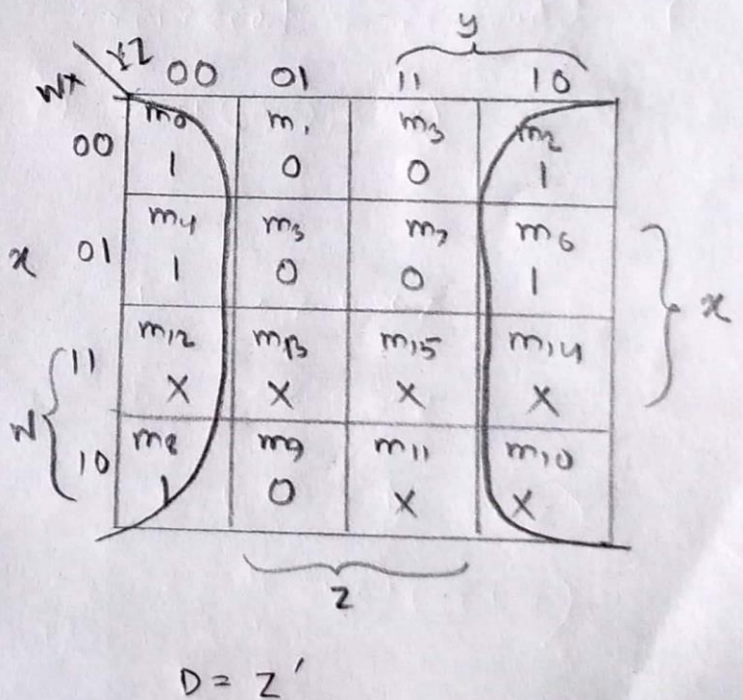
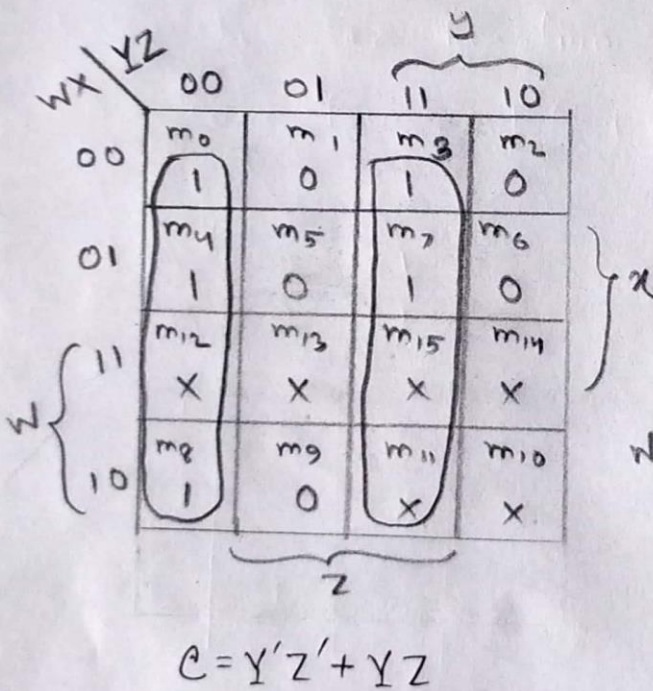
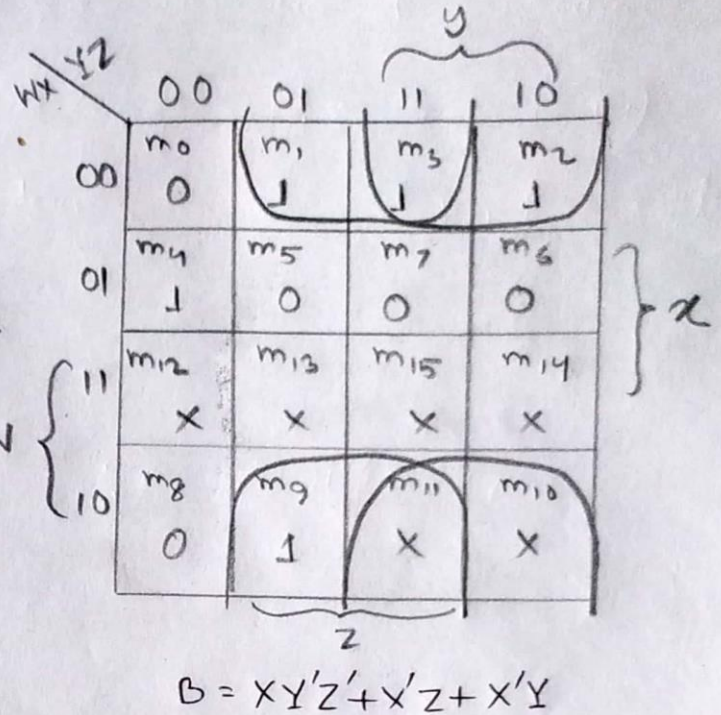
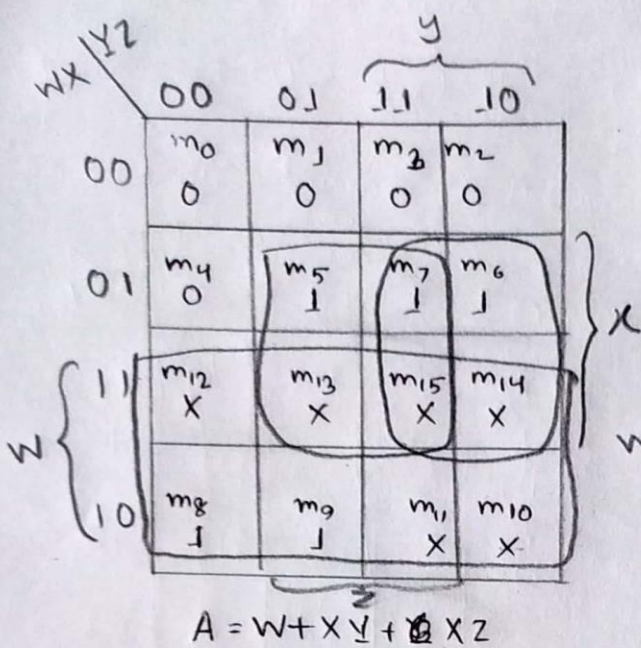


Figure F1: K-Maps

Name: Rafidul Islam, ID: 1912152642

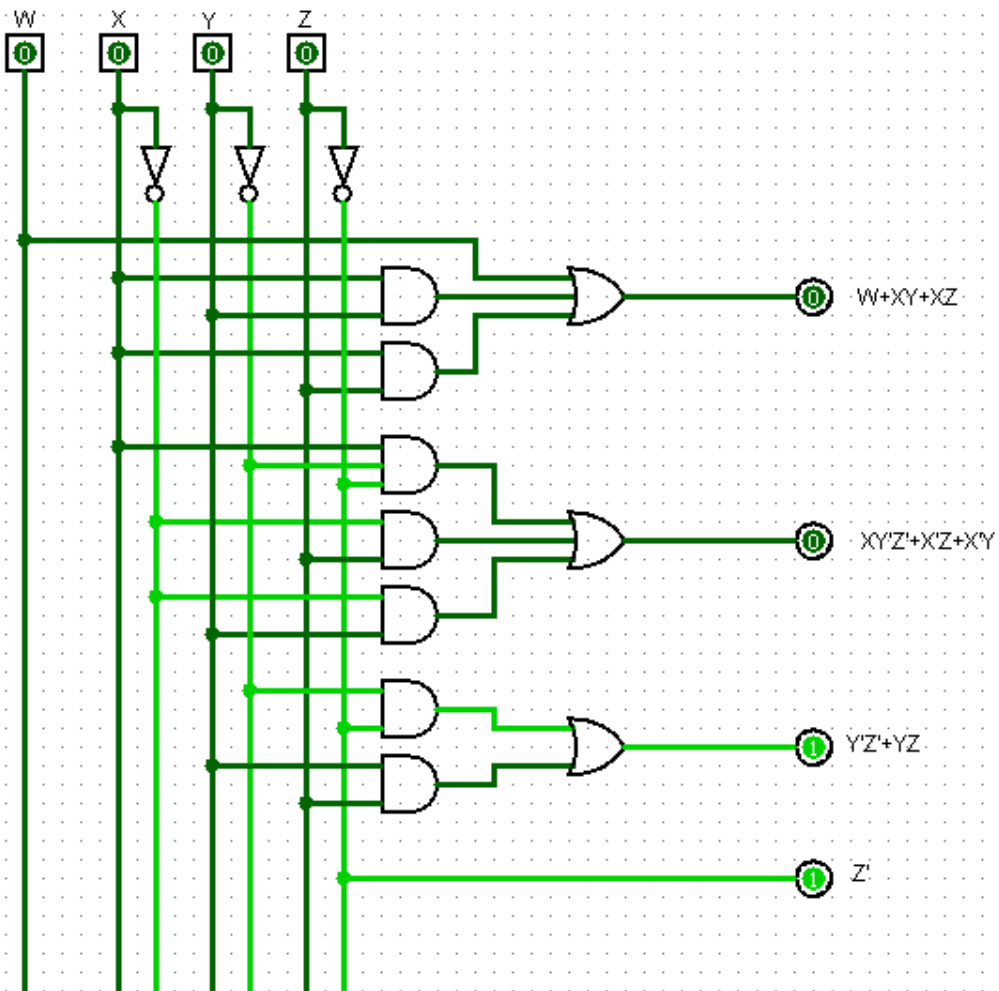


Figure F2: Minimal 1st canonical circuit of BCD to Excess-3 converter

**Figure F3: Minimal universal gate implementation of BCD to  
Excess-3 converter**