



Lecture – 3

Logic Gates

Lesson Outcomes

After completing this lecture, students will be able to

- *describe the operation of the inverter, the AND gate, and the OR gate*
- *describe the operation of the NAND gate and the NOR gate*
- *express the operation of NOT, AND, OR, NAND, and NOR gates with Boolean algebra*
- *describe the operation of the exclusive-OR and exclusive-NOR gates*
- *use logic gates in simple applications*



Key Terms

- ❑ **AND gate** A logic gate that produces a HIGH output only when all of the inputs are HIGH.
- ❑ **OR gate** A logic gate that produces a HIGH output when one or more inputs are HIGH.
- ❑ **NOT gate** A logic gate that inverts or complements its input.
- ❑ **NAND gate** A logic gate that produces a LOW output only when all the inputs are HIGH.
- ❑ **NOR gate** A logic gate in which the output is LOW when one or more of the inputs are HIGH.
- ❑ **Exclusive-NOR (XNOR) gate** A logic gate that produces a LOW only when the two inputs are at opposite levels.
- ❑ **Exclusive-OR (XOR) gate** A logic gate that produces a HIGH output only when its two inputs are at opposite levels.
- ❑ **Boolean algebra** The mathematics of logic circuits.
- ❑ **Truth table** A table showing the inputs and corresponding output(s) of a logic circuit.
- ❑ **Inverter** A logic circuit that inverts or complements its input.



Key Terms (continue)

- ❑ **CMOS** Complementary metal-oxide semiconductor; a class of integrated logic circuits that is implemented with a type of field-effect transistor.
- ❑ **EEPROM** A type of nonvolatile PLD reprogrammable link based on electrically erasable programmable read-only memory cells and can be turned on or off repeatedly by programming.
- ❑ **EPROM** A type of PLD nonvolatile programmable link based on electrically programmable read-only memory cells and can be turned either on or off once with programming.
- ❑ **SRAM** A type of PLD volatile reprogrammable link based on static random-access memory cells and can be turned on or off repeatedly with programming.
- ❑ **Propagation delay time** The time interval between the occurrence of an input transition and the occurrence of the corresponding output transition in a logic circuit.
- ❑ **VHDL** A standard hardware description language that describes a function with an entity/architecture structure.




Common logic term

TABLE 3-1 Common logic terms.

Logic 0	Logic 1
False	True
Off	On
LOW	HIGH
No	Yes
Open switch	Closed switch

Operation of OR gate


 


Symbol of TWO input OR gate


Truth Table

A	B	$x = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

Internal structure

  

Boolean expression: $x = A + B + C$

 


Symbol of THREE input OR gate

Truth Table


A	B	C	$x = A + B + C$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Operation of OR gate (contd..)

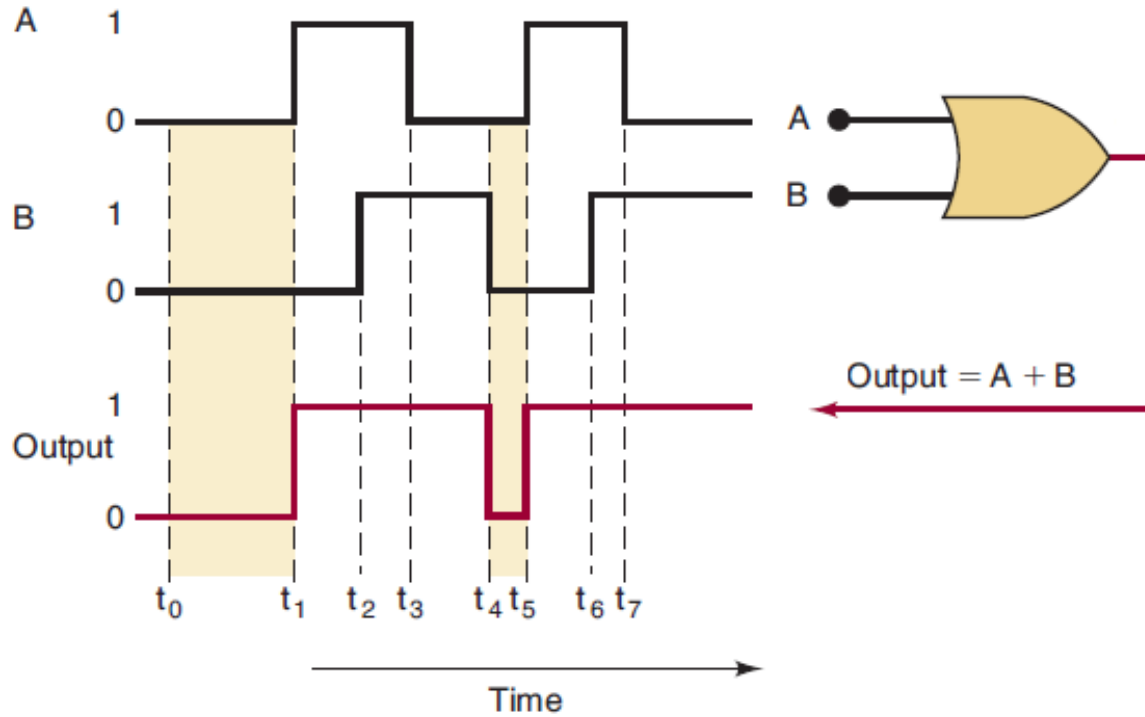


TWO input OR operation


THREE input OR operation

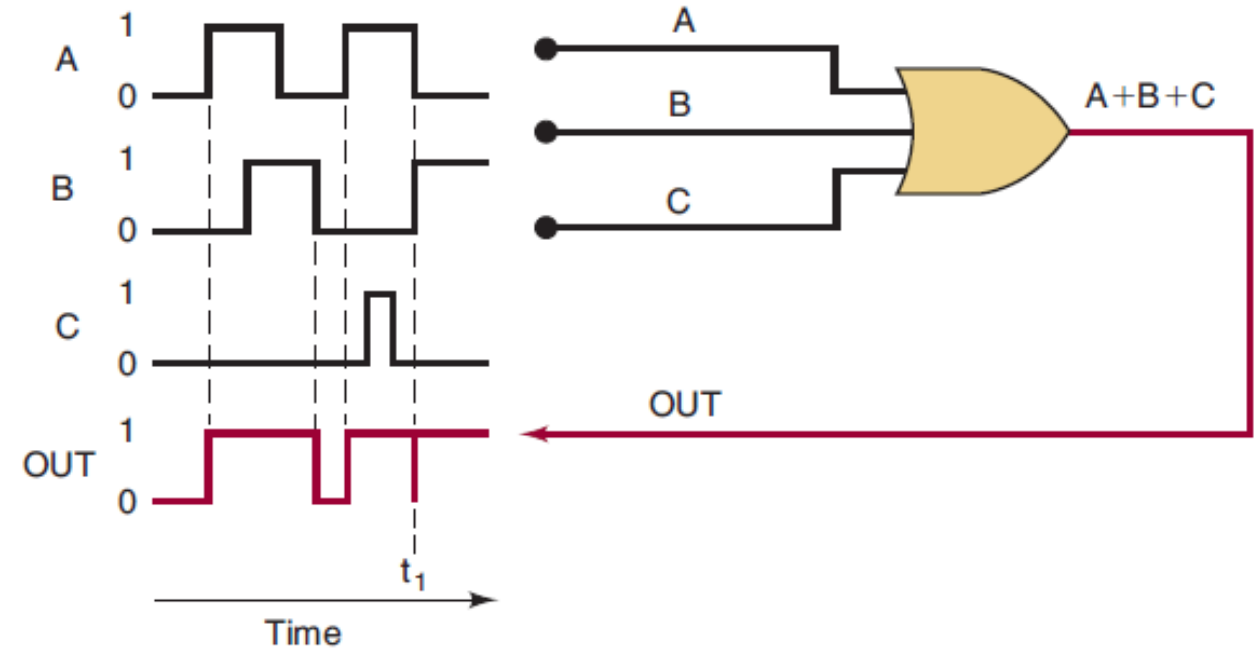

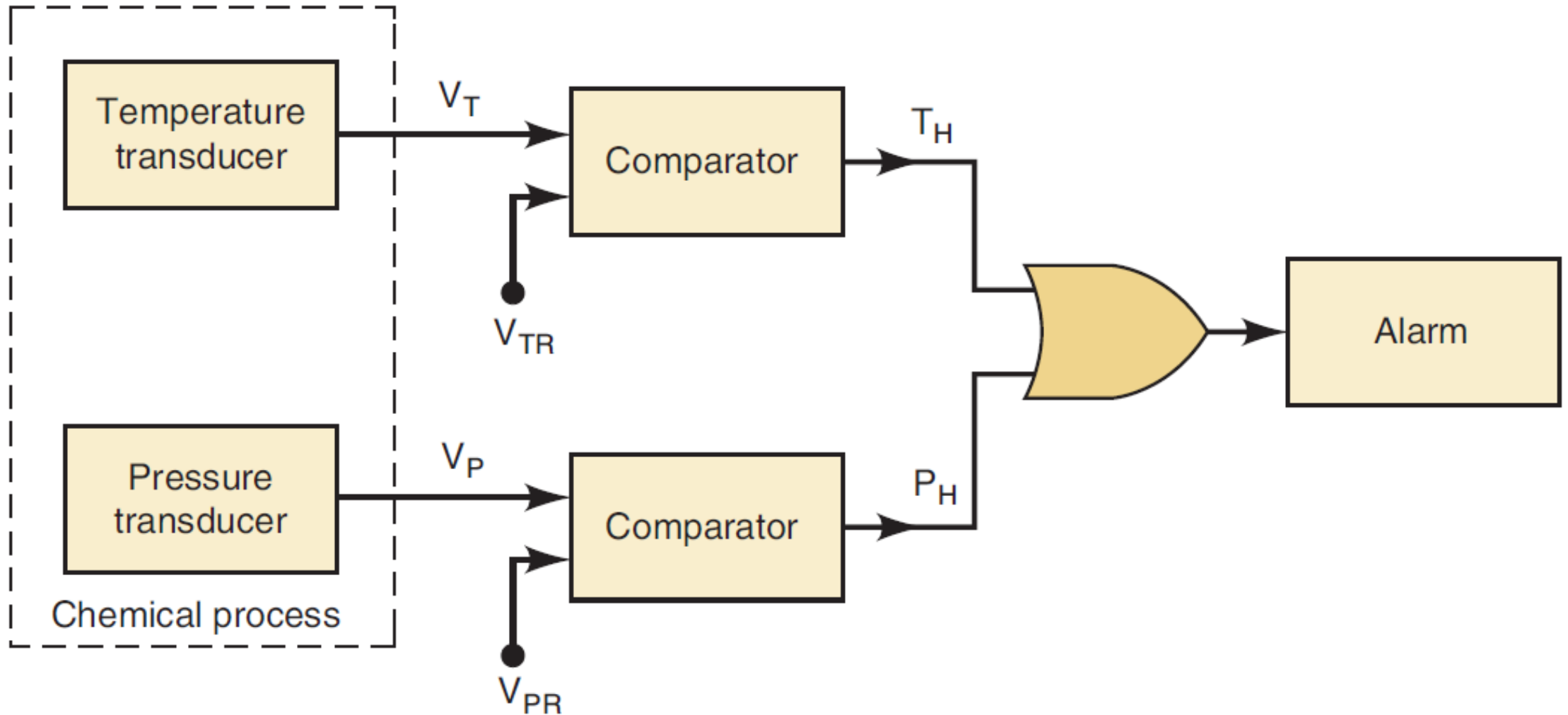OR GATE application – alarms system in chemical process



Operation of AND gate

 



Symbol of TWO input **AND** gate

Boolean expression: $x = A \cdot B$

Truth
Table


A	B	$x = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

Internal
structure

  

Operation of AND gate

 Boolean expression: $x = A \bullet B \bullet C$




Symbol of THREE input AND gate


Truth Table

A	B	C	$x = ABC$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1



Operation of AND gate

 

TWO input **AND** operation

 

TWO input **AND** operation

  


Operation of NOT gate


NOT

A	$x = \bar{A}$
0	1
1	0

(a)

 


(b)

 


(c)

Internal structure

 


Boolean expression of NOT operation: $x = \bar{A}$


Logic circuits with Boolean expression

 


(a)

 

(b)

 


(a)

 


(b)

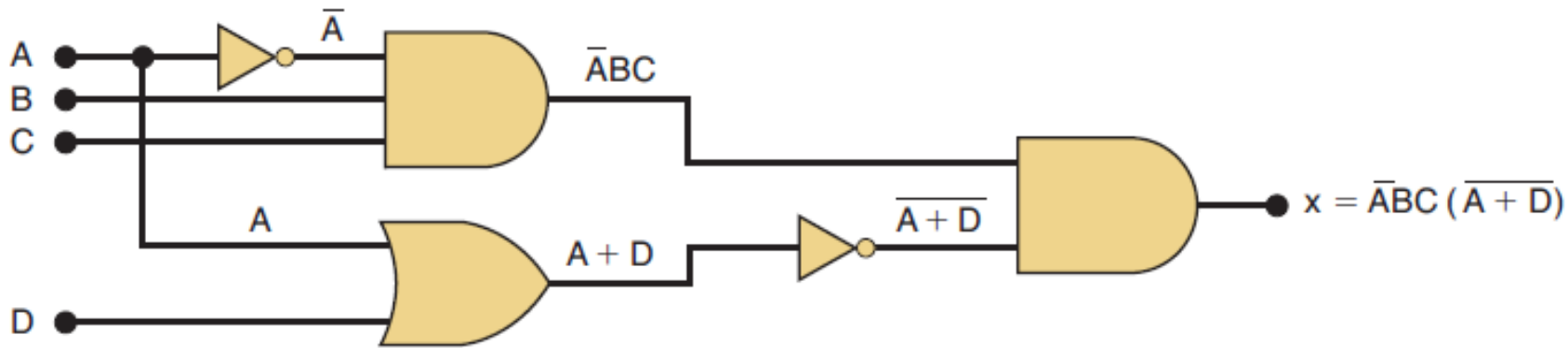Logic circuits with Boolean expression (contd..)




(a)

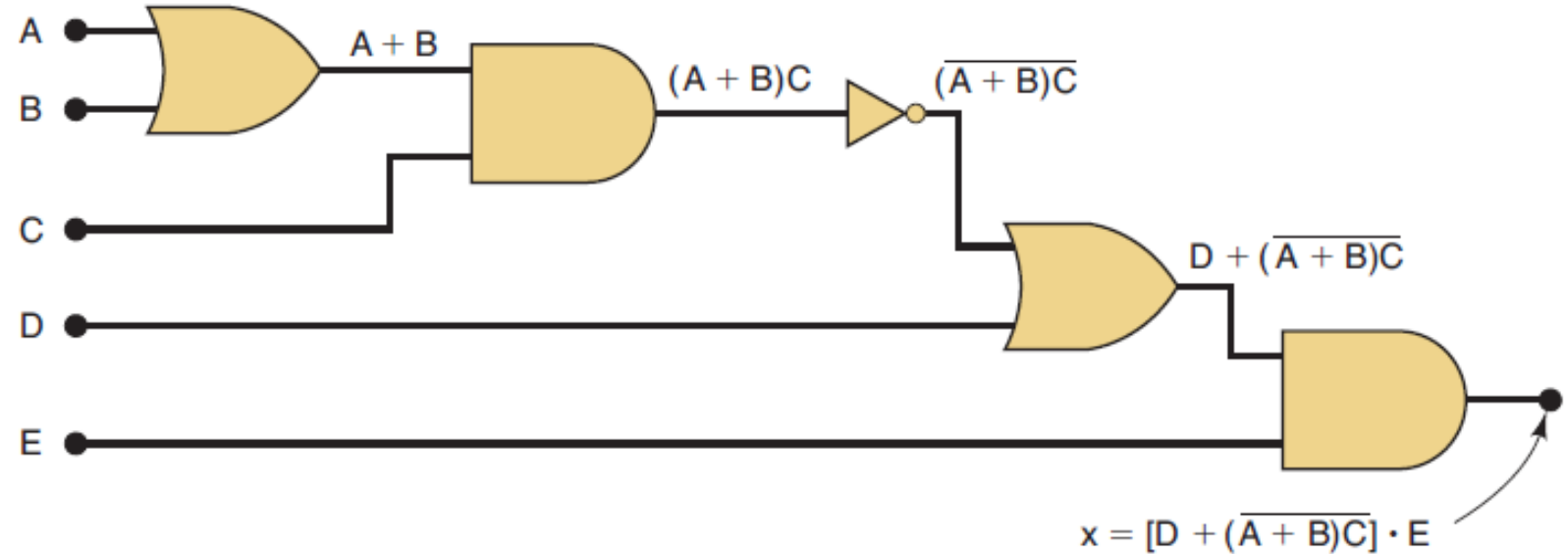

(b)



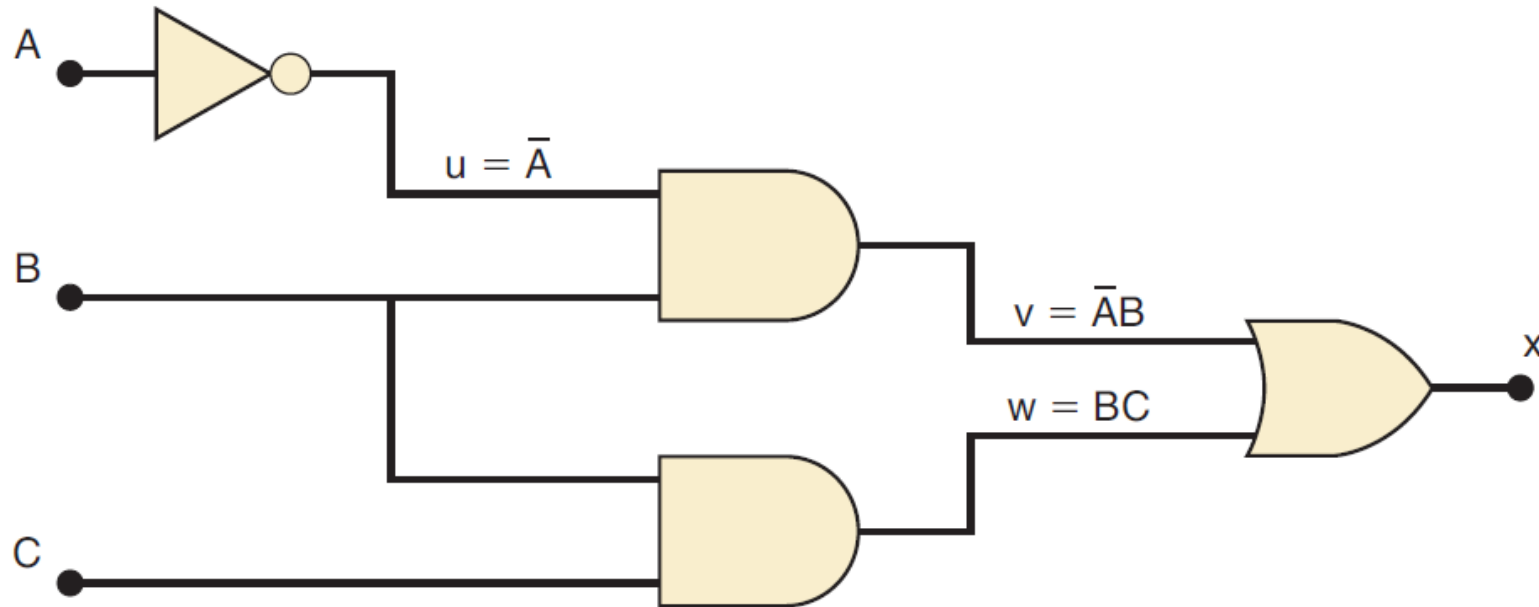Logic circuits with Boolean expression (contd..)




A	B	C	$\underline{u} = \bar{A}$	$\underline{v} = \bar{A}B$	$w = BC$	$x = v + w$
0	0	0	1	0	0	0
0	0	1	1	0	0	0
0	1	0	1	1	0	1
0	1	1	1	1	1	1
1	0	0	0	0	0	0
1	0	1	0	0	0	0
1	1	0	0	0	0	0
1	1	1	0	0	1	1

Constructing logic circuit from Boolean expression

PROBLEM Construct a logic circuit from Boolean expression: $y = AC + B\bar{C} + \bar{A}BC$

SOLUTION

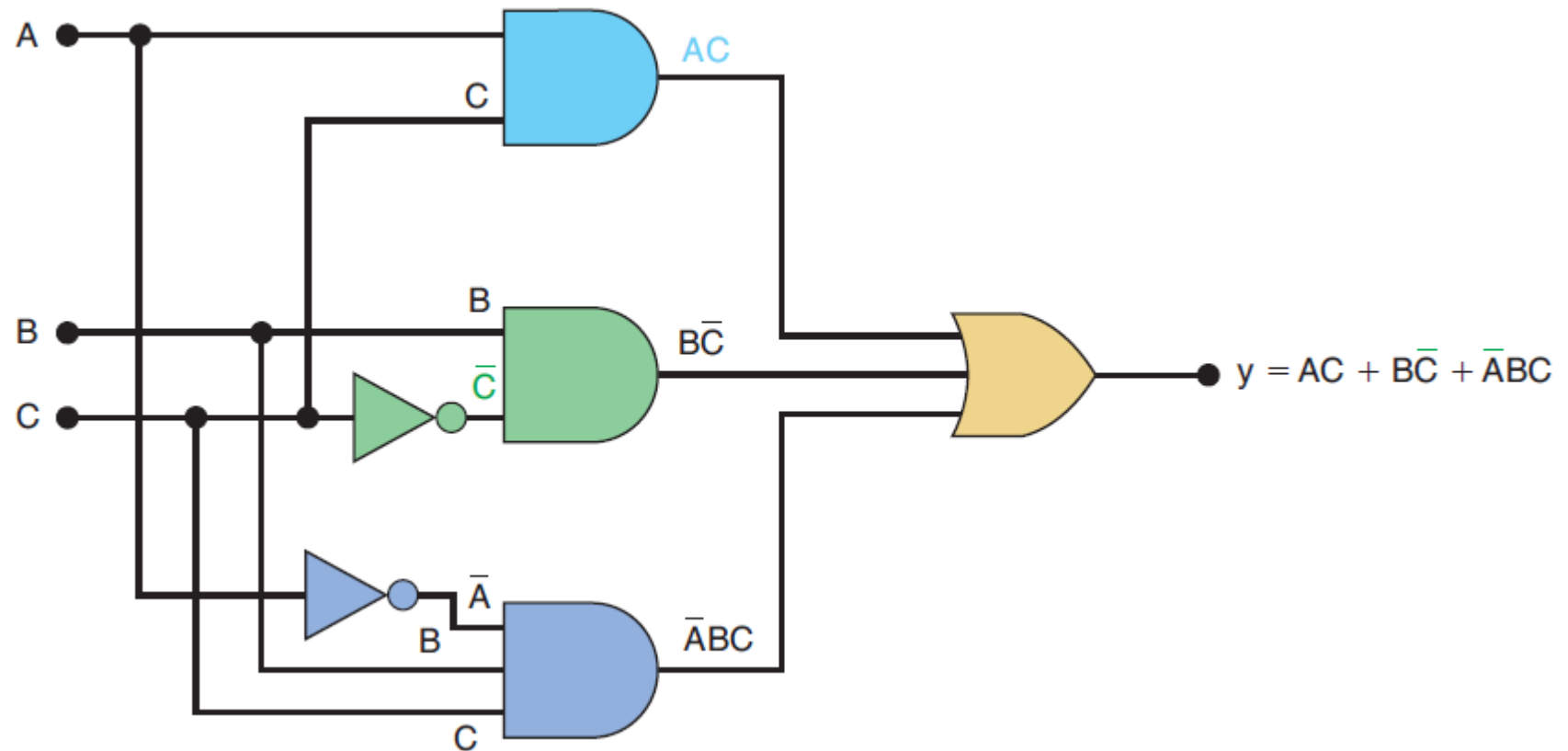





Constructing logic circuit from Boolean expression

PROBLEM Construct a logic circuit from Boolean expression: $x = (A + B)(\bar{B} + C)$

SOLUTION


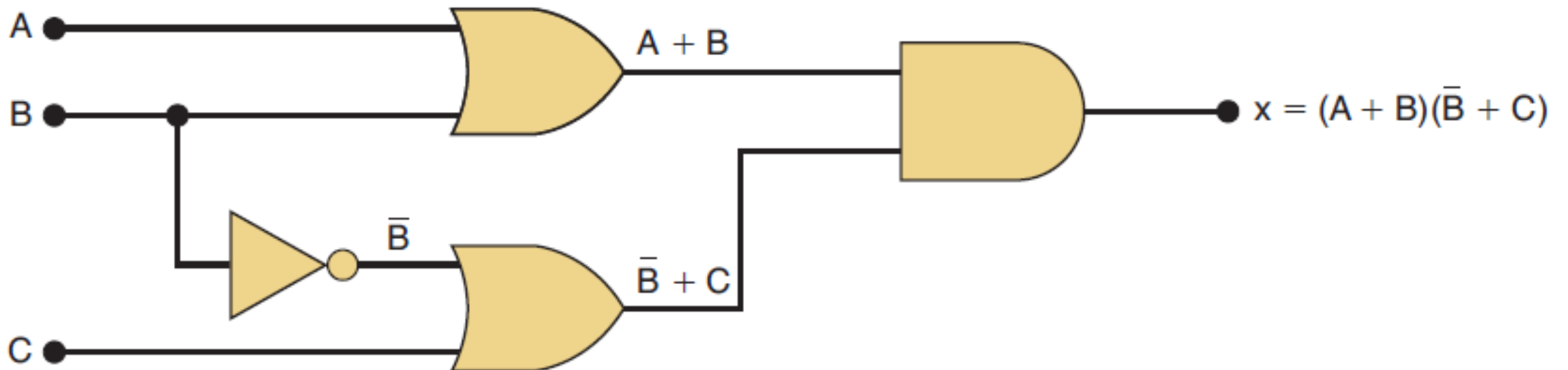


NOR operation


 


OR + NOT = NOT OR = NOR

		OR		NOR	
A	B		$A + B$		$\overline{A + B}$
0	0		0		1
0	1		1		0
1	0		1		0
1	1		1		0

 
 


NAND operation

 
 


AND + NOT = NOT AND = NAND

A	B	AND		NAND	
		AB		\overline{AB}	
0	0	0		1	
0	1	0		1	
1	0	0		1	
1	1	1		0	

  


  PROBLEM. Two tanks store certain liquid chemicals that are required in a manufacturing process. Each tank has a sensor that detects when the chemical level drops to 25% of full. It is required that a **green** LED on an indicator panel show when both tanks are more than one-quarter full. A **red** LED light will TURN ON when at least one of the tanks falls to the quarter-full level. Show how these requirements can be implemented.



NAND application

 PROBLEM. As part of an aircraft's functional monitoring system, a circuit is required to indicate the status of the landing gears prior to landing. A **green** LED display turns on if all three gears are properly extended when the "gear down" switch has been activated in preparation for landing. A **red** LED display turns on if any of the gears fail to extend properly prior to landing. When a landing gear is extended, its sensor produces a LOW voltage. When a landing gear is retracted, its sensor produces a HIGH voltage. Implement a circuit to meet this requirement.



Boolean theorems


 


FIGURE 3-25 Single-variable theorems.

 

Boolean theorems – multivariable theorems

Multivariable Theorems

The theorems presented below involve more than one variable:

$$(9) \quad x + y = y + x$$

$$(10) \quad x \cdot y = y \cdot x$$

$$(11) \quad x + (y + z) = (x + y) + z = x + y + z$$

$$(12) \quad x(yz) = (xy)z = xyz$$

$$(13a) \quad x(y + z) = xy + xz$$

$$(13b) \quad (w + x)(y + z) = wy + xy + wz + xz$$

$$(14) \quad x + xy = x$$

$$(15a) \quad x + \bar{x}y = x + y$$

$$(15b) \quad \bar{x} + xy = \bar{x} + y$$

Exclusive OR gate


 
 


TABLE 3-11

Truth table for an exclusive-OR gate.

Inputs		Output
<i>A</i>	<i>B</i>	<i>X</i>
0	0	0
0	1	1
1	0	1
1	1	0

 



Exclusive NOR




TABLE 3-12

Truth table for an exclusive-NOR gate.


Inputs		Output
<i>A</i>	<i>B</i>	<i>X</i>
0	0	1
0	1	0
1	0	0
1	1	1

  


NAND as universal gate

 


(a)

 


INVERTER

 


(b)

 

AND

 


(c)


 


OR



NOR as universal gate

 


(a)

  


(b)

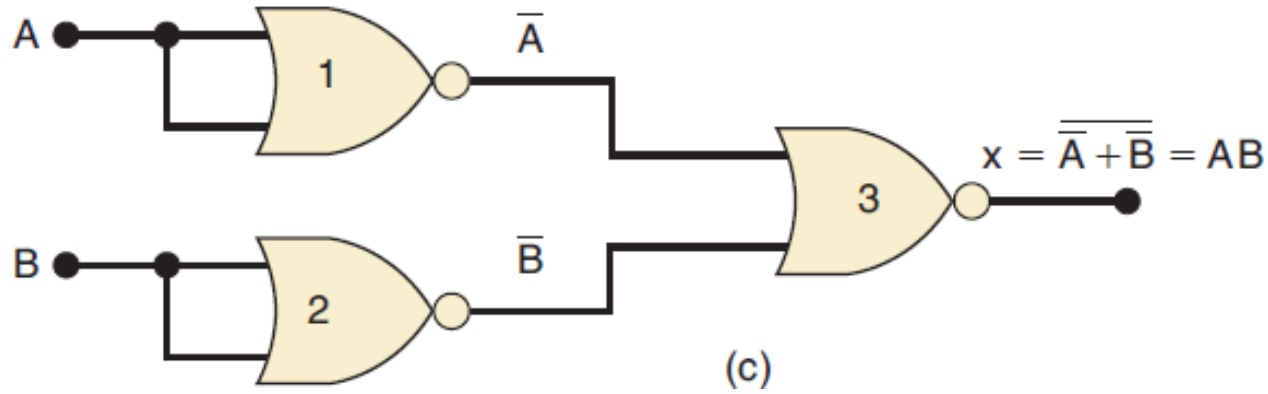 



(c)

 

Standard alternate symbols

 

Logic gates summary

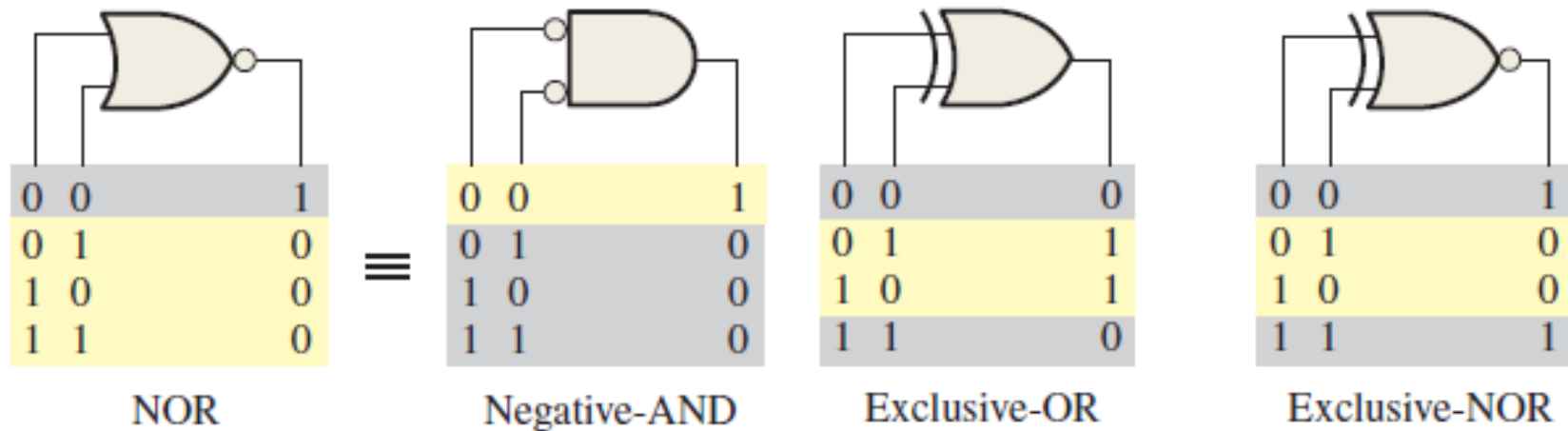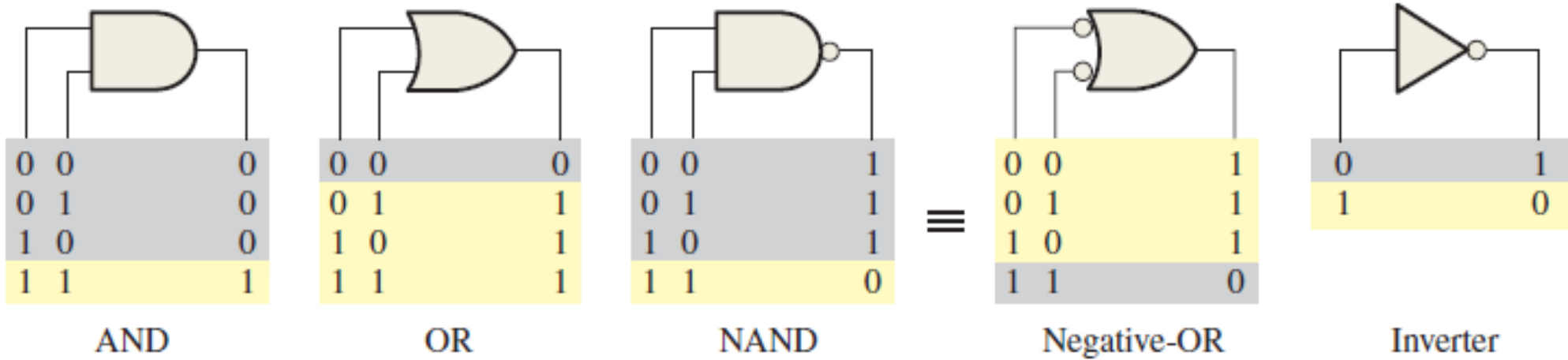



References

1. ***Digital Fundamentals*** by Thomas Floyd, Pearson International Edition, 11th Edition, Chapter 3, Page 125-170.
2. ***Digital Systems: Principles and Applications*** by Ronald Tocci, Neal Widmer and Greg Moss, Pearson International Edition, 12th Edition, Chapter 3, Page 68-90.



Next class



Boolean Algebra And Logic Simplification