

ETE 211/EEE 211


Digital Logic Design

Synchronous Sequential Logic - Analysis

Analysis of Clocked Sequential Circuits

- The analysis of a sequential circuit consists of obtaining a **table** or a **diagram for the time sequence of inputs, outputs, and internal states**.
- It is also possible to write **Boolean** expressions that describe the behavior of the sequential circuit.
- These expressions must include the necessary time sequence, either directly or indirectly.
- The behavior of a clocked sequential circuit can be described algebraically by means of state equations.
- **State equation** specifies the next state as a function of the present state and inputs.
 - ✓ A state equation is an algebraic expression that specifies the condition for a flip-flop state transition.
 - ✓ The left side of the equation with $(t+1)$ denotes the next state of the flip-flop one clock edge later.
 - ✓ The right side of the equation is Boolean expression that specifies the present state and input conditions that make the next state TRUE.

Example of Sequential Circuit

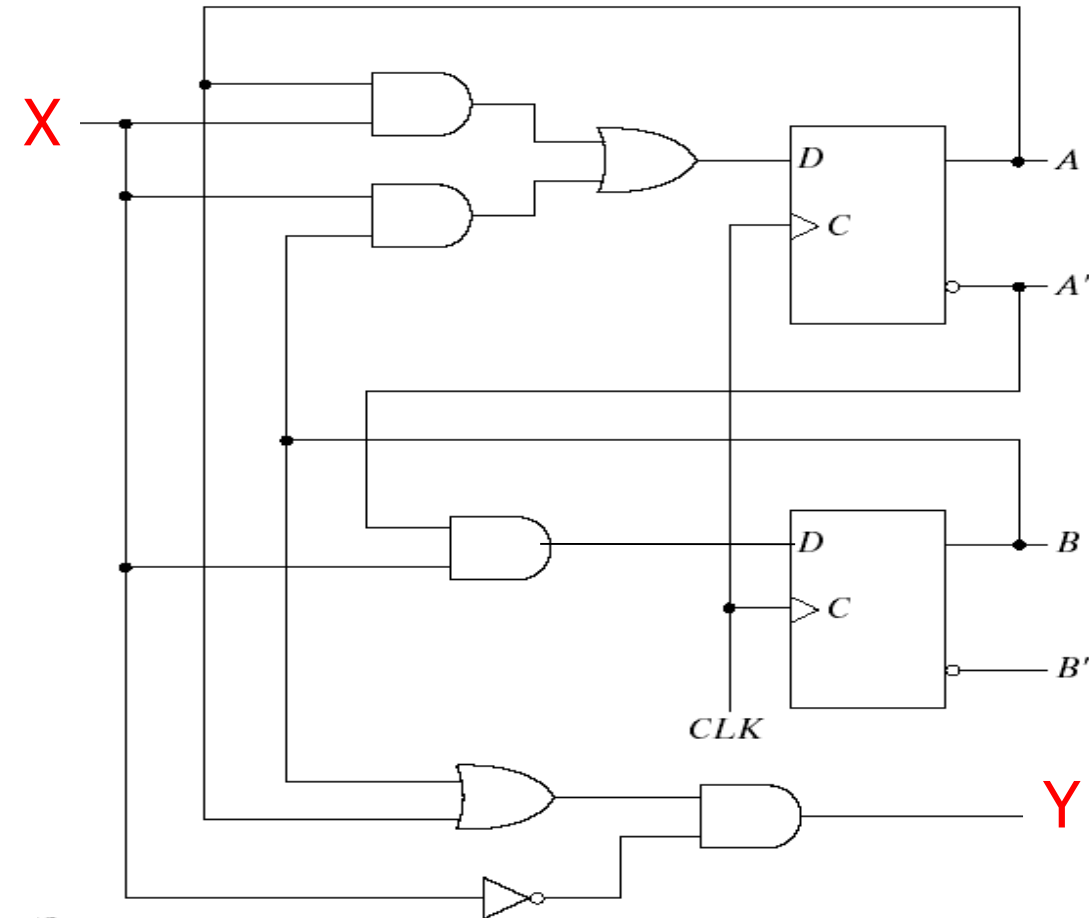

State Equation

$$A(t+1) = A(t) x(t) + B(t) x(t)$$

$$B(t+1) = A'(t) x(t)$$

$$Y(t) = (A(t) + B(t)) x(t)'$$

- This sequential circuit consists of two D flip-flops A and B, an input X and an output Y.


State Table

The time sequence of inputs, outputs, and flip-flop states can be enumerated in a **state table** (sometimes called **transition table**).

Present State		Input X	Next State		Output Y
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

State Diagram

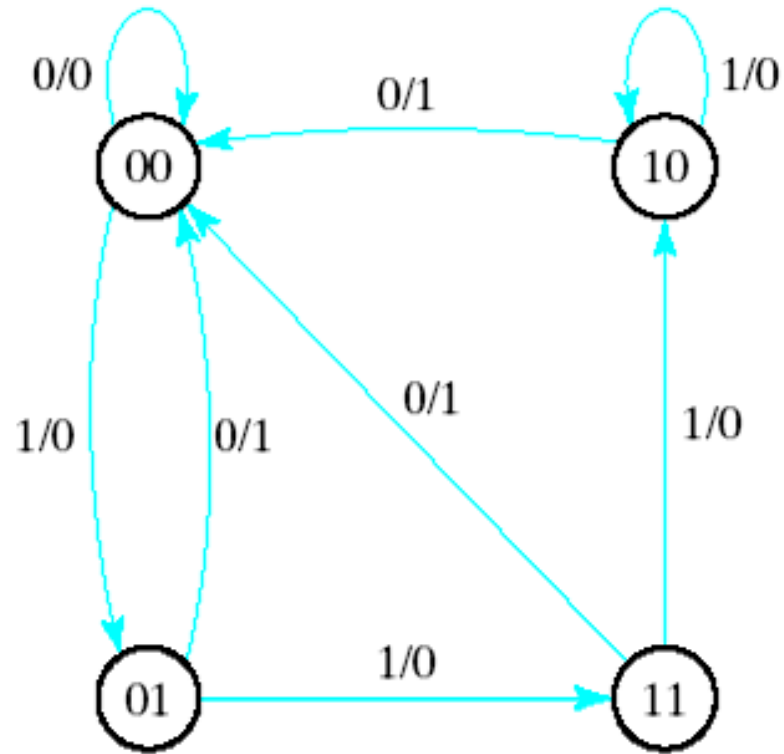- The information available in a state table can be represented graphically in the form of a **state diagram**.
- A state is represented by a circle, and the transitions between states are indicated by directed lines connecting the circles.




1/0 : means input =1
output=0

Flip-Flop Input Equations

- The part of the combinational circuit that generates external outputs is described algebraically by a set of Boolean functions called **output equations**.
- The part of the circuit that generates the inputs to flip-flops is described algebraically by a set of Boolean functions called flip-flop **input equations**.
- The logic diagram of the circuit can be expressed algebraically with **two flip-flop input equations** and **an output equation**:

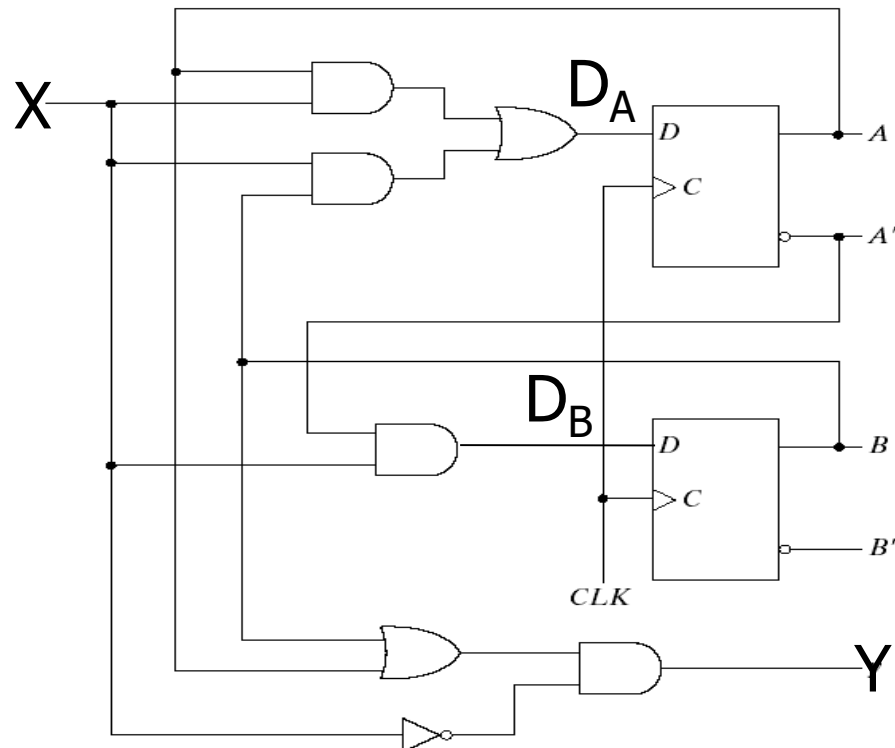
$$\begin{aligned}D_A &= AX + BX \\D_B &= A'X \\y &= (A + B)X'\end{aligned}$$



Analysis with D Flip-Flop

The circuit we want to analyze is described by the input equation $D_A = A \oplus x \oplus y$

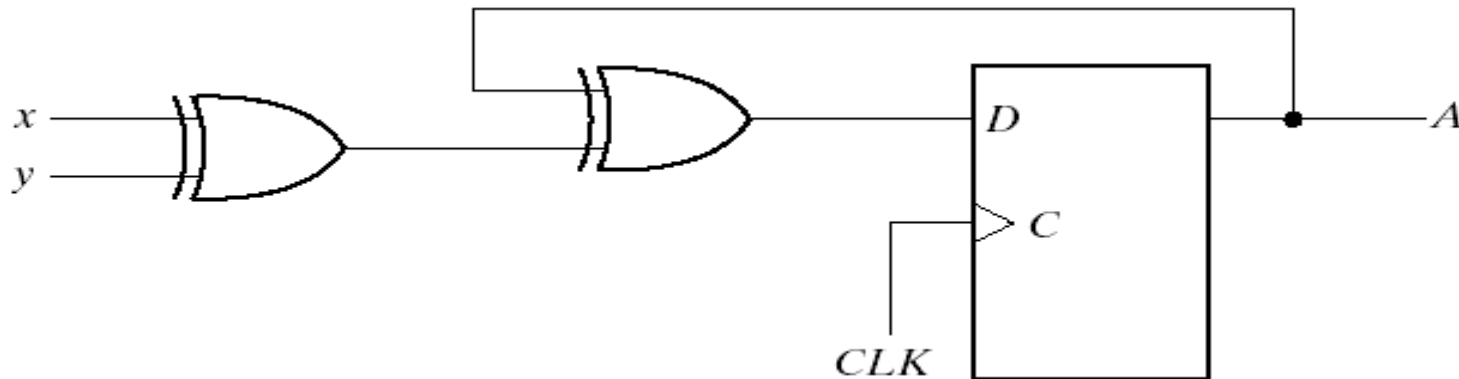- The D_A symbol implies a D flip-flop with output A.
- The x and y variables are the inputs to the circuit.
- No output equations are given, so the output is implied to come from the output of the flip-flop.




Analysis with D Flip-Flop

- The binary numbers under Axy are listed from 000 through 111
- The next state values are obtained from the state equation

$$A(t+1) = A \oplus x \oplus y$$
- The state diagram consists of two circles-one for each state

Present state	Inputs		Next state
A	x	y	A
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(b) State table

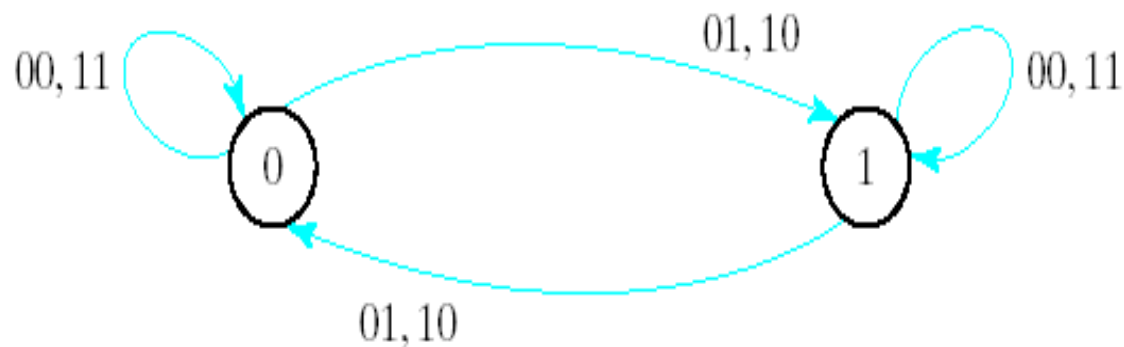


(c) State diagram

Analysis With T Flip-Flops


Characteristic equation

$$Q(t + 1) = T \oplus Q = T'Q + TQ'$$

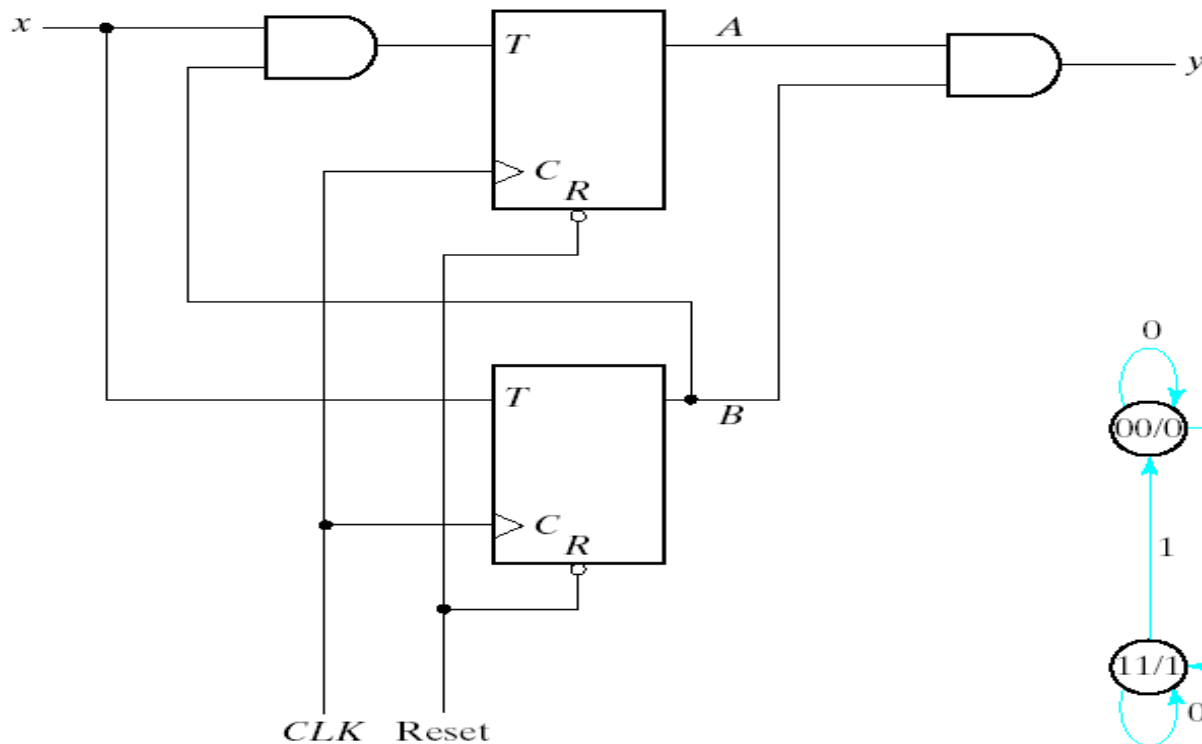

(a) Circuit diagram

00/0 : means
state is 00
output is 0

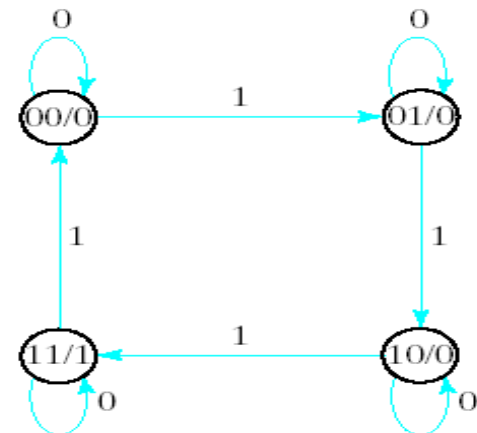

(b) State diagram

Analysis With T Flip-Flops

Two flip-flops A and B, one input x, and one output y.

Two input equations and an output equation:

$$T_A = Bx$$

$$T_B = x$$

$$y = AB$$

$$A(t+1) = (Bx)'A + (Bx)A'$$

$$= AB' + Ax' + A'Bx$$

$$B(t+1) = x \oplus B$$

Table 5-5

State Table for Sequential Circuit with T Flip-Flops

Present State		Input	Next State		Output
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	1