

Class Assignment 08

Complete the class work and attach the screenshots/images at the end.

F.1 Experimental Data: Constructing a Sequential Circuit using T Flip-Flops

Present state		Input	Next state		Output	Flip-flop input functions	
A	B	X	A	B	Y	T _A	T _B
0	0	0	0	1	0	0	1
0	0	1	1	0	1	1	0
0	1	0	0	1	0	0	0
0	1	1	1	0	1	1	1
1	0	0	1	0	0	0	0
1	0	1	0	0	0	1	0
1	1	0	X	X	X	X	X
1	1	1	X	X	X	X	X

Table F.2.1: State Table for circuit using T Flip-Flops

0	1	1	0
0	1	X	X

$$T_A = X$$

1	0	1	0
0	0	X	X

$$T_B = A'B'X' + BX$$

0	1	1	0
0	0	X	X

$$Y = A'X$$

Name: Rafidul Islam, ID: 1912152642

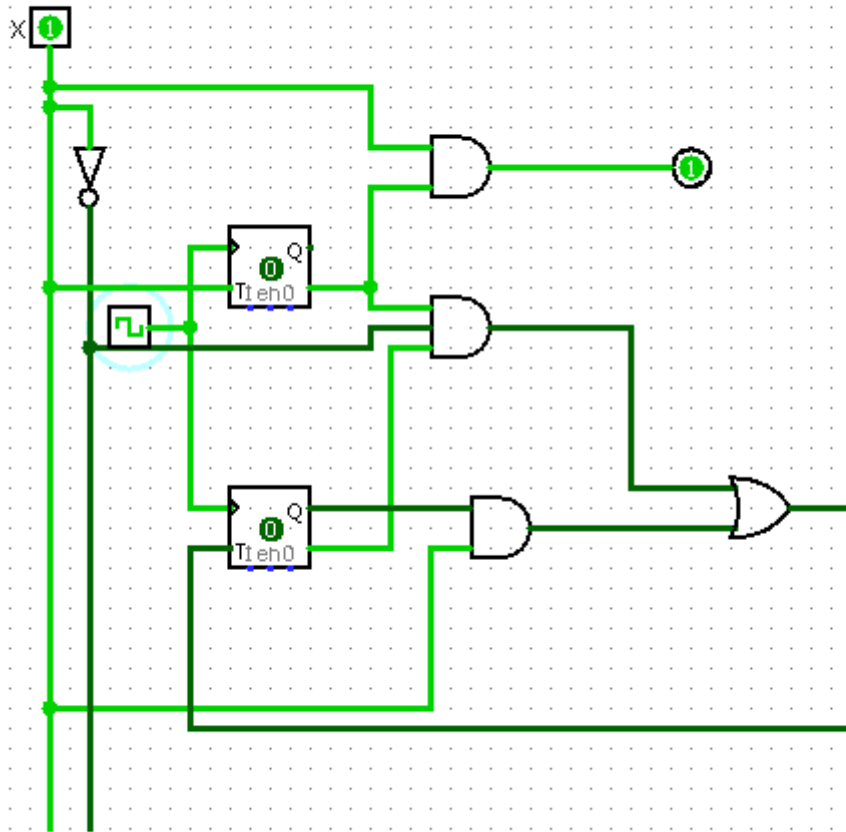


Figure F.2.1: Circuit Diagram

F.2 Experimental Data: Constructing a Sequential Circuit using D Flip-Flops

Present state		Input	Next state		Output	Flip-flop input functions	
A	B	X	A	B	Y	D _A	D _B
0	0	0	1	1	0	1	1
0	0	1	0	1	0	0	1
0	1	0	1	1	0	1	1
0	1	1	0	0	0	0	0
1	0	0	1	0	0	1	0
1	0	1	1	1	1	1	1
1	1	0	1	0	0	1	0
1	1	1	1	0	1	1	0

Table F.3.1: State Table for circuit using D Flip-Flops

1	0	0	1
1	1	1	1

$$D_A = x' + A$$

1	1	0	1
0	1	0	0

$$D_B = A'x' + B'x$$

0	0	0	0
0	1	1	0

$$Y = Ax$$

Name: Rafidul Islam, ID: 1912152642

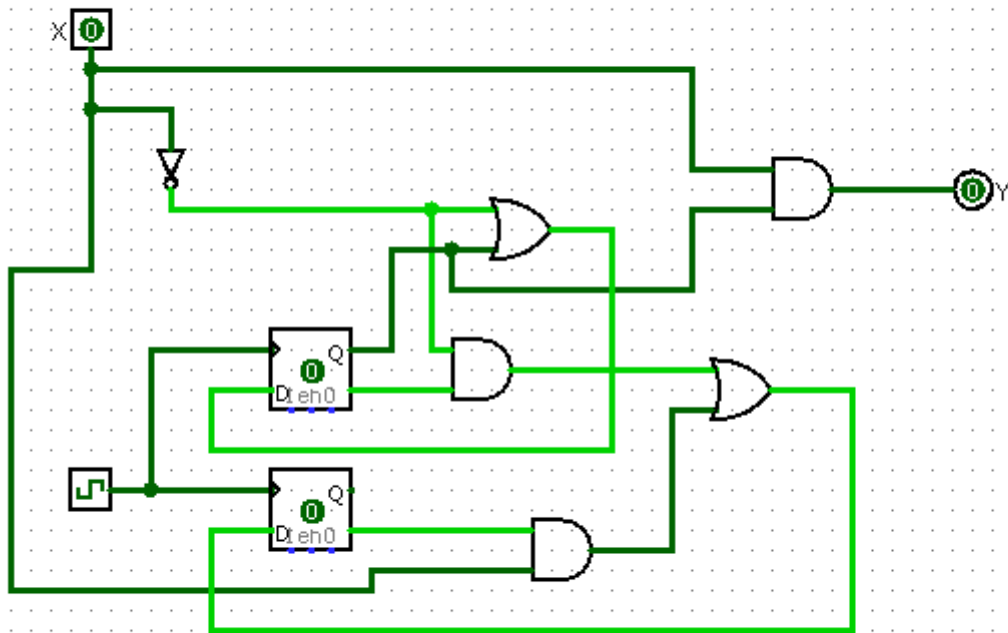


Figure F.3.1: Circuit Diagram